



**SRI CHANDRASEKHARENDRASARASWATHI VISWA
MAHAVIDYALAYA**

(University established under section 3 of UGC Act 1956)

(Accredited with 'A' Grade by NAAC)

Enathur, Kanchipuram – 631 561

DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

**Lab Manual
VLSI Design Lab
B.E(FULL TIME) III YEAR, VIth SEMESTER**

Prepared by:

G.Poornima, Assistant Professor




Index

EX.NO	NAME OF THE EXPERIMENTS	PAGE NO	SIGN
	CYCLE- I Tools- XILINX ISE 14.1		
1	Design Entry and Simulation of Combinational Circuits		
2	Place and Route and Post Place & Route Simulation		
3	Design and FPGA Implementation of Combinational		
4	Design and FPGA Implementation of Sequential Circuits		
5	Analysis of Area, Power and Delay For Sequential		
6	Invoke PLL to generate Real Time Clock		
	CYCLE-II Tools – LT-SPICE and ELECTRIC VLSI System Design EDA		
7	Ring Oscillator		
8	Differential Amplifier		
9	CMOS Inverter		
10	Layout CMOS Inverter		
11	CMOS Inverter – Place and Route		
12	Layout CMOS NAND Gate		
	Study Experiments Tools- Synopsys		
13	Static Timing Analysis		
14	DFT-Scan Chain Insertion		

XILINX SPARTAN 3E TRAINER KIT

 The Spartan-3E Trainer Kit is a demonstration platform intended to become familiar with the new features and availability of the Spartan-3E FPGA family. This Kit provides a easy-to-use development and evaluation platform for Spartan-3E FPGA designs.



Slide Switch connections with FPGA - INPUT PIN

SWITCHES	FPGA PINS
SW4	T14
SW5	T12
SW6	T9
SW7	T7
SW8	T2
SW9	G12
SW10	H1
SW11	R3
SW12	N11
SW13	N3
SW14	M13
SW15	M7
SW16	M3
SW17	K4
SW18	J12
SW19	J11

OUTPUT PINS

LEDS	FPGA PINS
L16	R1
L15	R2
L14	K3
L13	T4
L12	T5
L11	R6
L10	T8
L9	R10
L8	N10
L7	P12
L6	N9
L5	N12
L4	P13
L3	R13
L2	T13
L1	P14


Procedure for simulation and implementation of Xilinx tool and FPGA

STEP 1:


Click Xilinx ISE 9.1

STEP 2:

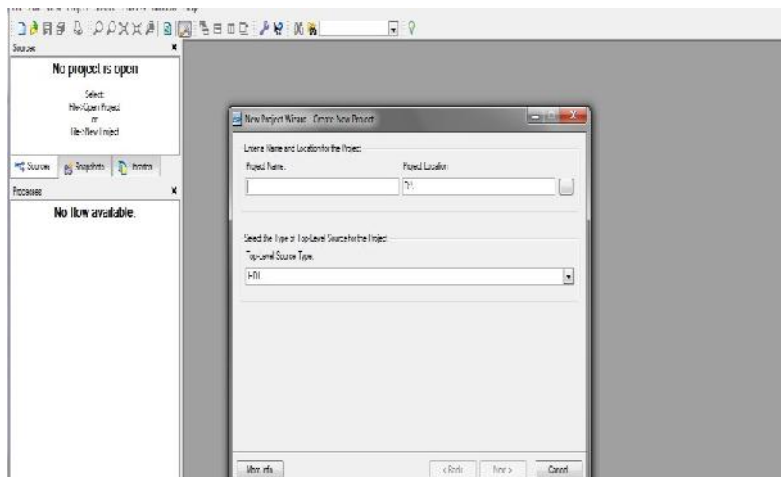
File->New project and type the project name and check the top level source type as HDL



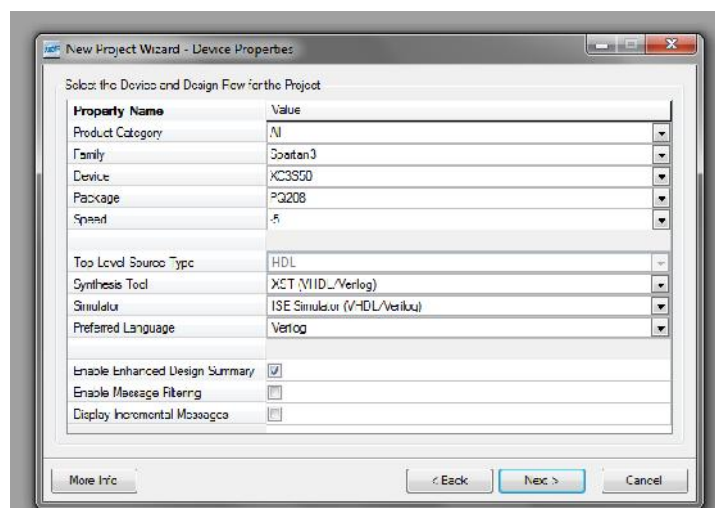STEP 3: Check the device properties and click next




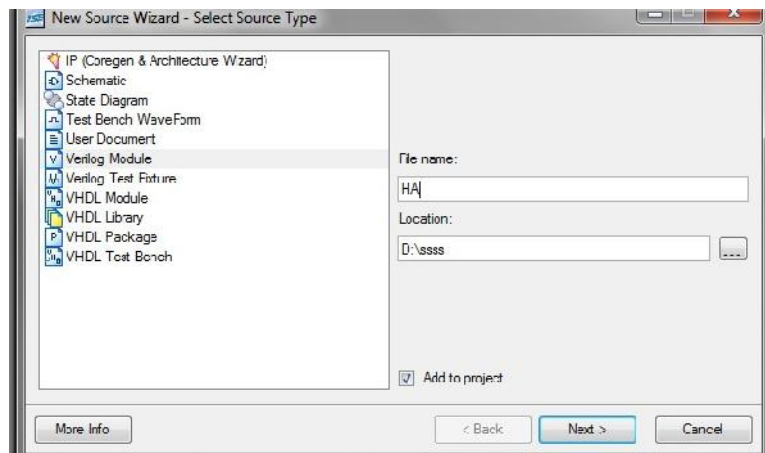STEP4: Click New Source And Select the Verilog Module and then give the filename




STEP5:

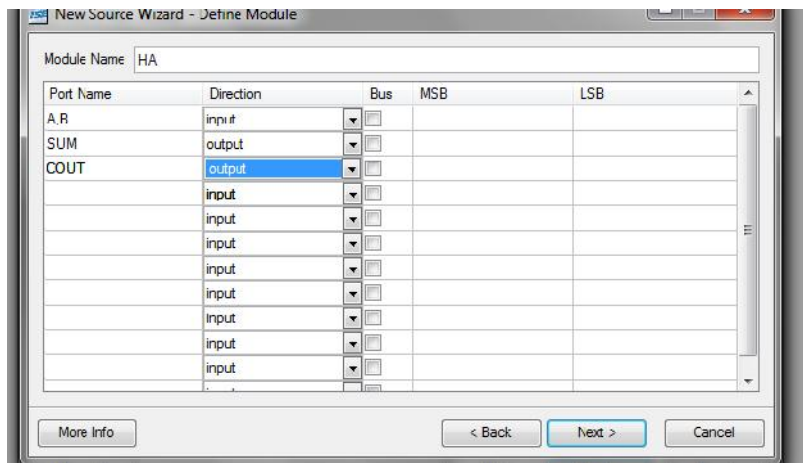Select the Input, Output port names and click finish.




STEP6:


Type the program and save it

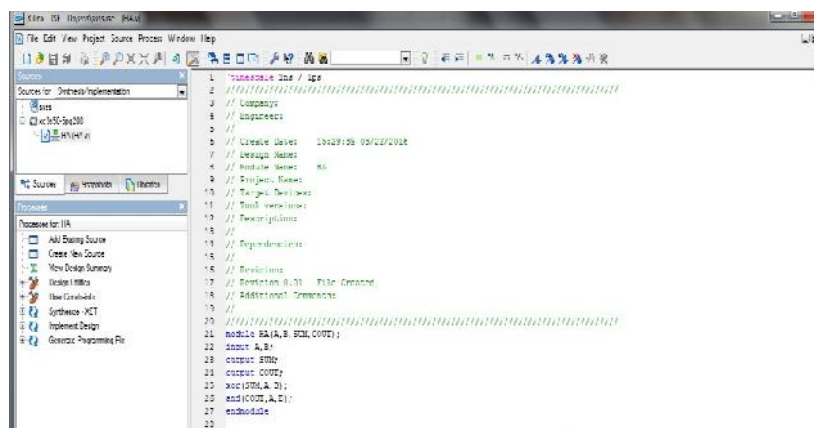

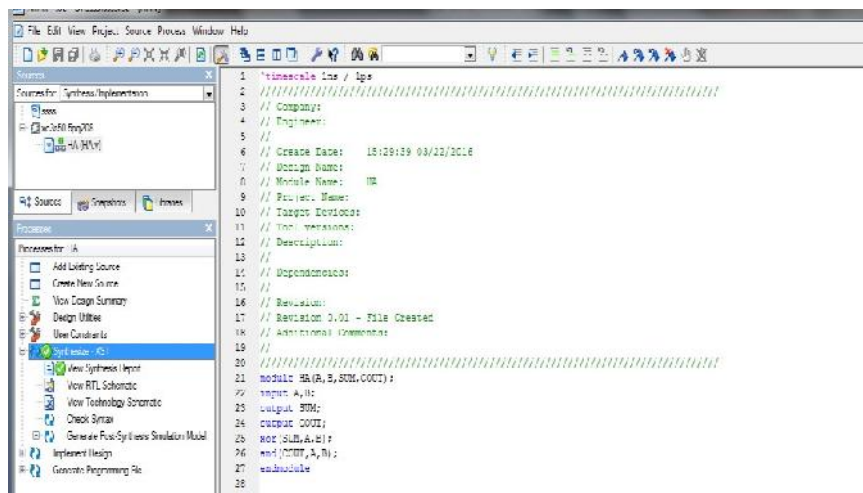STEP7: Check the synthesis XST and check syntax




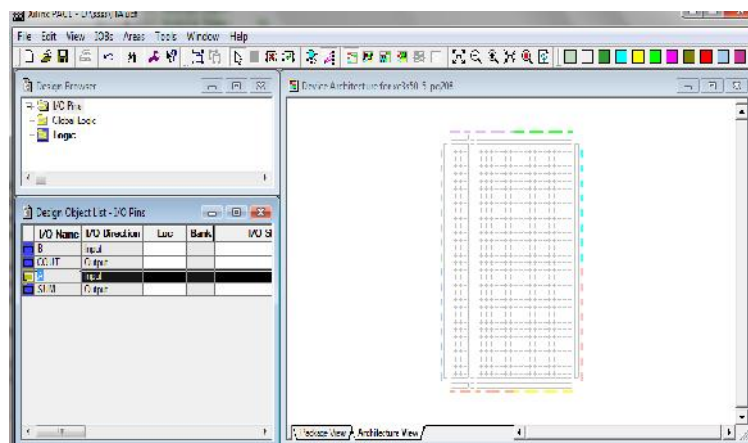STEP8: Select user constraints-> assign package pins, set port numbers and save it then select IO Bus delimiter as XST default <->-> click ok



STEP9:

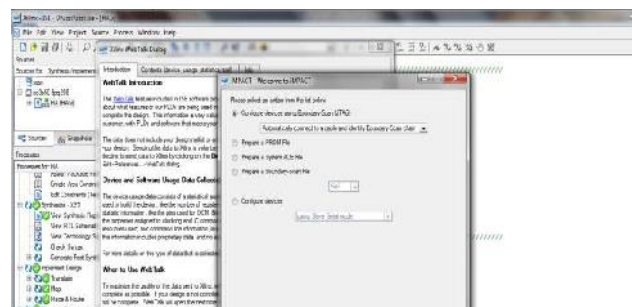
Double click implement design and click generate programming file-> configure device (impact)-> finish then select bit file



STEP10:

Rightclickonthexc3s400figure->program-
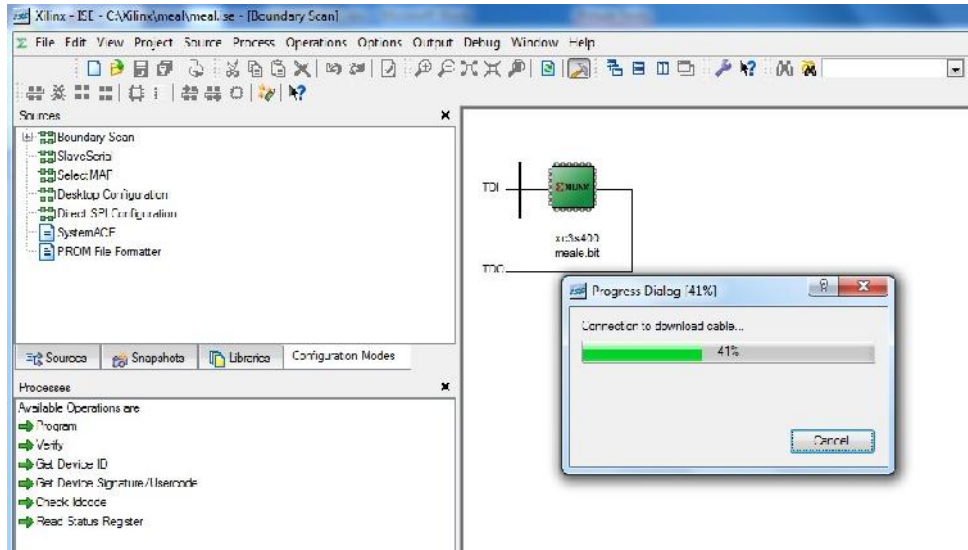
>filenamethen clickfinishandFinallycheckthefunctionalityinhardware



EXP NO: 1
Date:

Design Entry and Simulation of Combinational Circuits

AIM:

To write a Verilog code for the 4-bit Ripple carry adder and 4-bit Comparator and simulate it using Xilinx project navigator.

APPARATUS REQUIRED:


S.No	Name of the equipment/ software	Quantity
1.	PC with Windows	1
2.	Xilinx Project navigator	1

PROCEDURE:


1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the filename → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Click on the symbol of FPGA device and then right click → click on new source.
10. Select the Test Bench Waveform and give the filename → select entity click next and finish.
11. Select the desired parameters for simulating your design. In this case combinational circuit and simulation time click finish.
12. Assign all input signals using just click on graph and save file.
13. From the source process window. Click Behavioral simulation from drop-down menu
14. Select the test bench file (.tbw) and click process button → double click the Simulation Behavioral Model
15. Verify your design in wave window by seeing behavior of output signal with respect to input signal

4-Bit Ripple Carry Adder

Block Diagram:

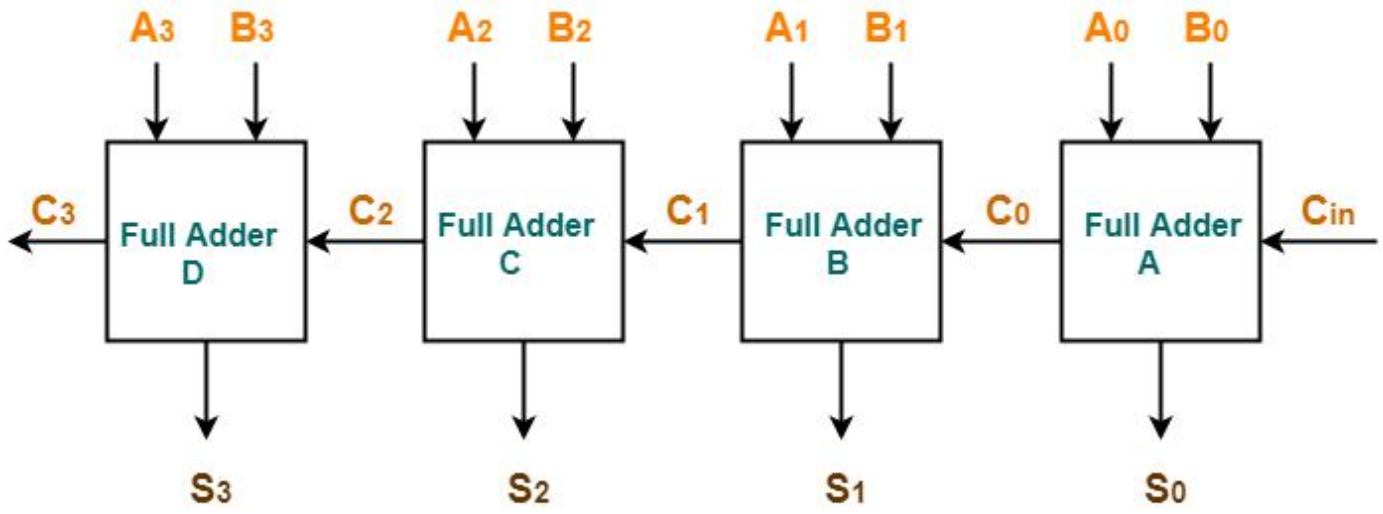

4-bit Ripple Carry Adder

 

Adding two 4-bit Numbers

CODING :

```

module ripple_carry_adder(a, b, cin, sum, cout);
input [03:0] a;
input [03:0] b;
input cin;
output [03:0] sum;
output cout;
wire [2:0]c;
fulladd a1(a[0],b[0],cin, sum[0],c[0]);
fulladd a2(a[1],b[1],c[0],sum[1],c[1]);
fulladd a3(a[2],b[2],c[1],sum[2],c[2]);
fulladd a4(a[3],b[3],c[2],sum[3],cout);
endmodule


```

```



module fulladd(a,b,cin,sum,cout);
input a,b,cin;
output sum,cout;
assign sum=(a^b^cin);
assign cout=((a&b)|(b&cin)|(a&cin));
endmodule

```


RTL SCHEMATIC:

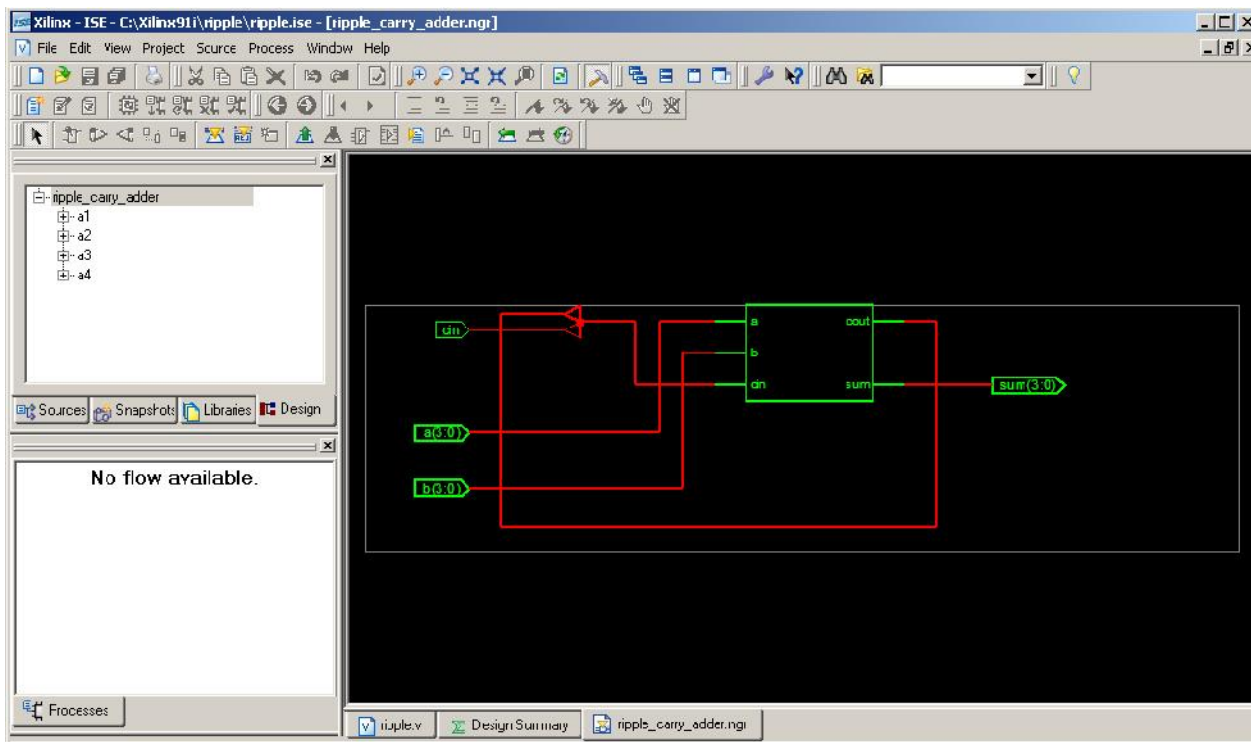

TECHNOLOGY SCHEMATIC:

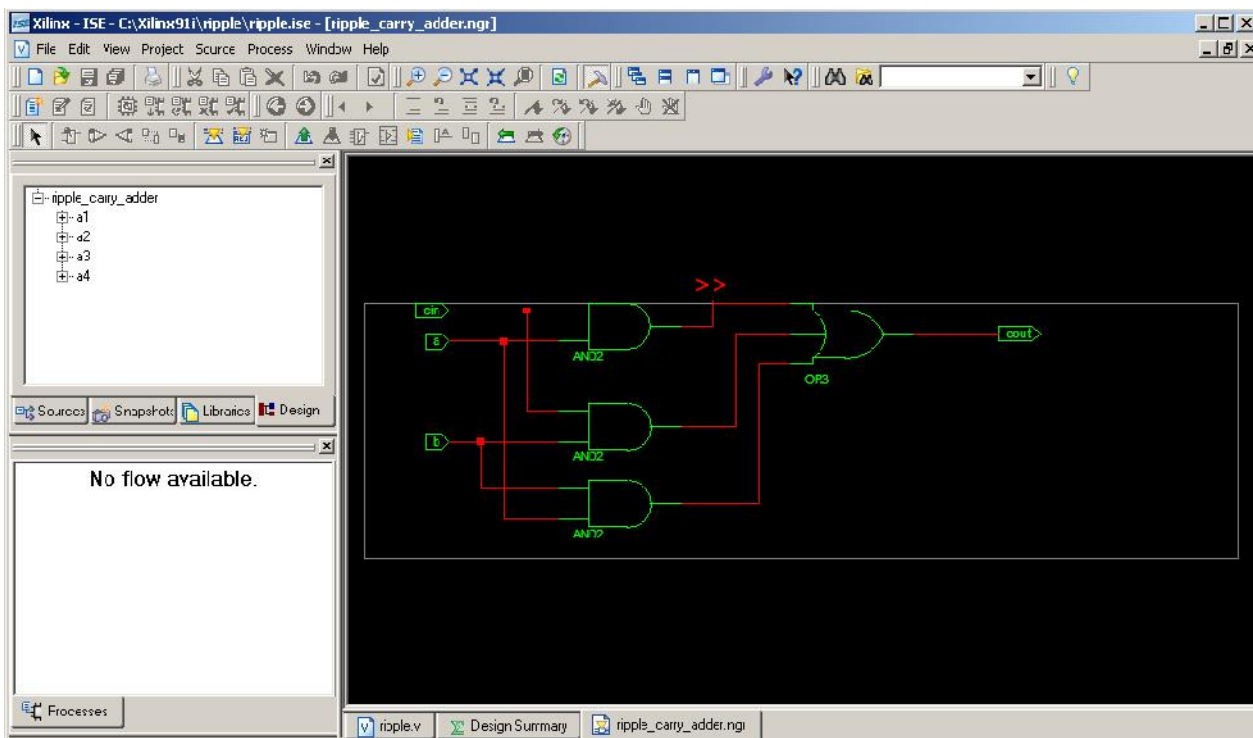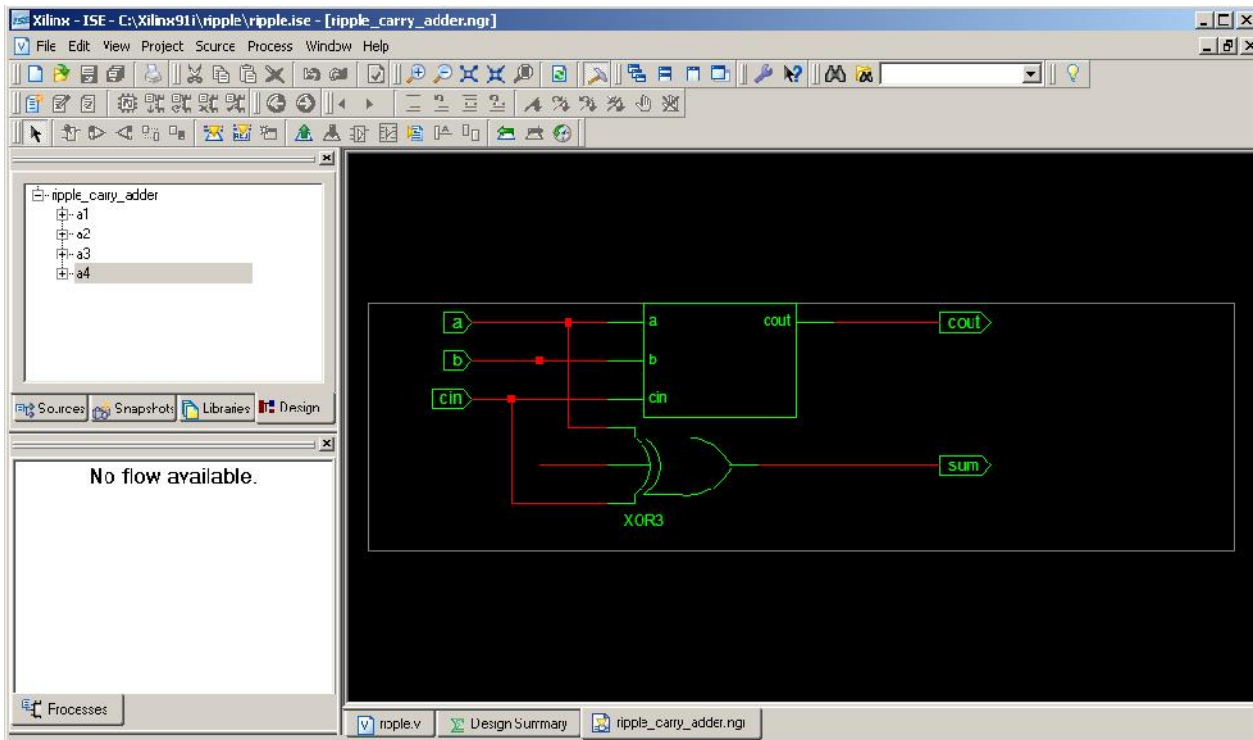

SIMULATION OUTPUT:

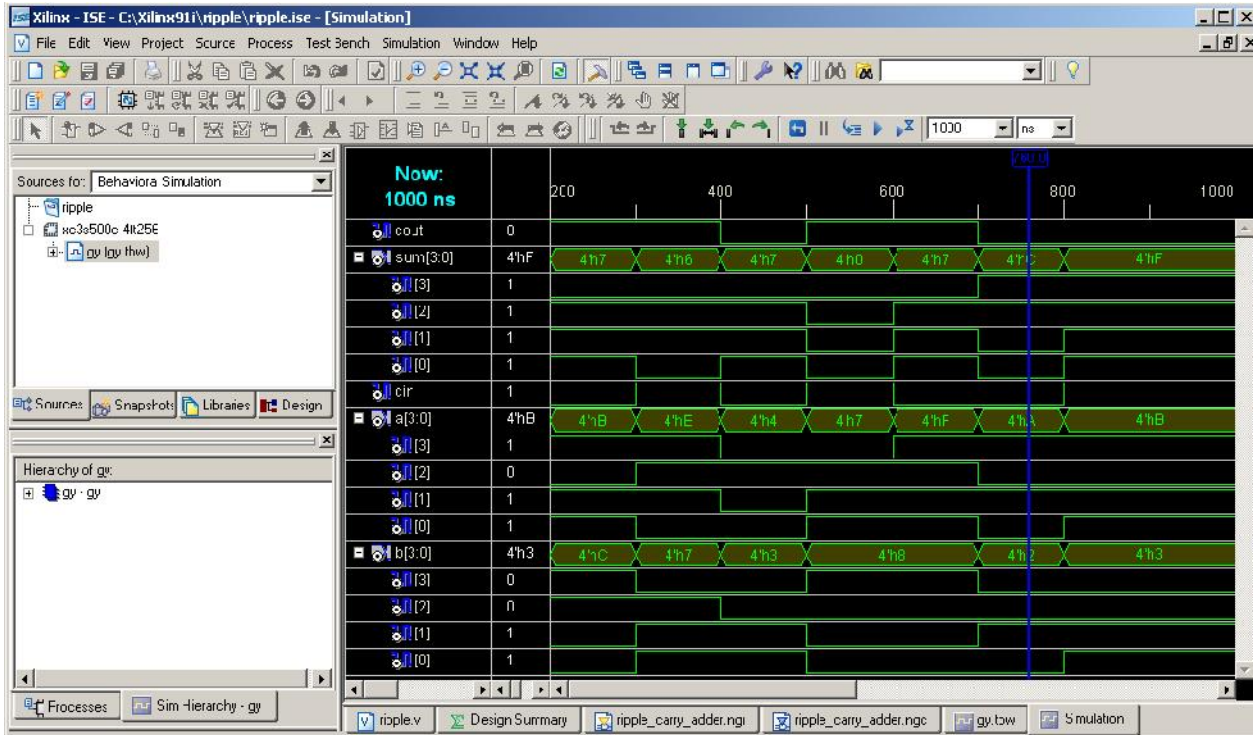

RESULT:

Thus the Verilog code for 4 bit Ripple Carry Adder is simulated using Xilinx project navigator.

AIM:

To synthesis 4- Bit Comparator and then Place& Route and Post Place & Root using Implementation option available in Xilinx project navigator.

APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	XilinxProject navigator	1

Theory:

- Back annotation is the translation of a routed or fitted design to a timing simulation netlist.
- To define the behavior of the FPGA, a hardware description language (HDL) or a schematic design methods are used. Common HDLs are VHDL and Verilog. Then, using an electronic design automation (EDA) tool, a technology-mapped net list is generated.
- The net list can then be fitted to the actual FPGA architecture using a process called place and- route, usually performed by the FPGA vendor's proprietary place-and-route software.
- The user will validate the map, place and route results via timing analysis, simulation, and other verification methodologies. Once the design and validation process is complete, the binary file generated is used to (re)configure the FPGA.
- In an attempt to reduce the complexity of designing in HDLs, which have been compared to the equivalent of assembly
- In a typical design flow, an FPGA application developer will simulate the design at multiple stages throughout the design process.
- Initially the RTL description in VHDL or Verilog is simulated by creating test benches to simulate the system and observe results.
- Then, after the synthesis engine has mapped the design to a net list, the net list is translated to a gate level description where simulation is repeated to confirm the synthesis proceeded without errors.
- Finally the design is laid out in the FPGA at which point propagation delays can be added and the simulation run again with these values back-annotated onto the net list.
- Place & Route, the process of optimization of logic cells for effective utilization of FPGAarea and the speed of operation, is used to modify and infer the following:
 1. Re-assignment of Pins
 2. Re-location of Slices
 3. Run time minimization

Procedure:

1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the file name → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Synthesis your design, from the source window select, synthesis/implementation from the window Now double click the Synthesis -XST
10. After Synthesis you assign the Pin Value for your design so, → double click the Assign Package Pins
11. Enter the Pin value for your input and output signals. if you want see your Pin assignment in FPGA zoom in Architecture View or Package View
12. Check the Pins in FPGA. Save file as XST Default click ok and close the window
13. Design Implementation begins with the mapping or fitting of a logical design file to a specific device and is complete when the physical design is successfully routed and a bit stream is generated. Double Click Implementation Design.
14. After finishing the Implementation, you can view the Implementation report.
15. After implementation you see Design Summary, you get the all details about your design. If you want edit the place and route double click View/Edit placed design
16. Check where your IOs are placed in FPGA. And zoom to view how Pins are placed in FPGA. You can see where your pins are placed
17. Just double click View/Edit Routed Design to view interconnection wires and blocks
18. Click the pin to see where its placed in FPGA. And Zoom particular area to see Place and Routing.
19. If required to change the place of the design, click and trace to another slice. View changed place and route of the design
20. Double click Back annotated Pin Location. Once back annotation is completed, constraint file is generated.

Block Diagram:



Truth Table

INPUT				OUTPUT		
A1	A0	B1	B0	A<B	A=B	A>B
0	0	0	0	0	1	0
0	0	0	1	1	0	0
0	0	1	0	1	0	0
0	0	1	1	1	0	0
0	1	0	0	0	0	1
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	0	0
1	0	0	0	0	0	1
1	0	0	1	0	0	1
1	0	1	0	0	1	0
1	0	1	1	1	0	0
1	1	0	0	0	0	1
1	1	0	1	0	0	1
1	1	1	0	0	0	1
1	1	1	1	0	1	0

Coding :


```

//declare the Verilog module - The inputs and output signals.
module comparator(
    Data_in_A, //input A
    Data_in_B, //input B
    less,      //high when A is less than B
    equal,     //high when A is equal to B
    greater    //high when A is greater than B
);


//what are the input ports.
input [3:0] Data_in_A;
input [3:0] Data_in_B;
//What are the output ports.
output less;
output equal;
output greater;
//Internal variables
reg less;
reg equal;
reg greater;

    • //When the inputs and A or B are changed execute this block
    always @(Data_in_A or Data_in_B)
    begin
        if(Data_in_A > Data_in_B) begin //check if A is bigger than B.
            less = 0;
            equal = 0;
            greater = 1; end
        else if(Data_in_A == Data_in_B) begin //Check if A is equal to B
            less = 0;
            equal = 1;
            greater = 0; end
        else begin //Otherwise - check for A less than B.
            less = 1;
            equal = 0;
            greater = 0;
        end
    end
endmodule



```

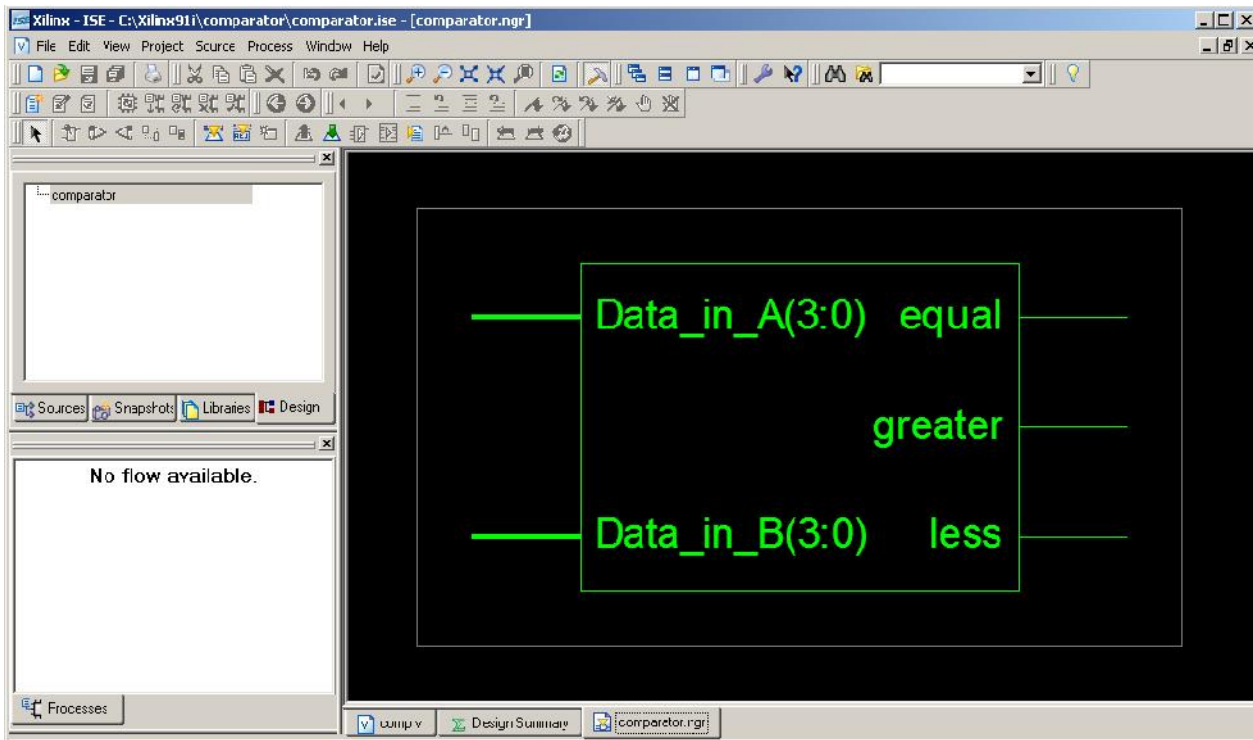

TECHNOLOGY SCHEMATIC:

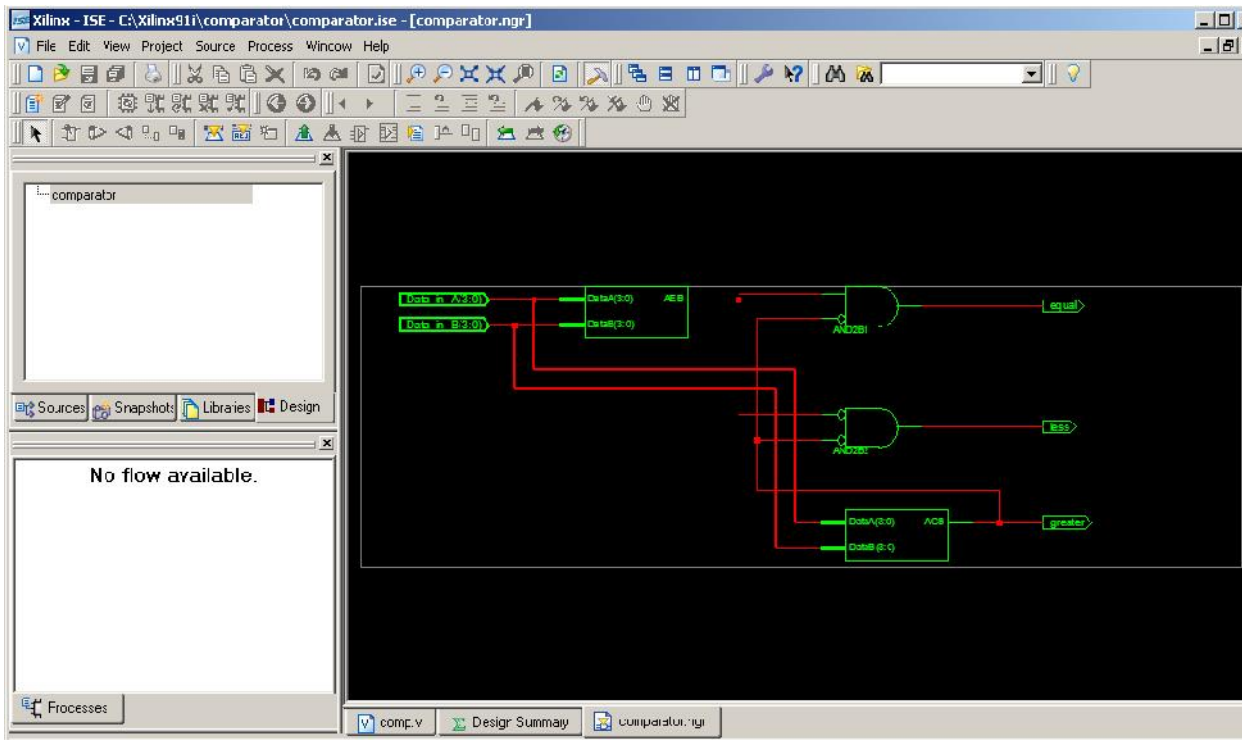

PLACE AND ROUTE.

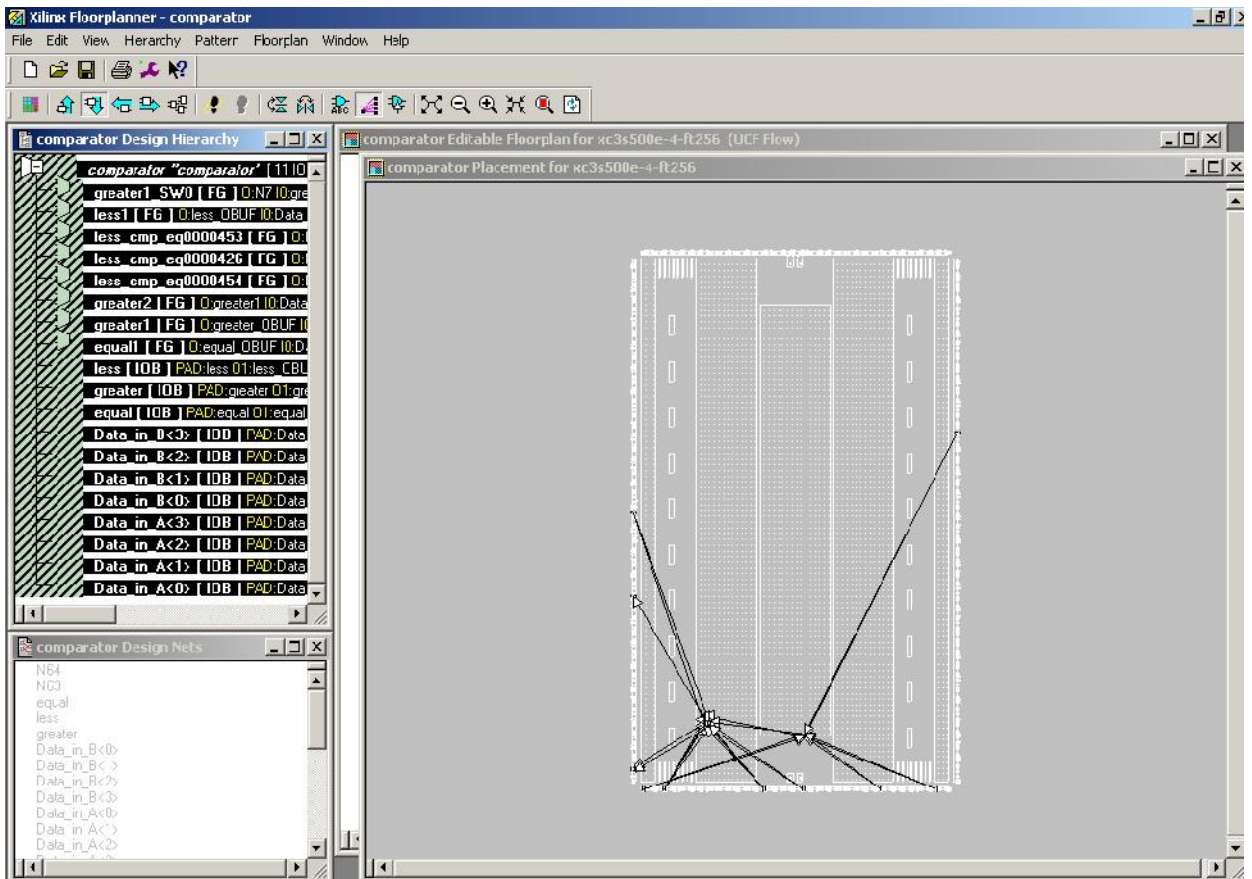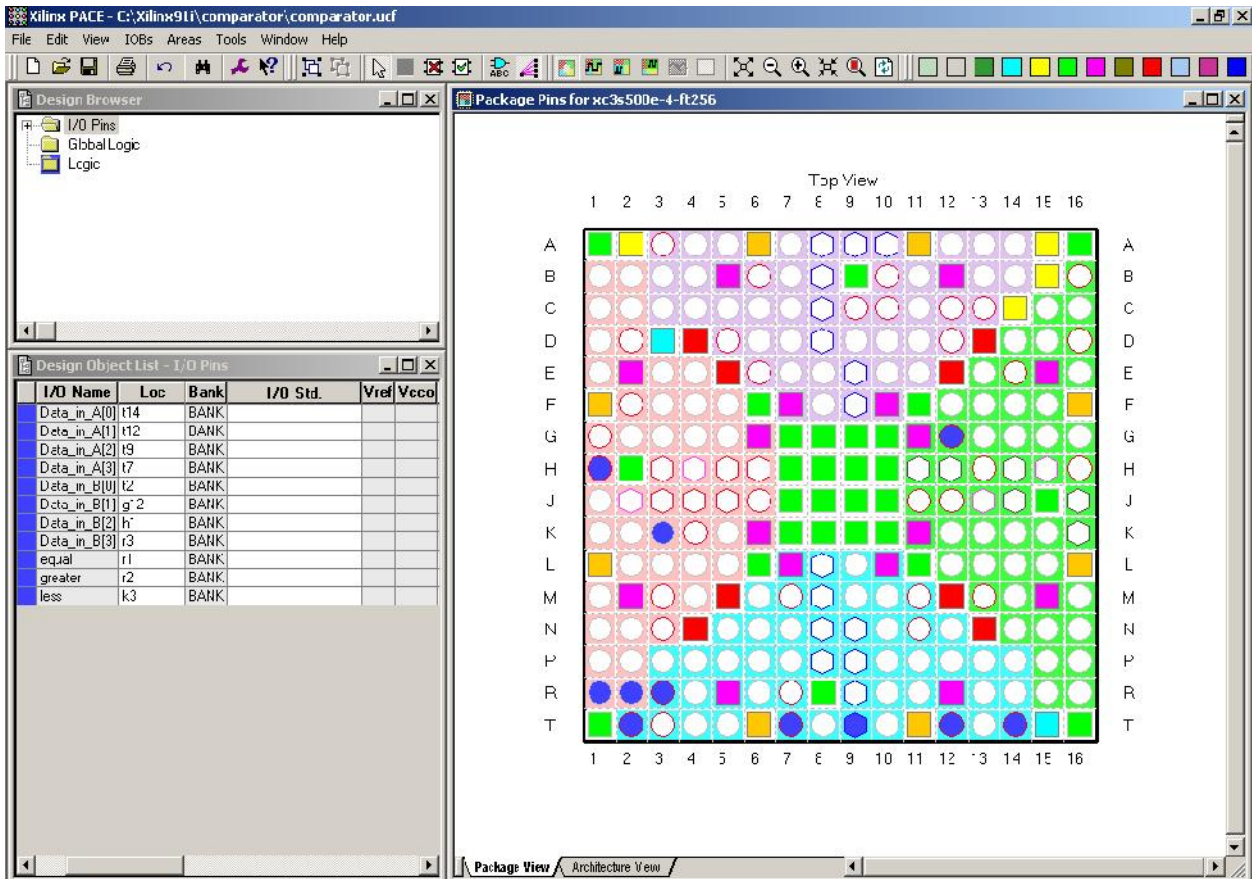

RESULT:

Thus, the Place and Route and Post Place and Route using Implementation options available in Xilinx project navigator were synthesized for 4-bit Comparator.

EXP NO: 3
Date:

Design and FPGA Implementation of Combinational Circuits

AIM:

To design and implement Booth Multiplier and Carry select Adder in FPGA Spartan 3E Trainer kit using Xilinx project navigator.


APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	XilinxProject navigator	1

PROCEDURE:

1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the file name → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → Synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Synthesis your design, from the source window select, synthesis/implementation from the window Now double click the Synthesis -XST.
10. After Synthesis, Click on the symbol of FPGA device and Right click and select New Source, Select Implementation Constraints File and type file name and click next.
11. Type the Net list and click save.
12. Implement the design by double clicking Implement design in the process window.
13. Then double click Generate Programming File, Double click Configure Target Device and click OK.
14. Double click Create PROM File in the ISE iMPACT window, Select Storage Target Device as Xilinx Flash PROM and click forward.
15. Add storage Device as xcf01s [2 M] and click forward, Type Output File Name and Location and click OK.
16. Select the corresponding .bit file and click Open, Click No to Add Another Device and Click OK.
17. Double click Generate File.
18. Double click Boundary Scan and Right click on the window and select Initialize Chain, Now Select the corresponding .mcs file and click open.
19. Click OK in the Device Programming Properties window, Download the Program on to the kit by Right clicking on the device icon and select program.
20. Verify the output in the target device.


BOOTH ALGORITHM:

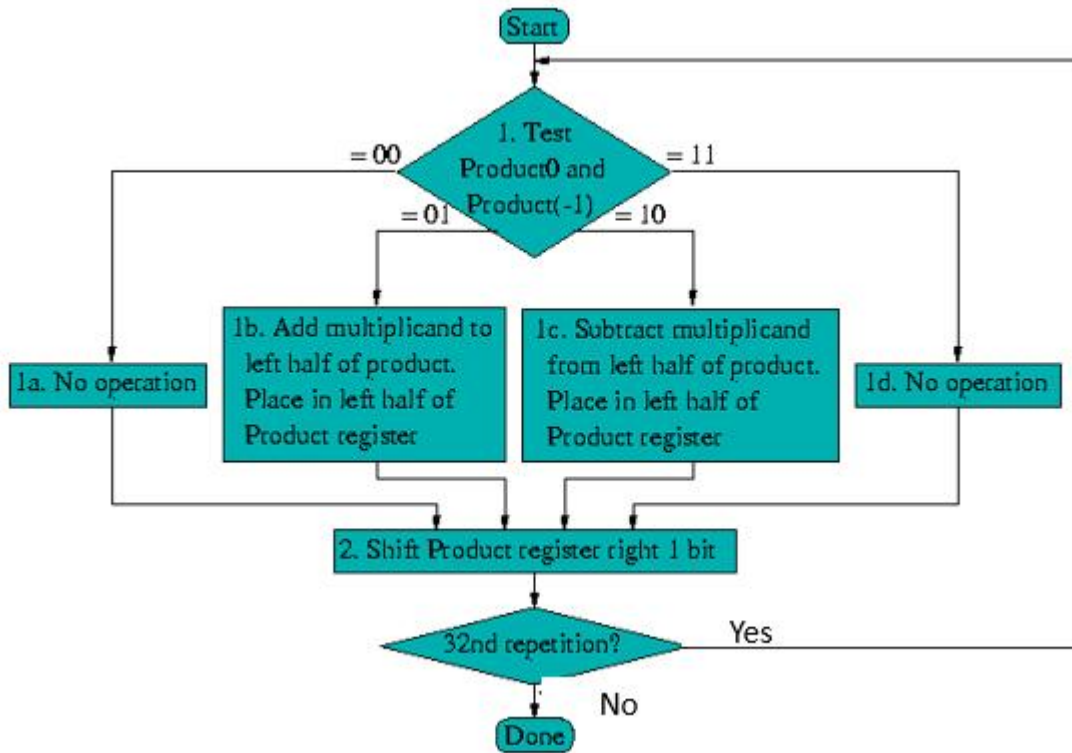


CODING:

```
module boothmulti(X, Y, Z);
    input signed [3:0] X, Y;
    output signed [7:0] Z;
    reg signed [7:0] Z;
    reg [1:0] temp;
    integer i;
    reg E1;
    reg [3:0] Y1;
    always @ (X, Y)
    begin
        Z = 8'd0;
        E1 = 1'd0;
        for (i = 0; i < 4; i = i + 1)
            begin
                temp = {X[i], E1};
                Y1 = - Y;
            case (temp)
                2'd2 : Z [7 : 4] = Z [7 : 4] + Y1;
                2'd1 : Z [7 : 4] = Z [7 : 4] + Y;
                default : begin end
            endcase
            Z = Z >> 1;
            Z[7] = Z[6];
            E1 = X[i];
        end
        if (Y == 4'd8)
            begin
                Z = - Z;
            end
        end
    endmodule
```




RTL SCHEMATIC:

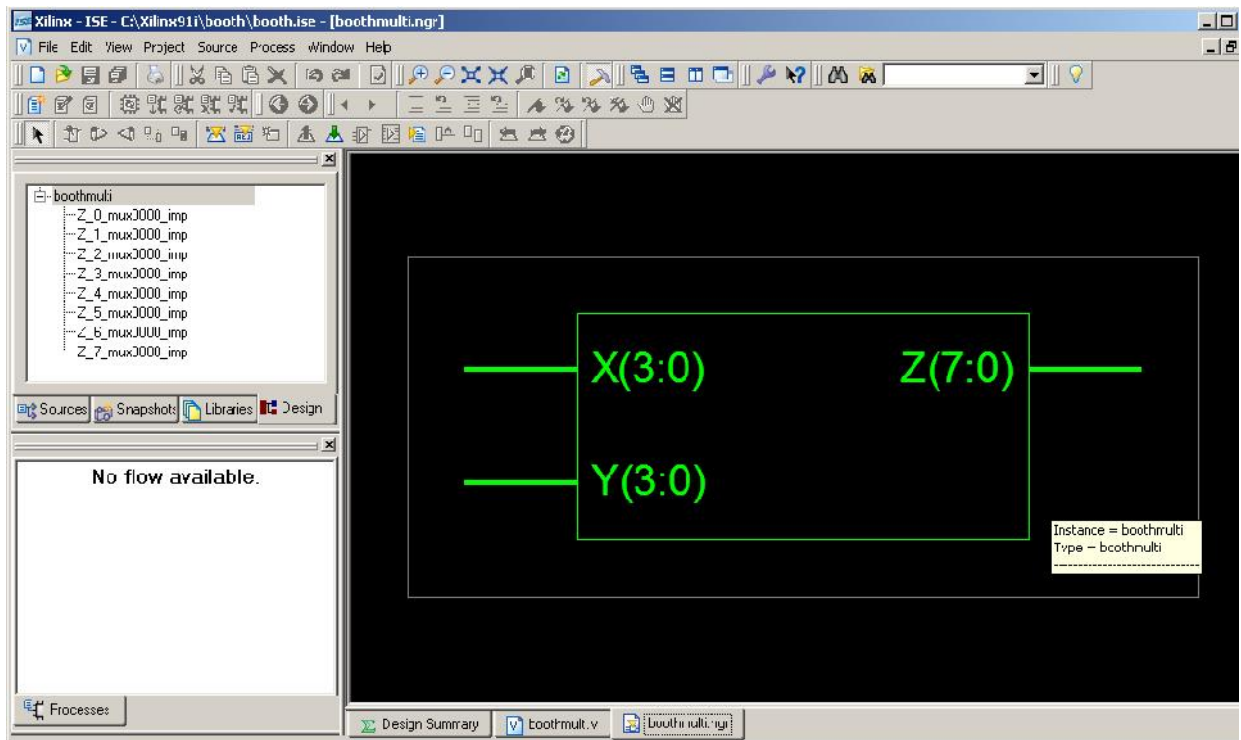


TECHNOLOGY SCHEMATIC:

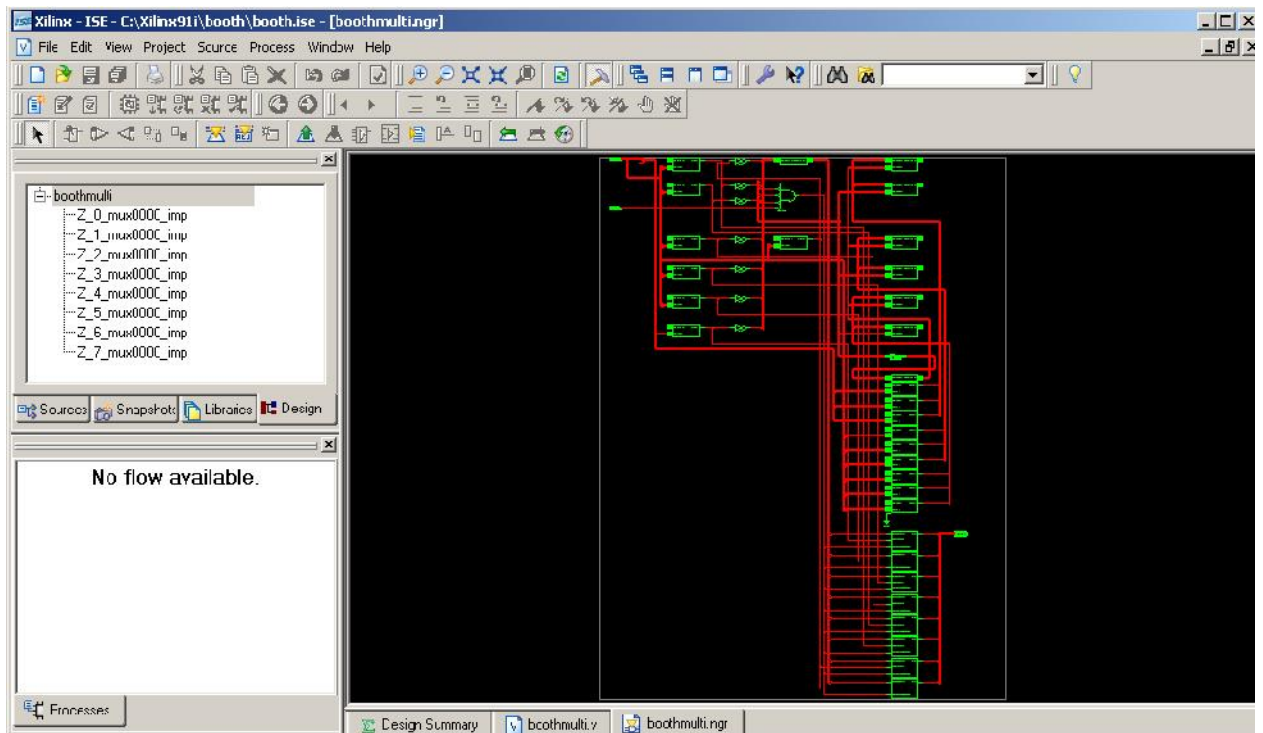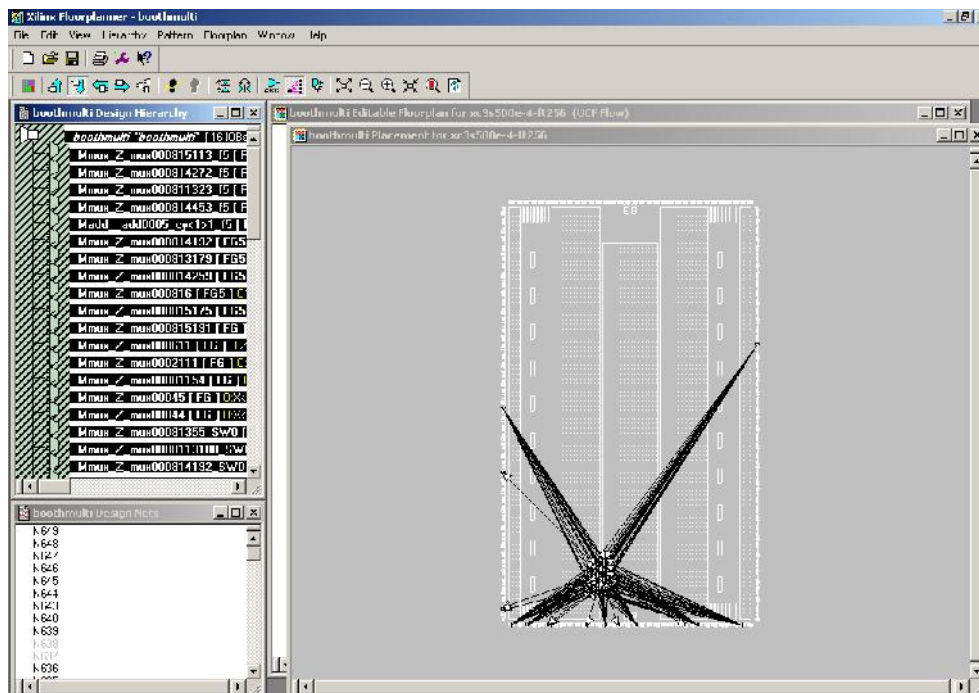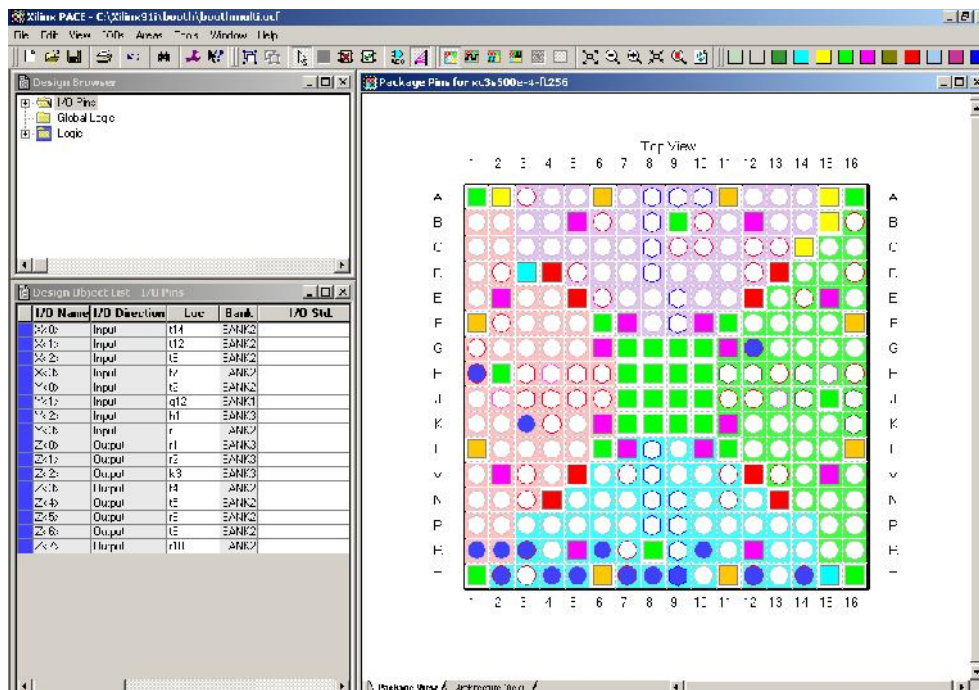

PLACE AND ROUTE:




HARDWARE FUSING:

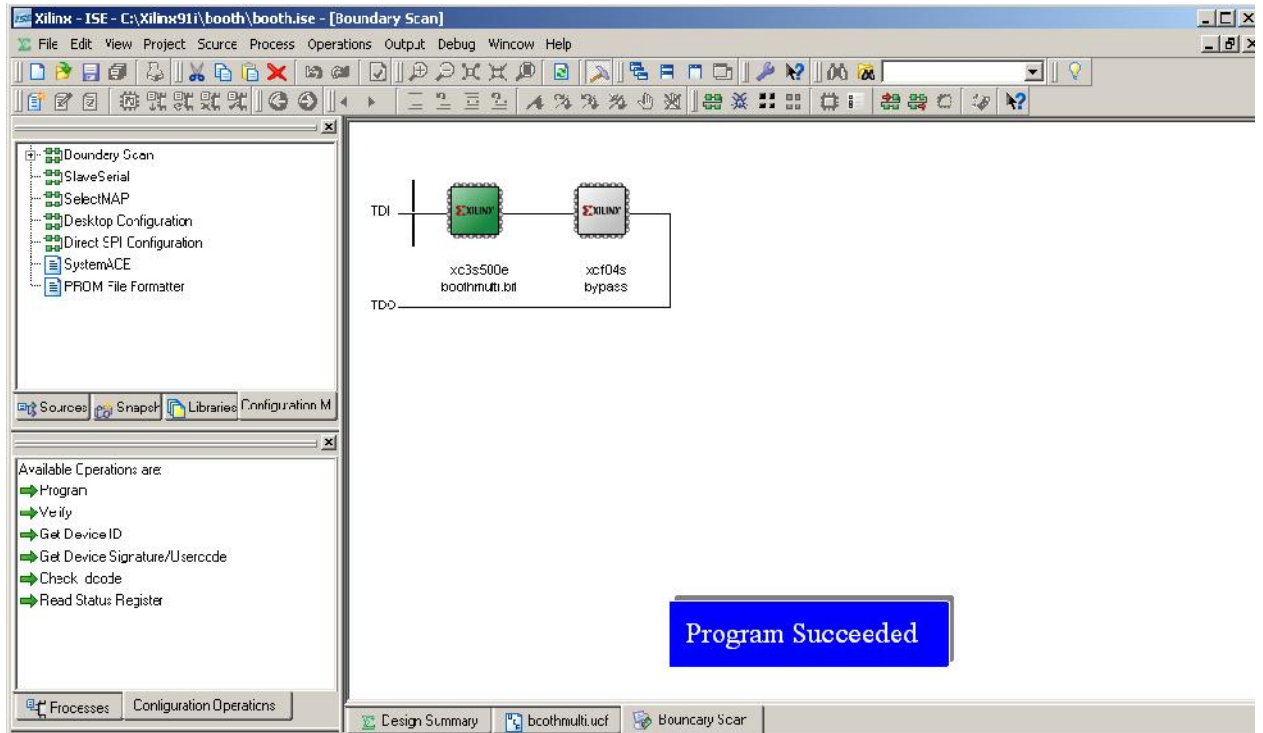

CARRY SELECT ADDER:

BLOCK DIAGRAM:

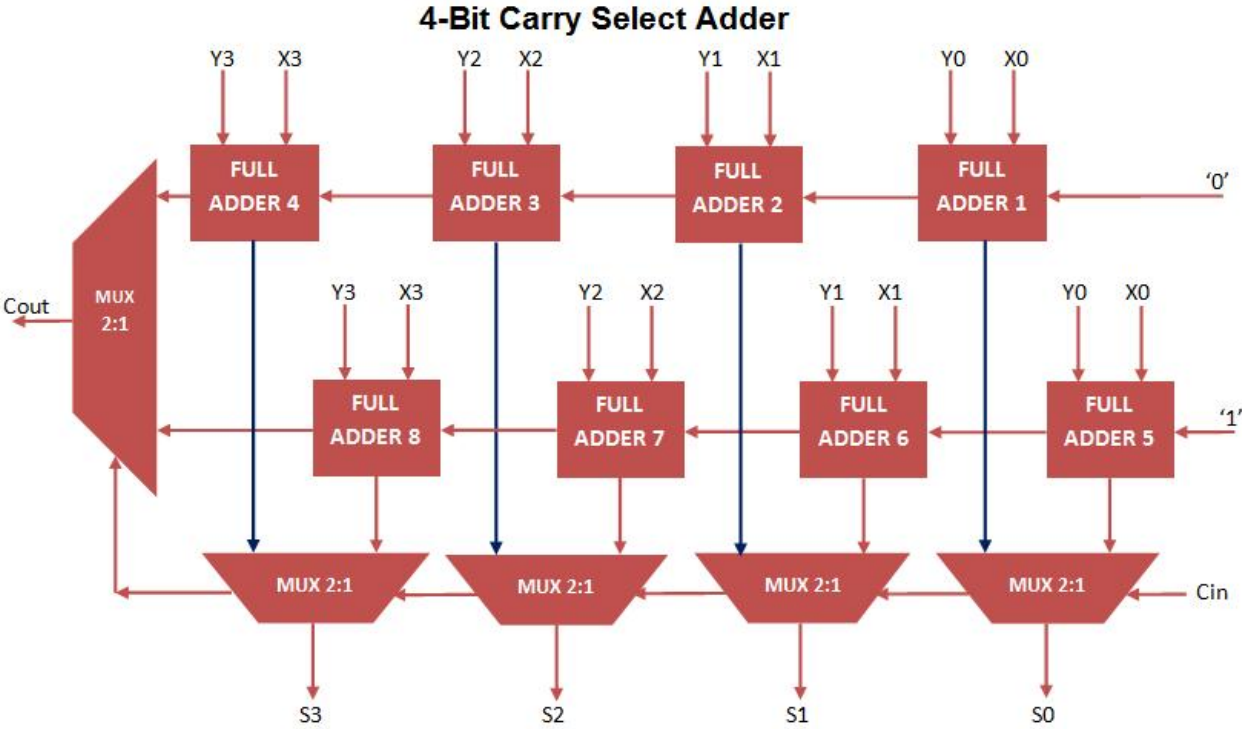

CODING:

```
module carry_select_adder
  ( input [3:0] A,B,
    input cin,
    output [3:0] S,
    output cout
  );

  wire [3:0] temp0,temp1,carry0,carry1;

  //for carry 0
  fulladder fa00(A[0],B[0],1'b0,temp0[0],carry0[0]);
  fulladder fa01(A[1],B[1],carry0[0],temp0[1],carry0[1]);
  fulladder fa02(A[2],B[2],carry0[1],temp0[2],carry0[2]);
  fulladder fa03(A[3],B[3],carry0[2],temp0[3],carry0[3]);

  //for carry 1
  fulladder fa10(A[0],B[0],1'b1,temp1[0],carry1[0]);
  fulladder fa11(A[1],B[1],carry1[0],temp1[1],carry1[1]);
  fulladder fa12(A[2],B[2],carry1[1],temp1[2],carry1[2]);
  fulladder fa13(A[3],B[3],carry1[2],temp1[3],carry1[3]);

  //mux for carry
  multiplexer2 mux_carry(carry0[3],carry1[3],cin,cout);
  //mux's for sum
  multiplexer2 mux_sum0(temp0[0],temp1[0],cin,S[0]);
  multiplexer2 mux_sum1(temp0[1],temp1[1],cin,S[1]);
  multiplexer2 mux_sum2(temp0[2],temp1[2],cin,S[2]);
  multiplexer2 mux_sum3(temp0[3],temp1[3],cin,S[3]);

  endmodule
```

```
module fulladder
  ( input a,b,cin,
    output sum,carry
  );
```

```
  assign sum = a ^ b ^ cin;
  assign carry = (a & b) | (cin & b) | (a & cin);
```


```
endmodule
```

```
module multiplexer2
  ( input i0,i1,sel,
    output reg bitout
  );
```


```
  always@(i0,i1,sel)
  begin
    if(sel == 0)
      bitout = i0;
    else
      bitout = i1;
  end
```

```
endmodule
```



RTL SCHEMATIC:

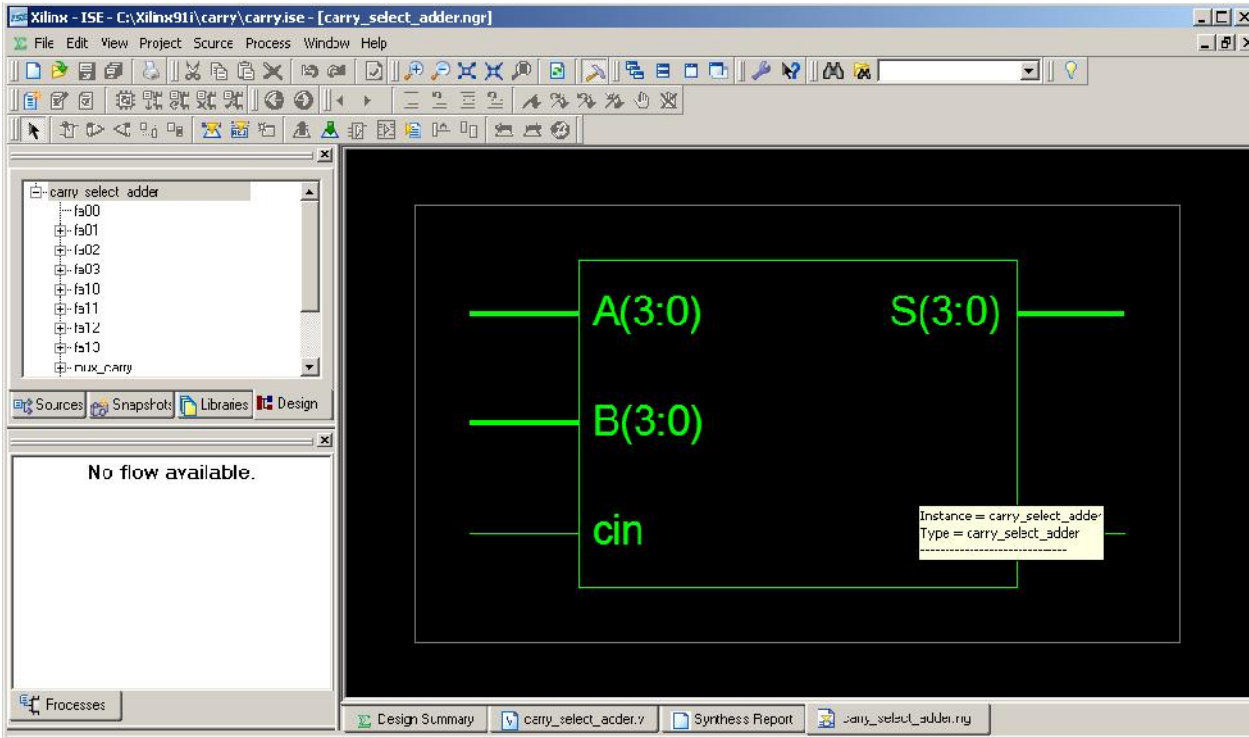


TECHNOLOGY SCHEMATIC:

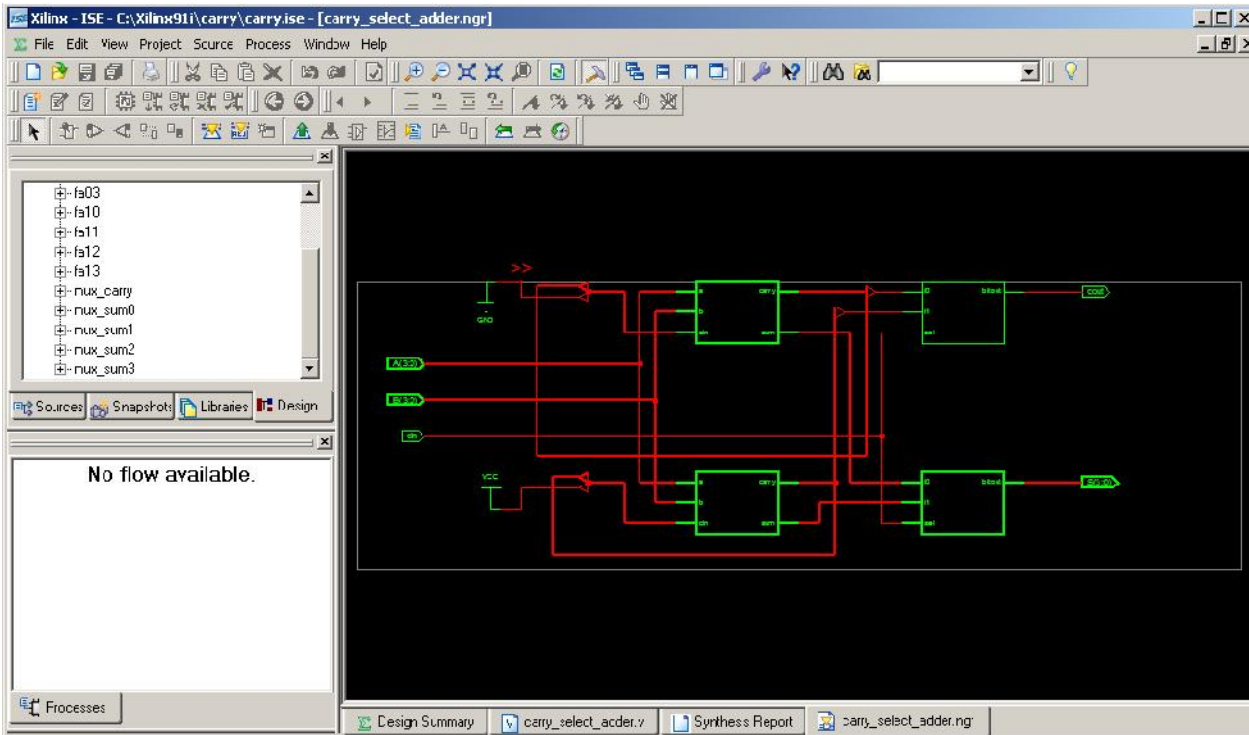

PLACE AND ROUTE:

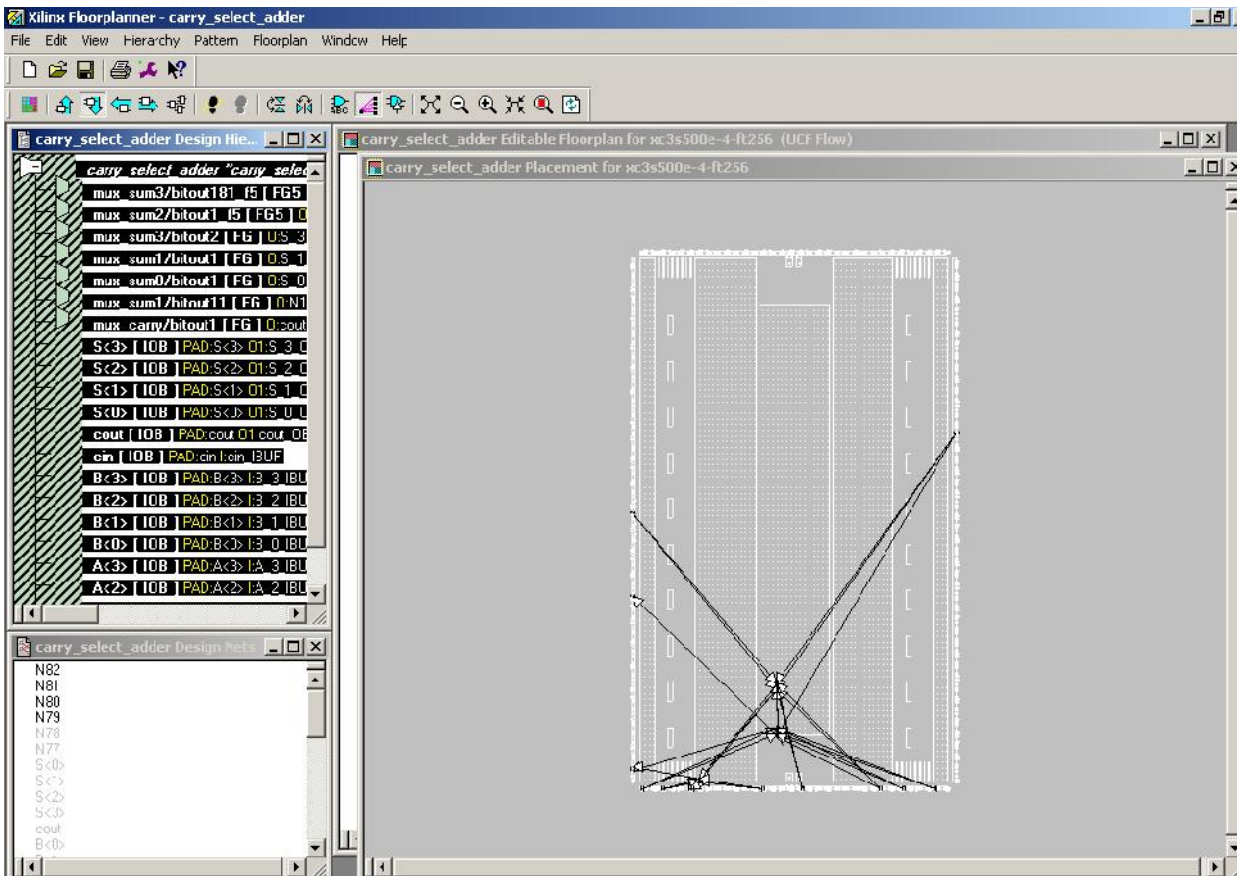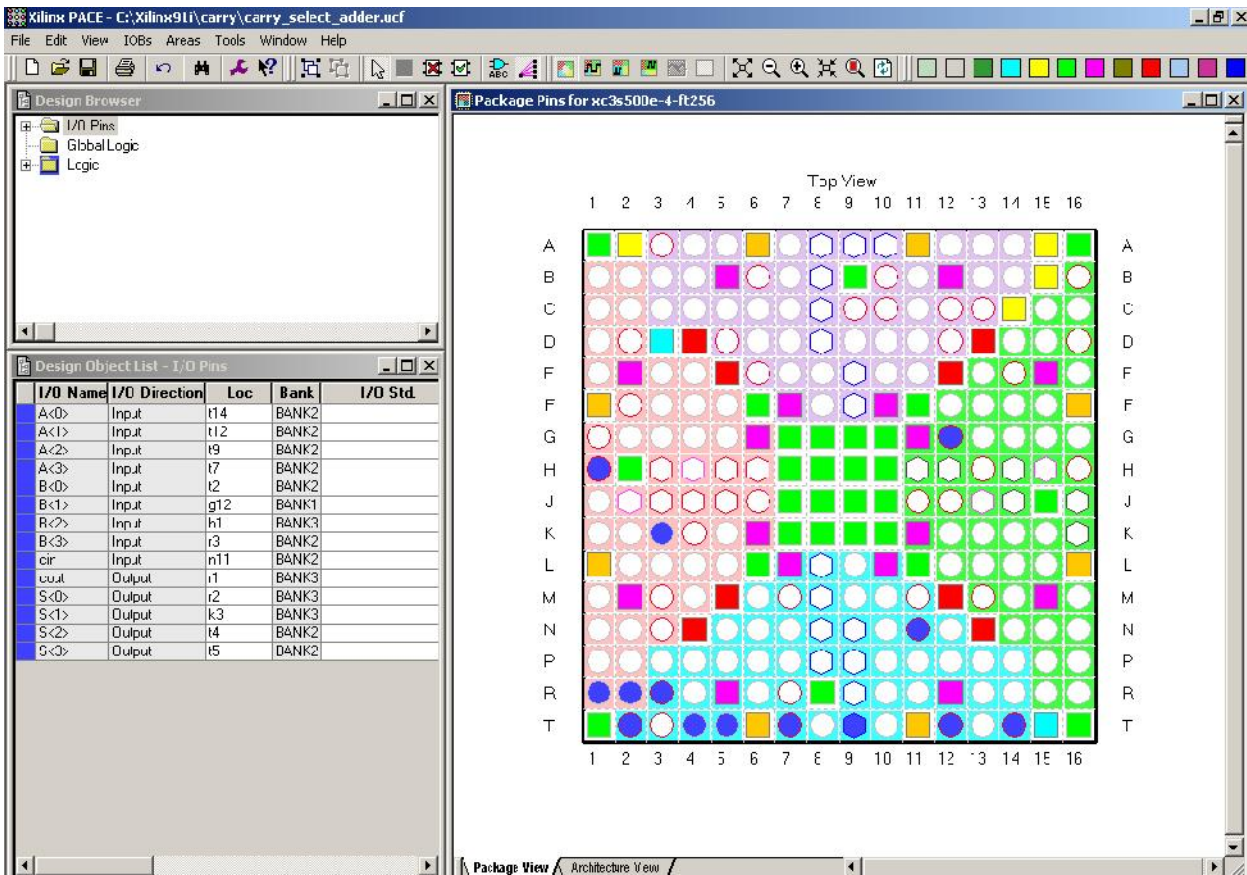

HARDWARE FUSING:

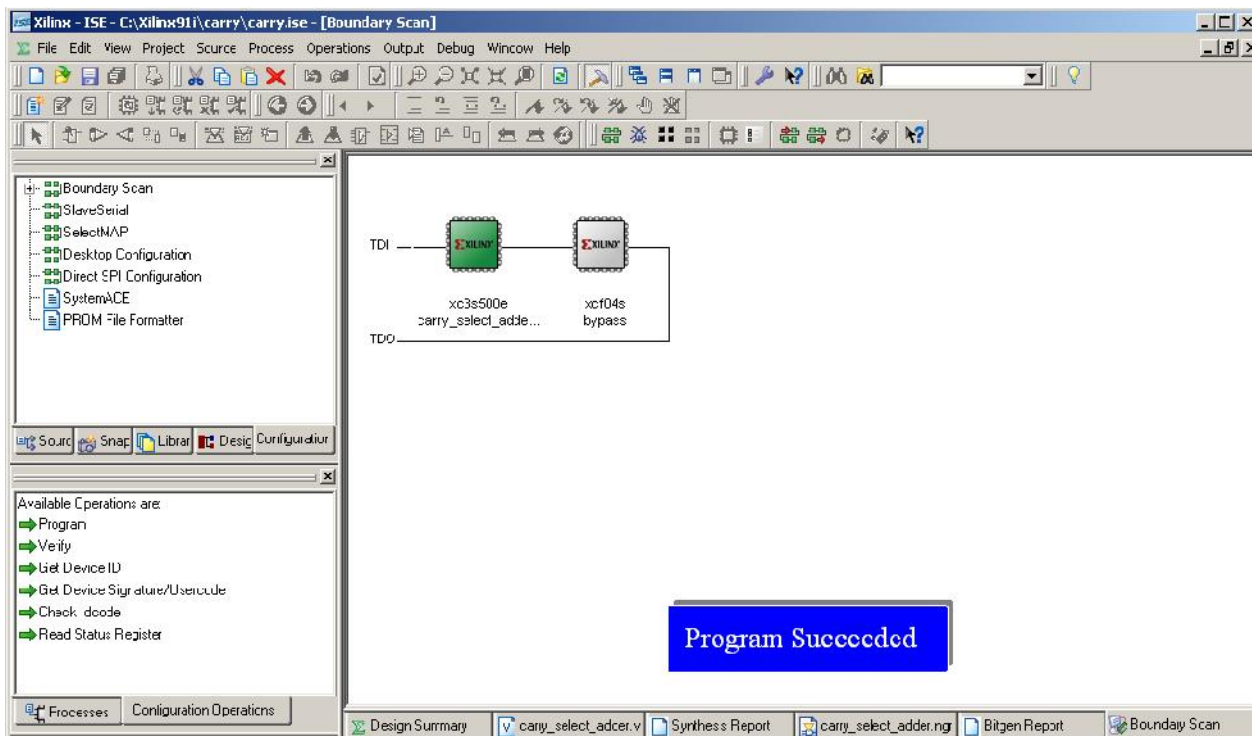

RESULT:

Thus, the Hardware fusing and testing of Booth Multiplier and Carry Select Adder were implemented in Spartan 3E FPGA trainer kit using Xilinx project navigator.

EXP NO: 4
Date:

Design and FPGA Implementation of Sequential Circuits

AIM:

To design and implement Counter in FPGA Spartan 3E Trainer kit using Xilinx project navigator.

APPARATUS REQUIRED:

S.No	Name of the equipment/ software	Quantity
1.	PC with Windows	1
2.	Xilinx Project navigator	1


PROCEDURE:

1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the file name → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → Synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Synthesis your design, from the source window select, synthesis/implementation from the window Now double click the Synthesis -XST.
10. After Synthesis, Click on the symbol of FPGA device and Right click and select New Source, Select Implementation Constraints File and type file name and click next.
11. Type the Net list and click save.
12. Implement the design by double clicking Implement design in the process window.
13. Then double click Generate Programming File, Double click Configure Target Device and click OK.
14. Double click Create PROM File in the ISE iMPACT window, Select Storage Target Device as Xilinx Flash PROM and click forward.
15. Add storage Device as xcf01s [2 M] and click forward, Type Output File Name and Location and click OK.
16. Select the corresponding .bit file and click Open, Click No to Add Another Device and Click OK.
17. Double click Generate File.
18. Double click Boundary Scan and Right click on the window and select Initialize Chain, Now Select the corresponding .mcs file and click open.
19. Click OK in the Device Programming Properties window, Download the Program on to the kit by Right clicking on the device icon and select program.
20. Verify the output in the target device.


CODING:

```
Module ripple counter (A0, A1, A2, A3, Count, Reset)
Output A0,A1, A2,A3;
Input Count,Reset;
ff f0(A0, Count, Reset);
ff f1(A1, A0, Reset);
ff f2(A2, A1, Reset);
ff f3(A3, A2, Reset);
end module
module ff
(Q, CLK, Reset);
output Q;
input CLK, Reset;
reg Q;
always @ (negedge CLK or negedge Reset)
if (~Reset)
Q=1'b0;
else Q=(~Q);
endmodule
```


RTL SCHEMATIC:

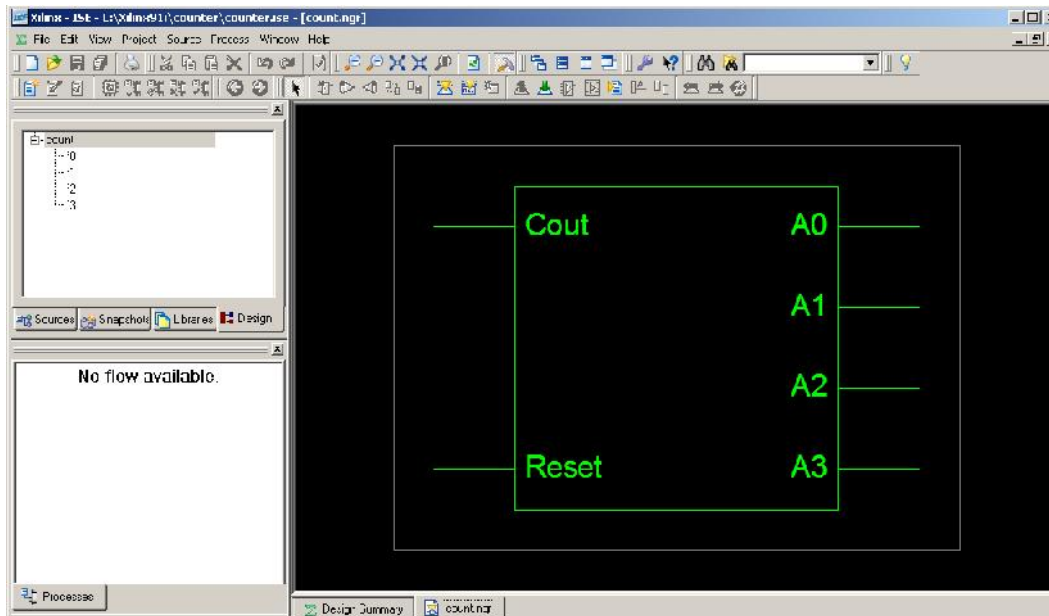


TECHNOLOGY SCHEMATIC:

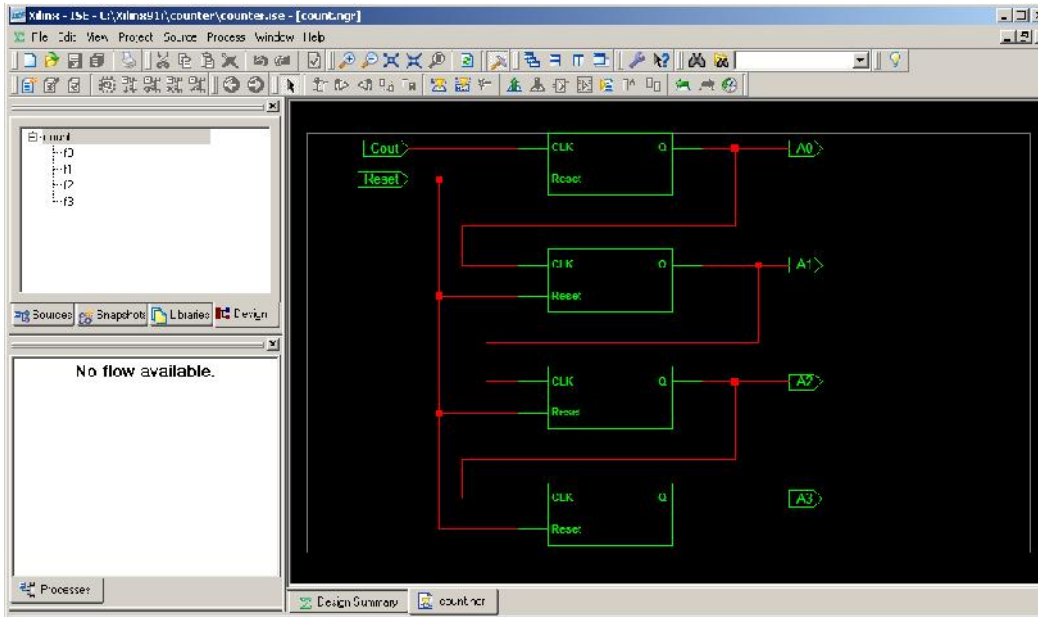


PLACE AND ROUTE:

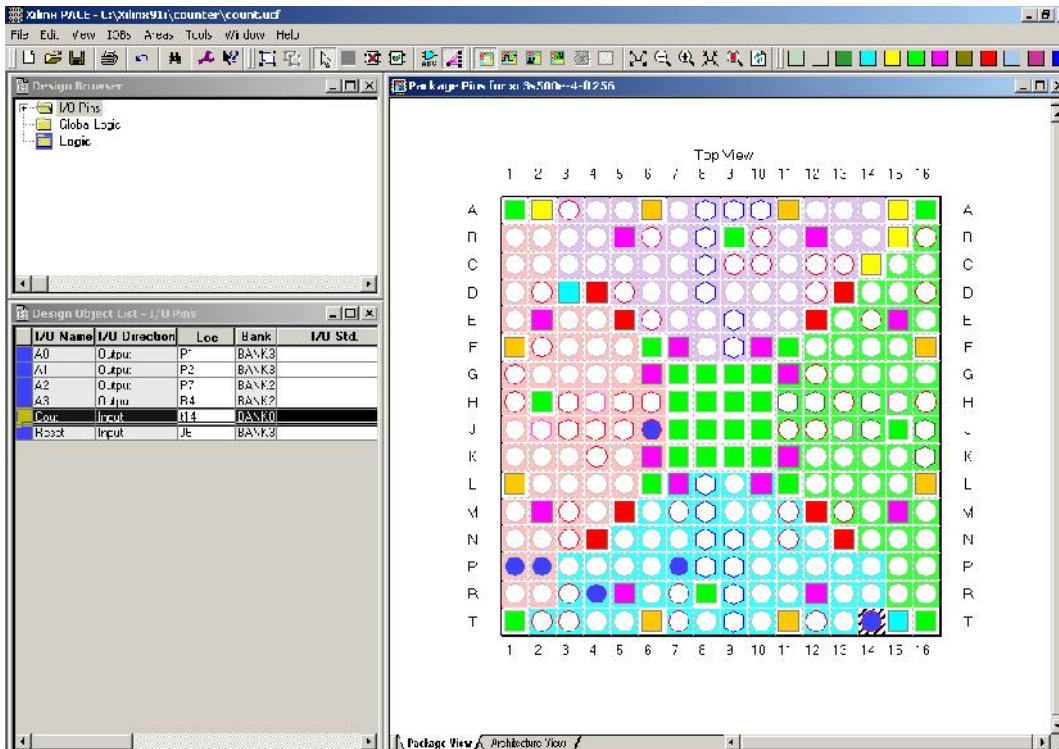

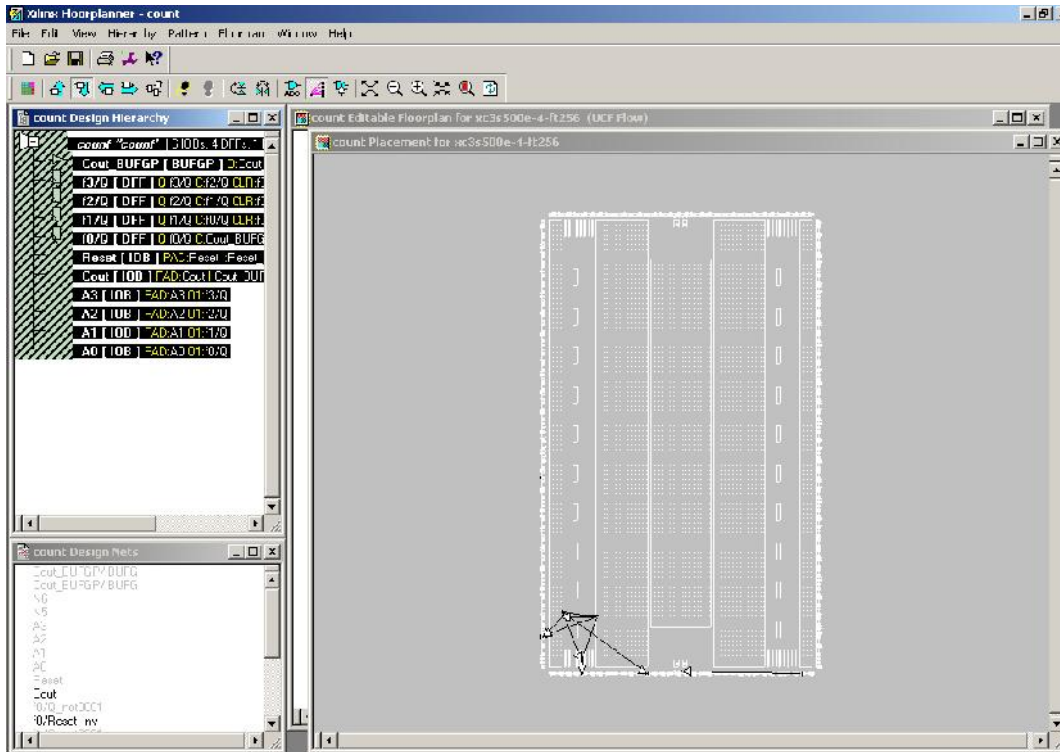

HARDWARE FUSING

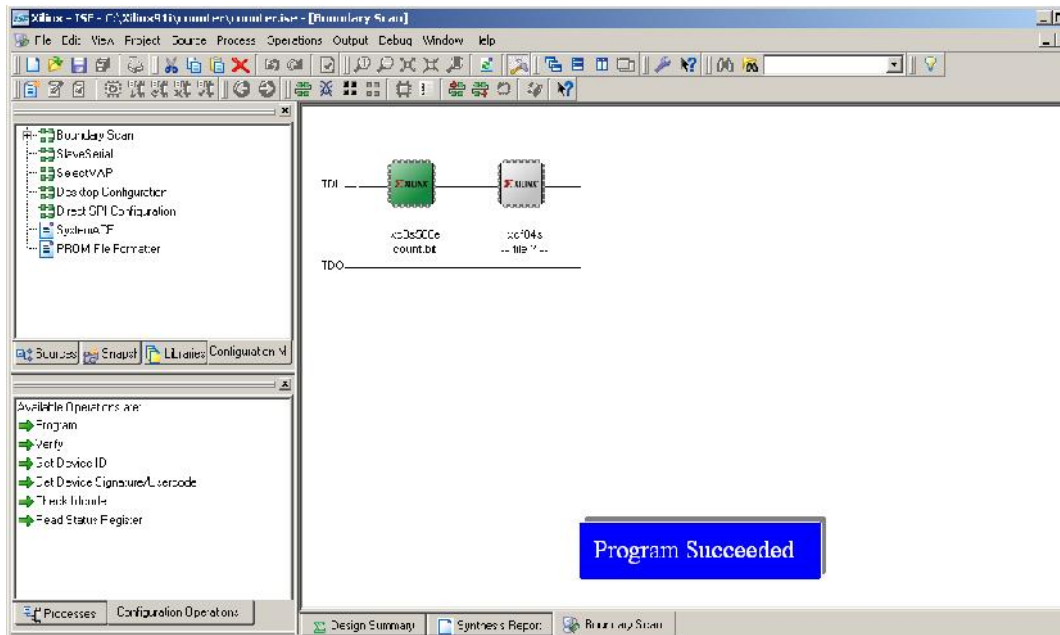

RESULT:

Thus, the Hardware fusing and testing of 4-Bit counter was implemented in Spartan 3E FPGA trainer kit using Xilinx project navigator.

EXP NO: 5
Date:

Analysis of Area, Power and Delay for Sequential Circuits

AIM:

To analyze area, power and delay for Counter and PRBS generator in FPGA Spartan 3E Trainer kit using Xilinx project navigator.

APPARATUS REQUIRED:

S.No	Name of the equipment/ software	Quantity
1.	PC with Windows	1
2.	Xilinx Project navigator	1

PROCEDURE:

1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the file name → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → Synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Synthesis your design, from the source window select, synthesis/implementation from the window Now double click the Synthesis -XST.
10. After Synthesis, Click on the synthesis report to generate the area and delay summary.
11. Type the Net list and click save.
12. Implement the design by double clicking Implement design in the process window.
13. Then double click Generate Programming File, Double click Configure Target Device and click OK.
14. Double click Create PROM File in the ISE iMPACT window, Select Storage Target Device as Xilinx Flash PROM and click forward.
15. Add storage Device as xcf01s [2 M] and click forward, Type Output File Name and Location and click OK.
16. Select the corresponding .bit file and click Open, Click No to Add another Device and Click OK.
17. Double click Generate File.
18. Double click Boundary Scan and Right click on the window and select Initialize Chain, Now Select the corresponding .mcs file and click open.
19. Click OK in the Device Programming Properties window, Download the Program on to the kit by Right clicking on the device icon and select program.
20. Verify the output in the target device.

RIPPLE COUNTER:

CODING:

```
Module ripple counter (A0, A1, A2, A3, Count, Reset)
Output A0,A1, A2,A3;
Input Count,Reset;
ff f0(A0, Count, Reset);
ff f1(A1, A0, Reset);
ff f2(A2, A1, Reset);
ff f3(A3, A2, Reset);
end module
module ff
(Q, CLK, Reset);
output Q;
input CLK, Reset;
reg Q;
always @ (negedge CLK or negedge Reset)
if (~Reset)
Q=1'b0;
else Q=~Q;
endmodule
```

ANALYZE REPORT:

Area analysis:

Device utilization summary:

Selected Device: 3s500eft256-4

Number of Slices:	3 out of	4656	0%
Number of Slice Flip Flops:	4 out of	9312	0%
Number of 4 input LUTs:	5 out of	9312	0%
Number of IOs:	6		
Number of bonded IOBs:	6 out of	190	3%
Number of GCLKs:	1 out of	24	4%

Partition Resource Summary:

No Partitions were found in this design.

=====

Power analysis:

Power summary:	I(mA)	P(mW)
Total estimated power consumption:		81
Vccint 1.20V:	26	31
Vccaux 2.50V:	18	45
Vcco25 2.50V:	2	5
Clocks:	0	0
Inputs:	0	0
Logic:	0	0
Outputs:		
Vcco25	0	0
Signals:	0	0
Quiescent Vccint 1.20V:	26	31
Quiescent Vccaux 2.50V:	18	45
Quiescent Vcco25 2.50V:	2	5

Thermal summary:	
Estimated junction temperature:	28C
Ambient temp:	25C
Case temp:	27C
Theta J-A:	31C/W

Delay Analysis:

Timing Summary:

Speed Grade: -4

Minimum period: 2.554ns (Maximum Frequency: 391.543MHz)

Minimum input arrival time before clock: No path found

Maximum output required time after clock: 4.394ns

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

Timing constraint: Default period analysis for Clock 'f2/Q'

Clock period: 2.470ns (frequency: 404.858MHz)

Total number of paths / destination ports: 1 / 1

Delay: 2.470ns (Levels of Logic = 1)

Source: f3/Q (FF)

Destination: f3/Q (FF)

Source Clock: f2/Q falling

Destination Clock: f2/Q falling

Data Path: f3/Q to f3/Q

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	
FDC_1:C->Q	2	0.591	0.447	f3/Q (f3/Q)	
INV:I->O	1	0.704	0.420	f3/Q_not00011_INV_0 (f3/Q_not0001)	
FDC_1:D		0.308		f3/Q	

Total 2.470ns (1.603ns logic, 0.867ns route)
(64.9% logic, 35.1% route)

Timing constraint: Default period analysis for Clock 'f1/Q'

Clock period: 2.554ns (frequency: 391.543MHz)

Total number of paths / destination ports: 1 / 1

Delay: 2.554ns (Levels of Logic = 1)

Source: f2/Q (FF)

Destination: f2/Q (FF)

Source Clock: f1/Q falling

Destination Clock: f1/Q falling

Data Path: f2/Q to f2/Q

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	
FDC_1:C->Q	3	0.591	0.531	f2/Q (f2/Q)	
INV:I->O	1	0.704	0.420	f2/Q_not00011_INV_0 (f2/Q_not0001)	
FDC_1:D		0.308		f2/Q	

Total 2.554ns (1.603ns logic, 0.951ns route)
(62.8% logic, 37.2% route)

Timing constraint: Default period analysis for Clock 'f0/Q'

Clock period: 2.554ns (frequency: 391.543MHz)

Total number of paths / destination ports: 1 / 1

Delay: 2.554ns (Levels of Logic = 1)

Source: f1/Q (FF)

Destination: f1/Q (FF)

Source Clock: f0/Q falling

Destination Clock: f0/Q falling

Data Path: f1/Q to f1/Q

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name (Net Name)	
FDC_1:C->Q	3	0.591	0.531	f1/Q (f1/Q)	
INV:I->O	1	0.704	0.420	f1/Q_not00011_INV_0 (f1/Q_not0001)	
FDC_1:D		0.308		f1/Q	

Total 2.554ns (1.603ns logic, 0.951ns route)
(62.8% logic, 37.2% route)

Timing constraint: Default period analysis for Clock 'Cout'

Clock period: 2.554ns (frequency: 391.543MHz)

Total number of paths / destination ports: 1 / 1

Delay: 2.554ns (Levels of Logic = 1)

Source: f0/Q (FF)

Destination: f0/Q (FF)

Source Clock: Cout falling

Destination Clock: Cout falling

Data Path: f0/Q to f0/Q

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name	(Net Name)
FDC_1:C->Q	3	0.591	0.531	f0/Q (f0/Q)	
INV:I->O	1	0.704	0.420	f0/Q_not00011_INV_0 (f0/Q_not0001)	
FDC_1:D		0.308		f0/Q	
Total		2.554ns (1.603ns logic, 0.951ns route)		(62.8% logic, 37.2% route)	

Timing constraint: Default OFFSET OUT AFTER for Clock 'Cout'

Total number of paths / destination ports: 1 / 1

Offset: 4.394ns (Levels of Logic = 1)

Source: f0/Q (FF)

Destination: A0 (PAD)

Source Clock: Cout falling

Data Path: f0/Q to A0

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name	(Net Name)
FDC_1:C->Q	3	0.591	0.531	f0/Q (f0/Q)	
OBUF:I->O		3.272		A0_OBUF (A0)	
Total		4.394ns (3.863ns logic, 0.531ns route)		(87.9% logic, 12.1% route)	

Timing constraint: Default OFFSET OUT AFTER for Clock 'f0/Q'

Total number of paths / destination ports: 1 / 1

Offset: 4.394ns (Levels of Logic = 1)

Source: f1/Q (FF)

Destination: A1 (PAD)

Source Clock: f0/Q falling

Data Path: f1/Q to A1

	Gate	Net			
Cell:in->out	fanout	Delay	Delay	Logical Name	(Net Name)
FDC_1:C->Q	3	0.591	0.531	f1/Q (f1/Q)	
OBUF:I->O		3.272		A1_OBUF (A1)	
Total		4.394ns (3.863ns logic, 0.531ns route)		(87.9% logic, 12.1% route)	

Timing constraint: Default OFFSET OUT AFTER for Clock 'f1/Q'
Total number of paths / destination ports: 1 / 1

Offset: 4.394ns (Levels of Logic = 1)
Source: f2/Q (FF)
Destination: A2 (PAD)
Source Clock: f1/Q falling

Data Path: f2/Q to A2

Cell:in->out	Gate	Net	fanout	Delay	Delay	Logical Name (Net Name)
--------------	------	-----	--------	-------	-------	-------------------------

FDC_1:C->Q	3	0.591	0.531	f2/Q (f2/Q)
OBUF:I->O	3.272	A2_OBUF (A2)		

Total 4.394ns (3.863ns logic, 0.531ns route)
(87.9% logic, 12.1% route)

Timing constraint: Default OFFSET OUT AFTER for Clock 'f2/Q'
Total number of paths / destination ports: 1 / 1

Offset: 4.310ns (Levels of Logic = 1)
Source: f3/Q (FF)
Destination: A3 (PAD)
Source Clock: f2/Q falling

Data Path: f3/Q to A3

Cell:in->out	Gate	Net	fanout	Delay	Delay	Logical Name (Net Name)
--------------	------	-----	--------	-------	-------	-------------------------

FDC_1:C->Q	2	0.591	0.447	f3/Q (f3/Q)
OBUF:I->O	3.272	A3_OBUF (A3)		

Total 4.310ns (3.863ns logic, 0.447ns route)
(89.6% logic, 10.4% route)

CPU : 3.91 / 4.03 s | Elapsed : 4.00 / 4.00 s

PRBS GENERATOR:


CODING:

```
module prbs1 (rand, clk, reset);
input clk, reset;
output rand;
wire rand;
reg [3:0] temp;
always @ (posedge reset) begin
temp <= 4'hf;
end
always @ (posedge clk) begin
if (~reset) begin
temp <= {temp[0]^temp[1],temp[3],temp[2],temp[1]};
end
end
assign rand = temp[0];
endmodule
```

RTL SCHEMATIC:



TECHNOLOGY SCHEMATIC:

 

REPORT:

Area Analysis:

Device utilization summary:

Selected Device: 3s500eft256-4

Number of Slices: 0 out of 4656 0%
Number of IOs: 3
Number of bonded IOBs: 1 out of 190 0%

Partition Resource Summary:

No Partitions were found in this design.

Power Analysis:

Power summary:	I(mA)	P(mW)
Total estimated power consumption:		81
Vccint 1.20V:	26	31
Vccaux 2.50V:	18	45
Vcco25 2.50V:	2	5
Inputs:	0	0
Outputs:		
Vcco25	0	0
Signals:	0	0
Quiescent Vccint 1.20V:	26	31
Quiescent Vccaux 2.50V:	18	45
Quiescent Vcco25 2.50V:	2	5

Thermal summary:	
Estimated junction temperature:	28C
Ambient temp:	25C
Case temp:	27C
Theta J-A:	31C/W

Delay Analysis:

TIMING REPORT

NOTE: THESE TIMING NUMBERS ARE ONLY A SYNTHESIS ESTIMATE.

FOR ACCURATE TIMING INFORMATION PLEASE REFER TO THE TRACE REPORT GENERATED AFTER PLACE-and-ROUTE.

Clock Information:

No clock signals found in this design

Asynchronous Control Signals Information:

No asynchronous control signals found in this design

Timing Summary:

Speed Grade: -4

Minimum period: No path found

Minimum input arrival time before clock: No path found

Maximum output required time after clock: No path found

Maximum combinational path delay: No path found

Timing Detail:

All values displayed in nanoseconds (ns)

CPU: 3.84 / 4.19 s | Elapsed: 4.00 / 4.00 s

RESULT:

Thus, area, power and delay for Counter and PRBS generator was analyzed in FPGA Spartan 3E Trainer kit using Xilinx project navigator.

EXP NO: 6
Date:

Invoke PLL to generate Real Time Clock

AIM:

To invoke the FPGA Spartan 3E PLL to generate Real time Clock kit using Xilinx project navigator.

APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	XilinxProject navigator	1

PROCEDURE:

1. Start the Xilinx ISE by using Start → Program files → Xilinx ISE → project navigator
2. Click File → New Project
3. Enter the Project Name and select the location then click next
4. Select the Device and other category and click next twice and finish.
5. Click on the symbol of FPGA device and then right click → click on new source.
6. Select the Verilog Module and give the file name → click next and define ports → click next and finish.
7. Writing the Verilog Code in Verilog Editor.
8. Run the Check syntax → Process window → Synthesize → double click check syntax. If any errors found then remove the errors with proper syntax & coding.
9. Synthesis your design, from the source window select, synthesis/implementation from the window Now double click the Synthesis -XST.
10. After Synthesis, Click on the symbol of FPGA device and Right click and select New Source, Select Implementation Constraints File and type file name and click next.
11. Type the Net list and click save.
12. Implement the design by double clicking Implement design in the process window.
13. Then double click Generate Programming File, Double click Configure Target Device and click OK.
14. Double click Create PROM File in the ISE iMPACT window, Select Storage Target Device as Xilinx Flash PROM and click forward.
15. Add storage Device as xcf01s [2 M] and click forward, Type Output File Name and Location and click OK.
16. Select the corresponding .bit file and click Open, Click No to Add Another Device and Click OK.
17. Double click Generate File.
18. Double click Boundary Scan and Right click on the window and select Initialize Chain, Now Select the corresponding .mcs file and click open.
19. Click OK in the Device Programming Properties window, Download the Program on to the kit by Right clicking on the device icon and select program.
20. Verify the output in the target device.

FPGA Connections to Seven-Segment Display

SEGMENT	FPGA PIN
A	P8
B	P10
C	P9
D	P6
E	P4
F	P5
G	P3
DP	P11

CLOCK SOURCE

Spartan3E FPGA works in different Clock frequencies

Clock Input	FPGA PIN
CLK	A8
RST	J6

Digit Enable Signals

Display	DISP 1	DISP 2	DISP 3	DISP 4	DISP 5	DISP 6
FPGA PIN	P1	P2	P7	R4	R11	N14

PLL OSCILLATOR SETTINGS

For PLL, ICS525-01 or ICS525-02 is used. Select the clock settings as per the PLL in the On board

0 = Shorted

1 = Open

For any other CLK frequency in between 1MHz to 100MHz use the following formula.

$$\text{CLK frequency} = \text{Input frequency} * 2 \frac{(\text{VDW} + 8)}{(\text{RDW} + 2)(\text{OD})}$$

Where,

Reference Divider Word (RDW) = 1 to 127 (0 is not permitted)

VCO Divider Word (VDW) = 4 to 511 (0, 1, 2, 3 are not permitted)

Output Divider (OD) = values below

CODING:

System Clock = 20MHz

Verilog Program

```
// System clock Frequency 20MHz
```

```
// MODE Functions
```

```
// 00 HOURS
```

```
// 01 Minutes
```

```
// 10 Seconds
```

```
// 11 Timer ON
```

```
module timer(clk, rst, mode, set, sl, atoh);  
input clk; // System Clock  
input rst; // Reset(micro switch)  
input [1:0] mode; // Mode Selection(switch 1 & switch 2)  
input [7:0] set; // Set Value(switch 4 to switch 11)  
output [5:0] sl; // Segment Selection  
output [7:0] atoh; // Segment Display Control Data  
reg [5:0] sl;  
reg [7:0] atoh;  
reg [26:0] sig2;  
reg [19:1] sig3;  
reg [7:0] ssdigit1;  
reg [7:0] ssdigit2;  
reg [7:0] ssdigit3;  
reg [7:0] ssdigit4;  
reg [7:0] ssdigit5;  
reg [7:0] ssdigit6;  
reg [3:0] digit1;  
reg [3:0] digit2;  
reg [3:0] digit3;  
reg [3:0] digit4;  
reg [3:0] digit5;  
reg [3:0] digit6;  
always @ (posedge clk or negedge rst)  
begin  
if (rst == 1'b0) begin  
sig2 = 0;  
sig3 = 0;  
digit1 = 0;  
digit2 = 0;  
digit3 = 0;  
digit4 = 0;  
digit5 = 0;  
digit6 = 0;  
end  
end
```

```
else begin
if (mode == 2'b00) begin // Hours
if (set[7:4] <= 4'b0001) begin
digit1 = set[7:4];
if (set[3:0] <= 4'b1001)
digit2 = set[3:0];
else
digit2 = 0;
end
else if (set[7:4] == 4'b0010) begin
if (set[3:0] <= 4'b0011) begin
digit1 = set[7:4];
digit2 = set[3:0];
end
else begin
digit1 = 0;
digit2 = 0;
end
end
else begin
digit1 = 0;
digit2 = 0;
end
end
else if (mode == 2'b01) begin // Minutes
if (set[7:4] <= 4'b0101) begin
digit3 = set[7:4];
if (set[3:0] <= 4'b1001)
digit4 = set[3:0];
else
digit4 = 0;
end
else begin
digit3 = 0;
digit4 = 0;
end
end
else if (mode == 2'b10) begin // Seconds
if (set[7:4] <= 4'b0101) begin
digit5 = set[7:4];
if (set[3:0] <= 4'b1001)
digit6 = set[3:0];
else
digit6 = 0;
end
else begin
digit5 = 0;
digit6 = 0;
end
end
end
```

```

else begin
sig2 = sig2 + 1;

case (sig2[24:23]) //RTC Function
2'b00 : begin
digit6 = digit6 + 1;
if (digit6 > 4'b1001) begin
digit6 = 4'b0000;
digit5 = digit5 + 1;
if (digit5 > 4'b0101) begin
digit5 = 4'b0000;
digit4 = digit4 + 1;
if (digit4 > 4'b1001) begin
digit4 = 4'b0000;
digit3 = digit3 + 1;
if (digit3 > 4'b0101) begin
digit3 = 4'b0000;
digit2 = digit2 + 1;
if (digit2 > 4'b1001) begin
digit2 = 4'b0000;
digit1 = digit1 + 1;
end
if ((digit1 >= 4'b0010) & (digit2 >= 4'b0100))
begin
digit1 = 4'b0000;
digit2 = 4'b0000;
end
end
end
end
end
end

sig2[24:23] = 2'b01;
end

2'b11 : begin
if (sig2[22:19] == 4'b1001)
sig2 = 0;
end
default : begin
end
endcase
end

```

Display Settings

```
sig3 = sig3 + 1;
case (sig3[17:15])
3'b000 : begin
sl = 6'b111110;
case (digit1)
4'b0000 : ssdigit1 = 8'b00111111;
4'b0001 : ssdigit1 = 8'b00000110;
4'b0010 : ssdigit1 = 8'b01011011;
default : ssdigit1 = 8'b00000000;
endcase
atoh = ssdigit1;
end
```

```
3'b001 : begin
sl = 6'b111101;
case (digit2)
4'b0000 : ssdigit2 = 8'b00111111;
4'b0001 : ssdigit2 = 8'b00000110;
4'b0010 : ssdigit2 = 8'b01011011;
4'b0011 : ssdigit2 = 8'b01001111;
4'b0100 : ssdigit2 = 8'b01100110;
4'b0101 : ssdigit2 = 8'b01101101;
4'b0110 : ssdigit2 = 8'b01111101;
4'b0111 : ssdigit2 = 8'b00000111;
4'b1000 : ssdigit2 = 8'b01111111;
4'b1001 : ssdigit2 = 8'b01101111;
default : ssdigit2 = 8'b00000000;
endcase
atoh = ssdigit2;
end
```

```
3'b011 : begin
sl = 6'b111011;
case (digit3)
4'b0000 : ssdigit3 = 8'b00111111;
4'b0001 : ssdigit3 = 8'b00000110;
4'b0010 : ssdigit3 = 8'b01011011;
4'b0011 : ssdigit3 = 8'b01001111;
4'b0100 : ssdigit3 = 8'b01100110;
4'b0101 : ssdigit3 = 8'b01101101;
default : ssdigit3 = 8'b00000000
endcase
atoh = ssdigit3;
end
```


```
3'b100 : begin
sl = 6'b110111;
case (digit4)
4'b0000 : ssdigit4 = 8'b00111111;
4'b0001 : ssdigit4 = 8'b00000110;
4'b0010 : ssdigit4 = 8'b01011011;
```

```
4'b0011 : ssdigit4 = 8'b01001111;
4'b0100 : ssdigit4 = 8'b01100110;
4'b0101 : ssdigit4 = 8'b01101101;
4'b0110 : ssdigit4 = 8'b01111101;
4'b0111 : ssdigit4 = 8'b00000111;
4'b1000 : ssdigit4 = 8'b01111111;
4'b1001 : ssdigit4 = 8'b01101111;
default : ssdigit4 = 8'b00000000;
endcase
atoh = ssdigit4;
end
```


```
3'b110 : begin
sl = 6'b101111;
case (digit5)
4'b0000 : ssdigit5 = 8'b00111111;
4'b0001 : ssdigit5 = 8'b00000110;
4'b0010 : ssdigit5 = 8'b01011011;
4'b0011 : ssdigit5 = 8'b01001111;
4'b0100 : ssdigit5 = 8'b01100110;
4'b0101 : ssdigit5 = 8'b01101101;
default : ssdigit5 = 8'b00000000;
endcase
atoh = ssdigit5;
end
```

```
3'b111 : begin
sl = 6'b011111;
case (digit6)
4'b0000 : ssdigit6 = 8'b00111111;
4'b0001 : ssdigit6 = 8'b00000110;
4'b0010 : ssdigit6 = 8'b01011011;
4'b0011 : ssdigit6 = 8'b01001111;
4'b0100 : ssdigit6 = 8'b01100110;
4'b0101 : ssdigit6 = 8'b01101101;
4'b0110 : ssdigit6 = 8'b01111101;
4'b0111 : ssdigit6 = 8'b00000111;
4'b1000 : ssdigit6 = 8'b01111111;
4'b1001 : ssdigit6 = 8'b01101111;
default : ssdigit6 = 8'b00000000;
endcase
atoh = ssdigit6;
end
endcase
end
end
endmodule
```


RTL SCHEMATIC

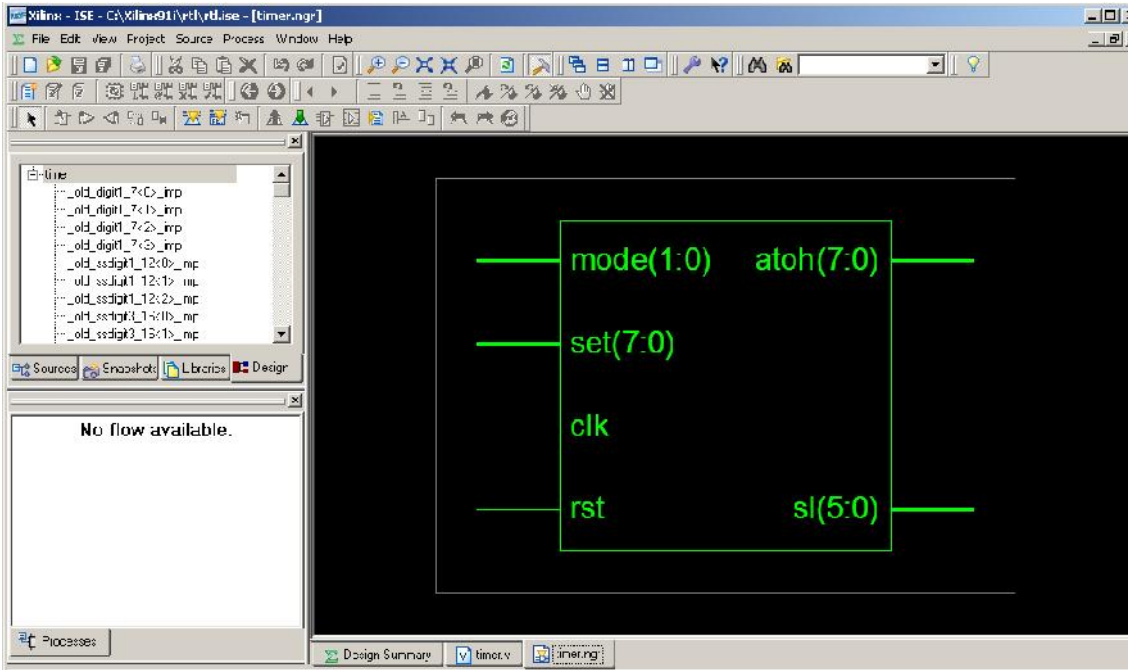

TECHNOLOGY SCHEMATIC

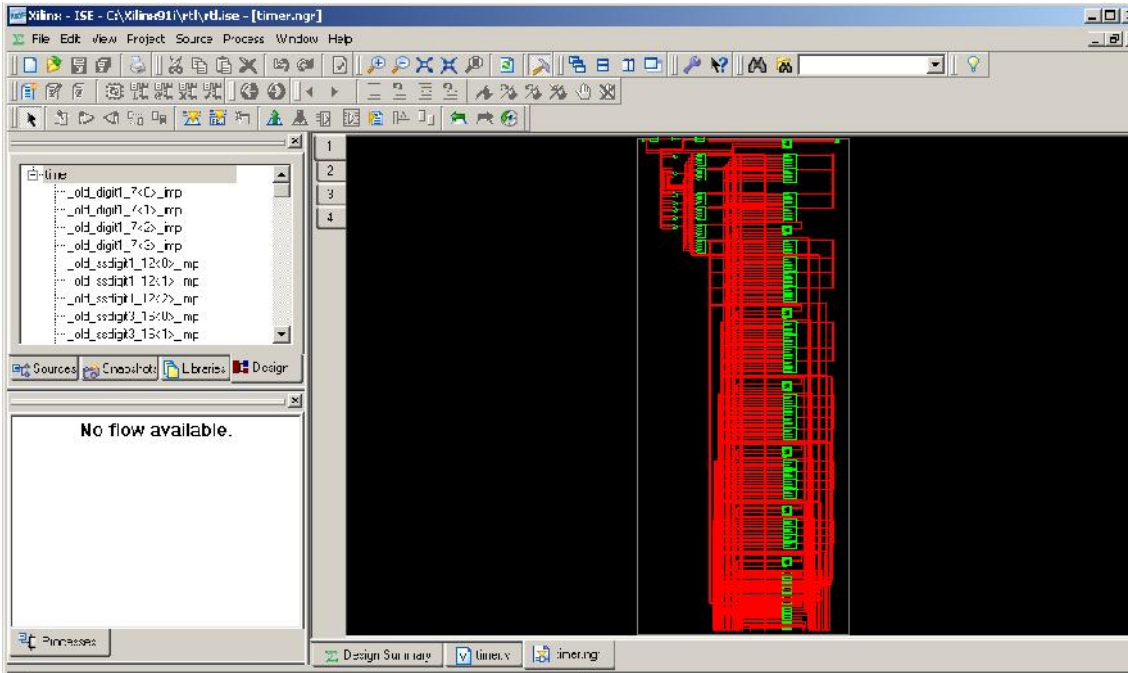

HARDWARE FUSING

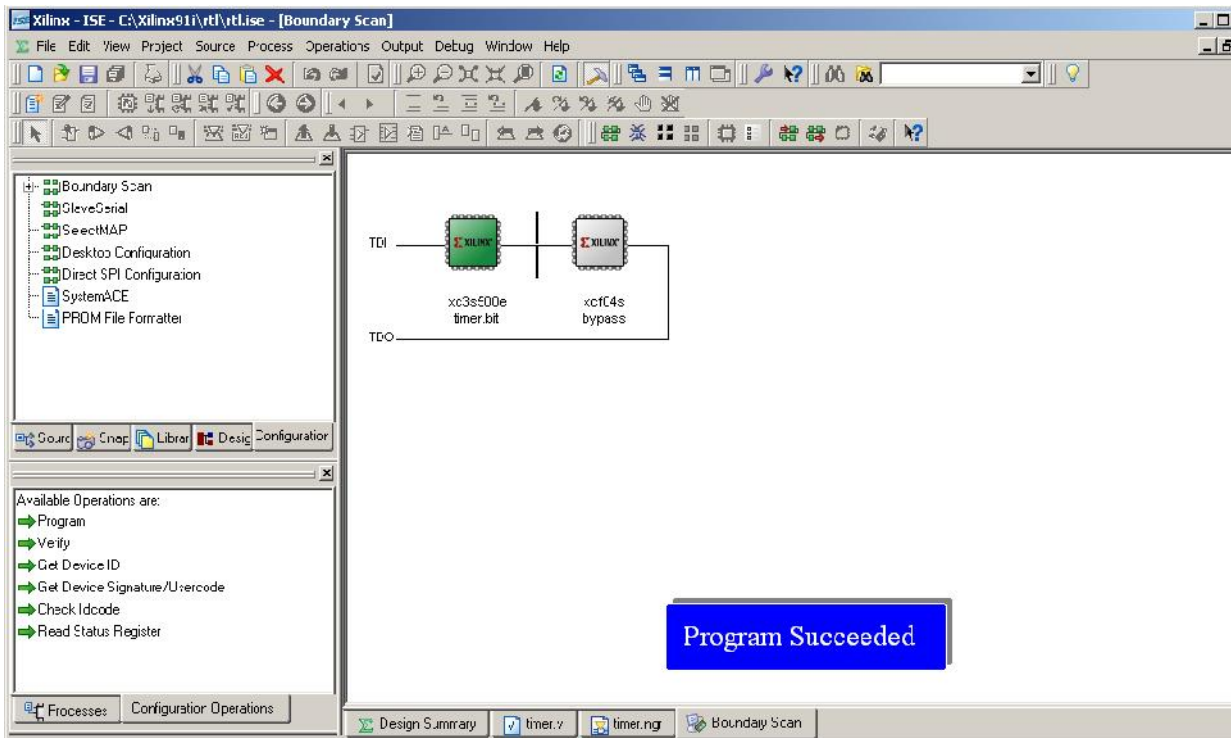


RESULT:

Thus, the FPGA Spartan 3E PLL was invoked to generate Real time Clock in kit using Xilinx project navigator.


LT SPICE

Procedure for simulation and implementation of EDA tool-LtSPICE

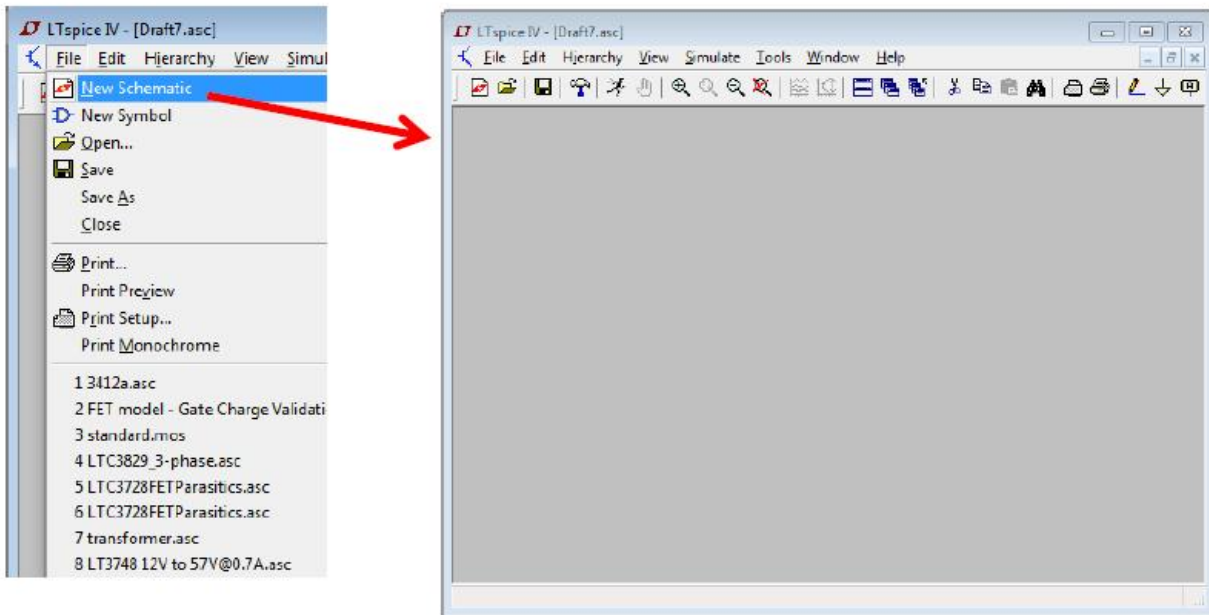- ❖ Step 1: Open up a blank schematic screen
 - ❖ Select "File" Menu and "New Schematic"




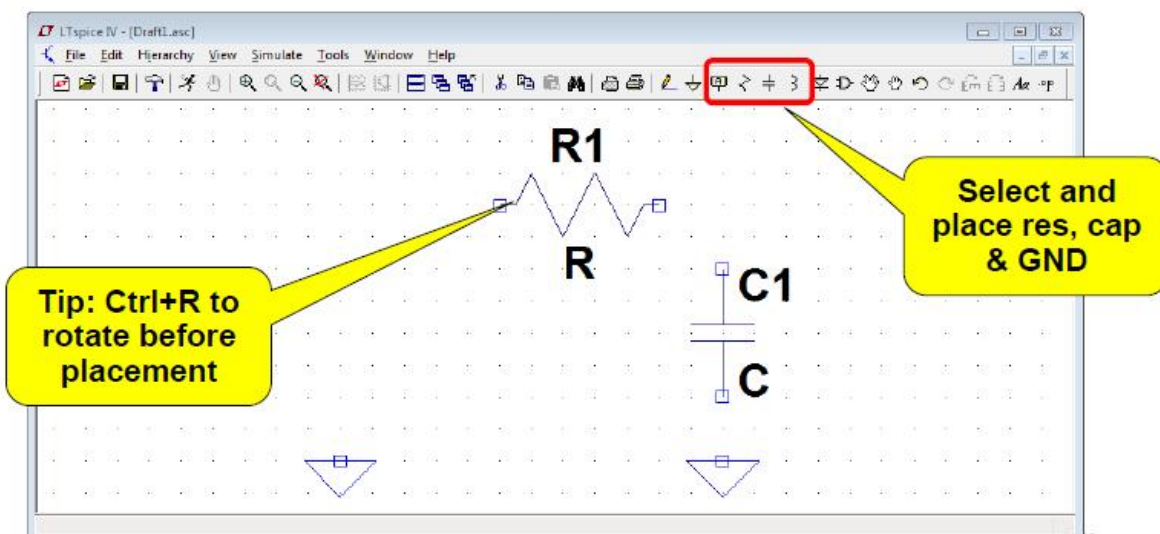- ❖ Step 2: Add the passives and grounds
 - ❖ Using the toolbar, select Resistor, Capacitor and Ground. Place these symbols on the schematic as shown below. Use Ctrl+R to rotate before placement.




❖ Step 3: Add the voltage source

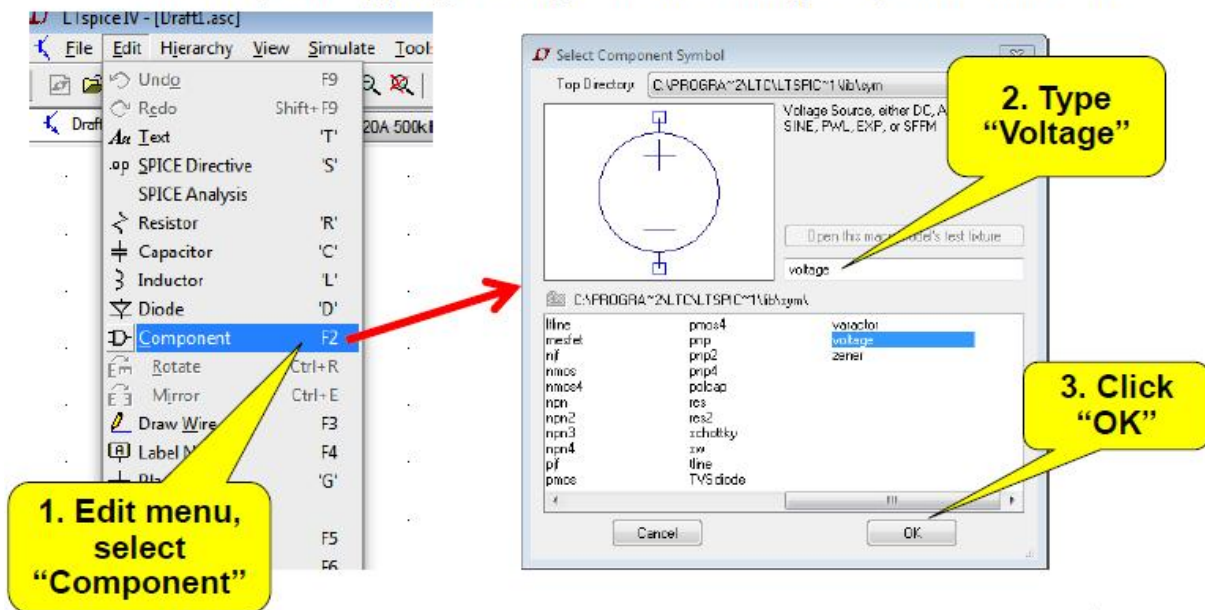- ❖ Select “Edit” Menu and “Component”. From the component window, start typing “voltage” in the dialog box, and click “OK”




Toolbar and Keyboard Shortcuts

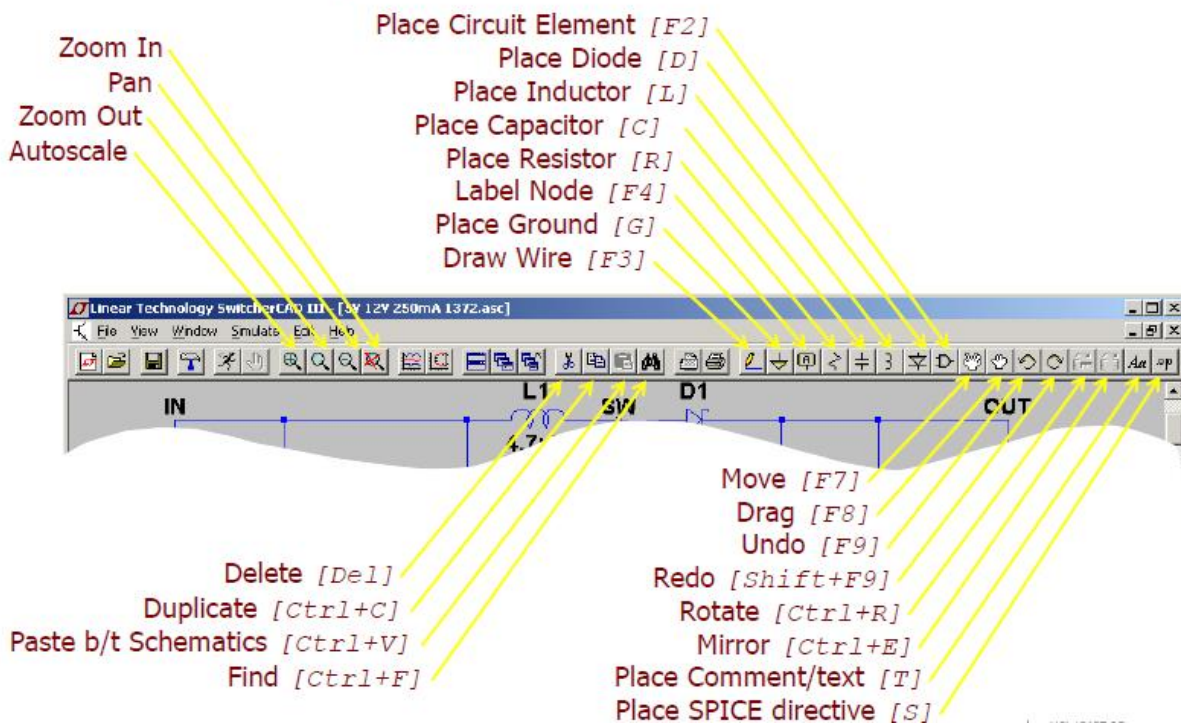


❖ Step 4: Wire up the circuit

- ❖ Using the toolbar, select Wire

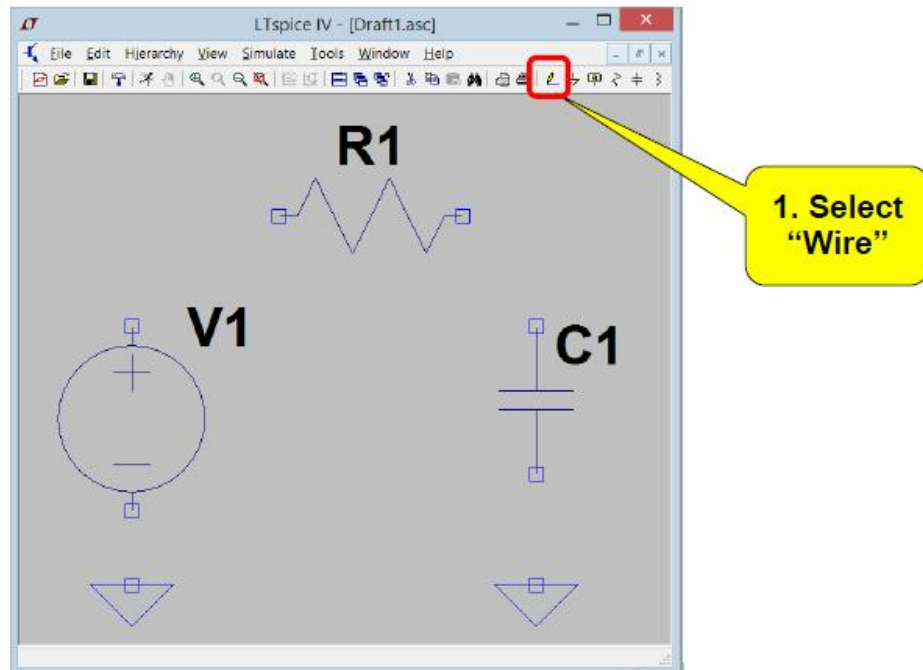


❖ Step 4: Wire up the circuit (cont.)

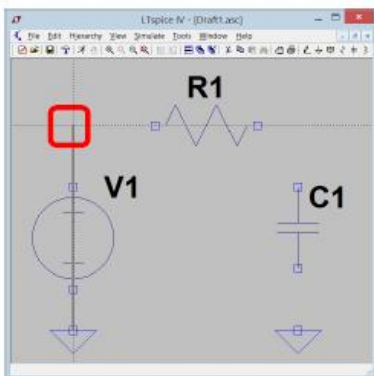

Left-Click ground


"Pull" wire up through the source

Left-Click here  to anchor

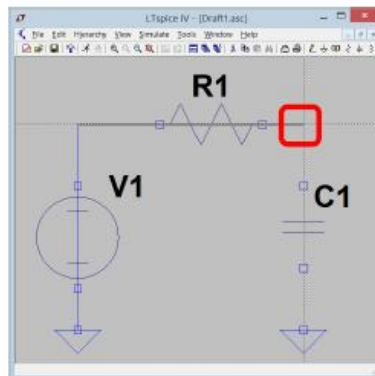

"Pull" wire through the resistor

Left-Click here  to anchor

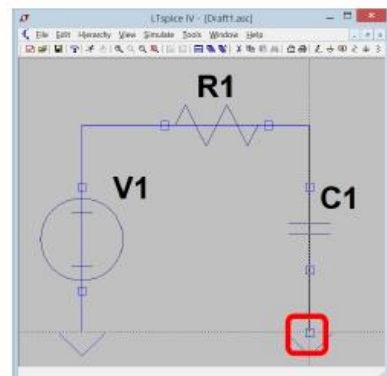

"Pull" wire down through the capacitor

Left-Click here  to anchor & finish

Hint: Press the ESC key at any time to clean up the schematic

❖ Step 5: Add net labels

- ❖ Using the toolbar, select Label Net. Label the input/output nodes as shown below

The screenshot shows the LTspice IV interface with a circuit diagram. A yellow callout box labeled "1. Select 'Label Net'" points to the "Label Net" icon in the toolbar. Another yellow callout box labeled "2. Enter net name" points to the "Net Name" dialog box, which has "IN" entered in the text field. A third yellow callout box labeled "3. Place on wire" points to the "IN" label placed on the wire connecting the voltage source V1 to the resistor R1.

❖ Step 6a: Component values

- ❖ Right-Click on each component symbol to change its value as shown below

The screenshot shows the circuit diagram with component values. A yellow callout box labeled "Right-click on symbol" points to the resistor R1. Another yellow callout box labeled "Or Right-click on value" points to the "10k" value. The "Resistor - R1" dialog box is open, showing "Resistance(Ω): 10k". The "Enter new Value for R1" dialog box is also open, showing "10k" in the text field.

❖ Step 6b: Source parameters

- ❖ Right-Click on the voltage source and enter the parameters shown below under the "Advanced" tab.

Right-click source

Click "Advanced"

Voltage Source - V1

DC value[V]:

Series Resistance[Ω]:

OK Cancel Advanced

Independent Voltage Source - V1

Functions

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Tton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE: Browse

Vinitial[V]: 0

Von[V]: 5

Tdelay[s]: 0

Trise[s]: 1u

Tfall[s]: 1u

Ton[s]: 10m

Tperiod[s]: 20m

Ncycles: 3

Additional PWL Points:

Make this information visible on schematic:

DC Value

DC value:

Make this information visible on schematic:

Small signal AC analysis(AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic:

Parasitic Properties

Series Resistance[Ω]:

Parallel Capacitance[F]:

Make this information visible on schematic:

Cancel OK

❖ Step 6b: Source parameters

- ❖ Right-Click on the voltage source and enter the parameters shown below under the "Advanced" tab.

Independent Voltage Source - V1

Functions

- (none)
- PULSE(V1 V2 Tdelay Trise Tfall Tton Period Ncycles)
- SINE(Voffset Vamp Freq Td Theta Phi Ncycles)
- EXP(V1 V2 Td1 Tau1 Td2 Tau2)
- SFFM(Voff Vamp Fcar MDI Fsig)
- PWL(t1 v1 t2 v2...)
- PWL FILE: Browse

Vinitial[V]: 0

Von[V]: 5

Tdelay[s]: 0

Trise[s]: 1u

Tfall[s]: 1u

Ton[s]: 10m

Tperiod[s]: 20m

Ncycles: 3

Additional PWL Points:

Make this information visible on schematic:

DC Value

DC value:

Make this information visible on schematic:

Small signal AC analysis(AC)

AC Amplitude:

AC Phase:

Make this information visible on schematic:

Parasitic Properties



Series Resistance[Ω]:


Parallel Capacitance[F]:

Make this information visible on schematic:


Cancel OK

- DC Sweep

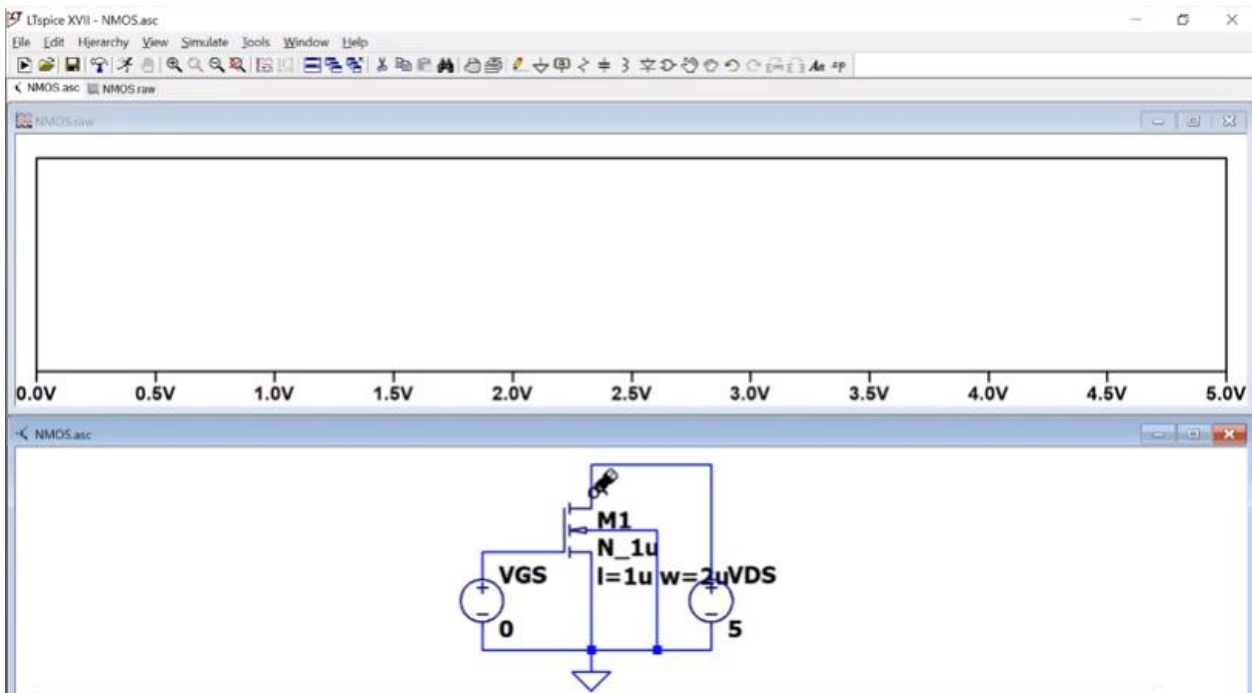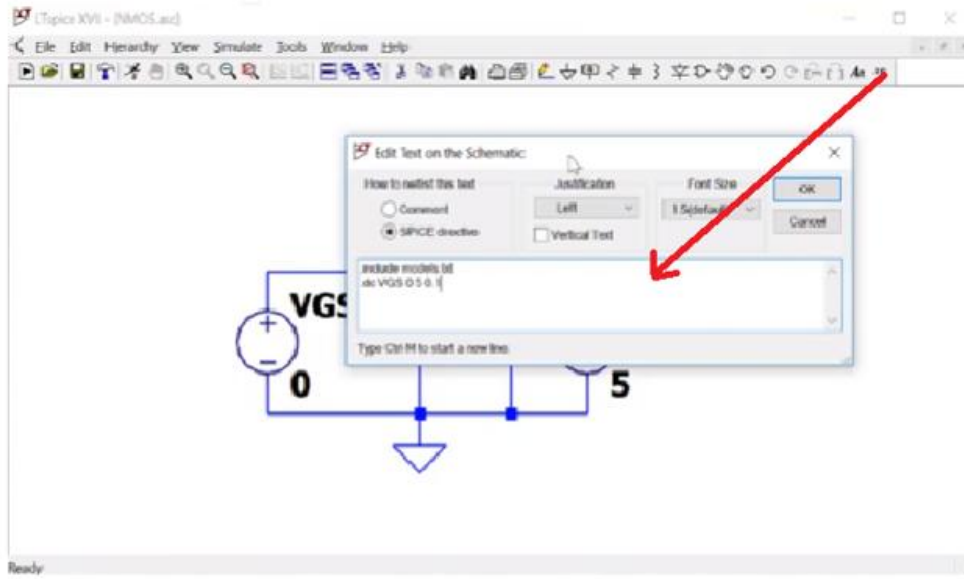


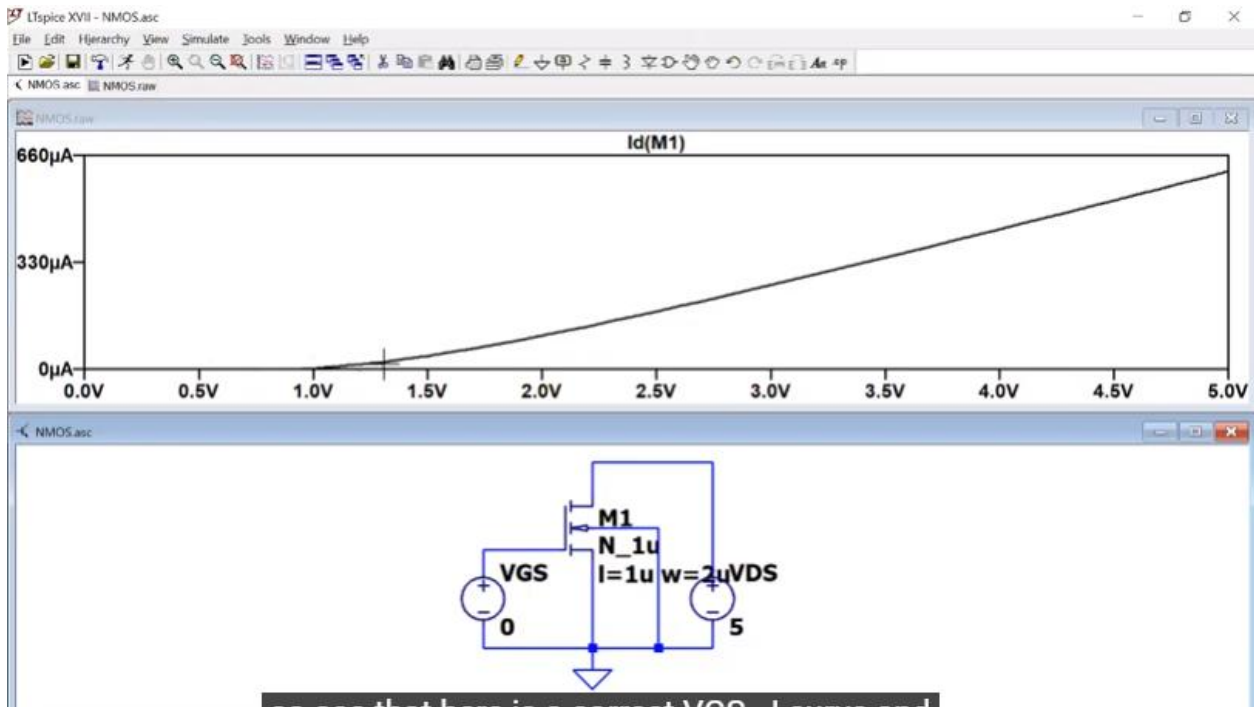

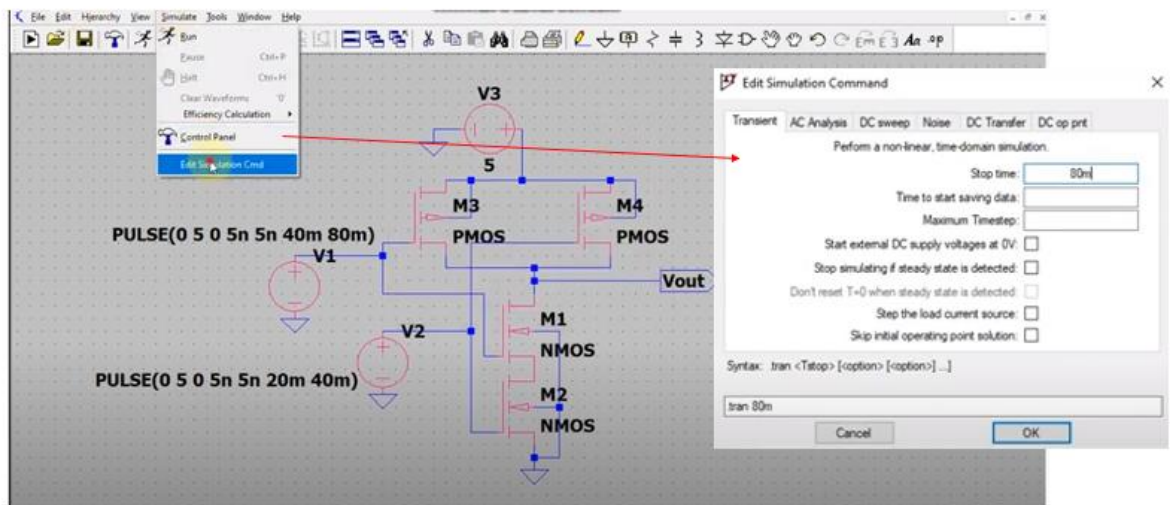
- Run the Simulation for Transient Response



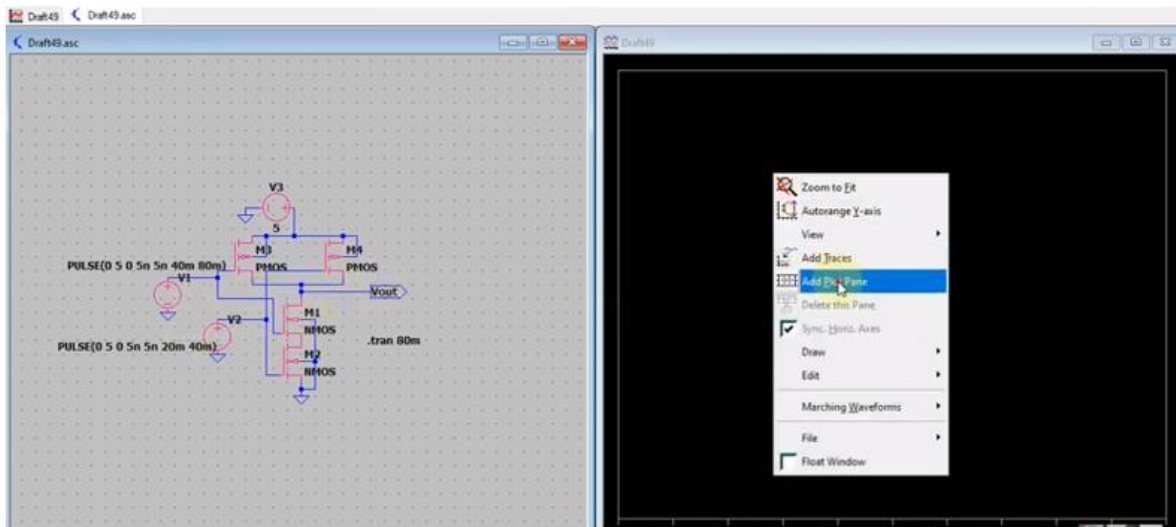- Add pane to output
- Right click -> add new pane



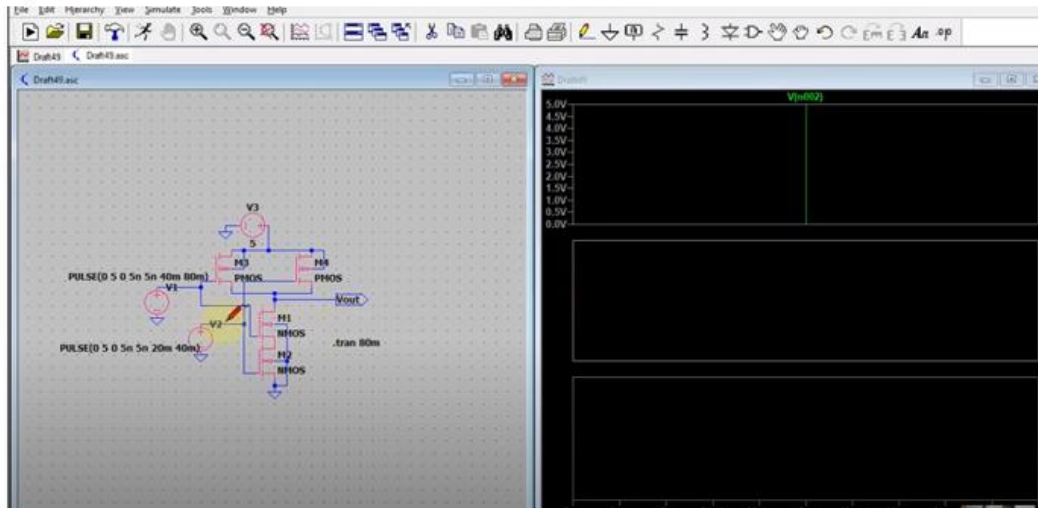- Viewing Differential Voltage Waveforms
- **Left-Click** on one node and drag the mouse to another node
- Red voltage probe at the first node
- Black probe on the second



TRANSISTOR MODELS

* Long channel models from CMOS Circuit Design, Layout, and Simulation,
* Level=3 models VDD=5V, see CMOSedu.com

*

.MODEL N_1u NMOS LEVEL = 3

```
+ TOX = 200E-10   NSUB = 1E17   GAMMA = 0.5
+ PHI = 0.7      VTO = 0.8     DELTA = 3.0
+ UO = 650      ETA = 3.0E-6   THETA = 0.1
+ KP = 120E-6   VMAX = 1E5    KAPPA = 0.3
+ RSH = 0       NFS = 1E12    TPG = 1
+ XJ = 500E-9   LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6   PB = 1      MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5
```

*

.MODEL P_1u PMOS LEVEL = 3

```
+ TOX = 200E-10   NSUB = 1E17   GAMMA = 0.6
+ PHI = 0.7      VTO = -0.9    DELTA = 0.1
+ UO = 250      ETA = 0      THETA = 0.1
+ KP = 40E-6    VMAX = 5E4    KAPPA = 1
+ RSH = 0       NFS = 1E12    TPG = -1
+ XJ = 500E-9   LD = 100E-9
+ CGDO = 200E-12 CGSO = 200E-12 CGBO = 1E-10
+ CJ = 400E-6   PB = 1      MJ = 0.5
+ CJSW = 300E-12 MJSW = 0.5
```

*

*

* Short channel models from CMOS Circuit Design, Layout, and Simulation,

* 50nm BSIM4 models VDD=1V, see CMOSedu.com

*

```
.model N_50n nmos level = 54
+binunit = 1   paramchk = 1   mobmod = 0
```



```

+capmod = 2      igcmod = 1      igbmod = 1      geomod = 0
+diomod = 1      rdsmod = 0      rbodymod= 1     rgatemod= 1
      +permod = 1      acnqsmod= 0     trnqsmod= 0
+tnom  = 27      toxo  = 1.4e-009  toxp  = 7e-010   toxm  = 1.4e-009
      +epsrox = 3.9      wint  = 5e-009   lint  = 1.2e-008
      +ll    = 0        wl    = 0        lln   = 1        wln   = 1
      +lw    = 0        ww    = 0        lwn   = 1        wwn   = 1
+lw1   = 0        ww1   = 0        xpart = 0        toxref = 1.4e-009
      +vth0  = 0.22      k1    = 0.35      k2    = 0.05      k3    = 0
+3k3b  = 0        w0    = 2.5e-006  dvt0  = 2.8       dvt1  = 0.52
      +dvt2  = -0.032    dvt0w = 0        dvt1w = 0        dvt2w = 0
+dsusb  = 2        minv  = 0.05      voffl  = 0        dvtp0  = 1e-007
+dvtp1 = 0.05      lpe0  = 5.75e-008  lpeb  = 2.3e-010  xj    = 2e-008
+ngate  = 5e+020    ndep  = 2.8e+018  nsd   = 1e+020    phin  = 0
      +cdsc  = 0.0002    cdsch = 0        cdsch = 0        cit   = 0
      +voff  = -0.15     nfactor = 1.2     eta0  = 0.15     etab  = 0
+vfb   = -0.55     u0    = 0.032     ua    = 1.6e-010  ub    = 1.1e-017
+uc    = -3e-011   vsat  = 1.1e+005  a0    = 2        ags   = 1e-020
      +a1    = 0        a2    = 1        b0    = -1e-020  b1    = 0
      +keta  = 0.04     dwg   = 0        dwb   = 0        pclm  = 0.18
+pdiblc1 = 0.028    pdiblc2 = 0.022  pdiblc = -0.005  drout = 0.45
+pvag  = 1e-020    delta = 0.01     pscbe1 = 8.14e+008  pscbe2 = 1e-007
+fprou = 0.2       pdits  = 0.2     pditsd = 0.23    pditsl = 2.3e+006
      +rsh   = 3        rdsw  = 150     rsw   = 150     rdw   = 150
      +rdswmin = 0      rdwmin = 0      rswmin = 0      prwg  = 0
+prwb  = 6.8e-011  wr    = 1        alpha0 = 0.074    alpha1 = 0.005
+beta0 = 30        agidl  = 0.0002  bgidl  = 2.1e+009  cgidl  = 0.0002
      +egidl = 0.8
      +aigbacc = 0.012    bigbacc = 0.0028  cigbacc = 0.002
+nigbacc = 1       aigbinv = 0.014  bigbinv = 0.004  cigbinv = 0.004
+eigbinv = 1.1    nigbinv = 3      aigc  = 0.017    bigc  = 0.0028
+cigc  = 0.002    aigsd  = 0.017  bigsd  = 0.0028  cigsd  = 0.002
      +nigc  = 1        poxedge = 1     pigcd  = 1        ntox  = 1
      +xrcrg1 = 12      xrcrg2 = 5
+cgso  = 6.238e-010  cgdo  = 6.238e-010  cgbo  = 2.56e-011  cgdl  = 2.495e-10
+cgsl  = 2.495e-10  ckappas = 0.02    ckappad = 0.02    acde  = 1
      +moin  = 15       noff   = 0.9     voffcv = 0.02
+kt1   = -0.21     kt1l  = 0.0      kt2   = -0.042    ute   = -1.5
+ua1   = 1e-009    ub1   = -3.5e-019  uc1   = 0         prt   = 0
      +at    = 53000
      +fnoimod = 1      tnoimod = 0
+js    = 0.0001    jsws  = 1e-011   jswgs = 1e-010   njs   = 1
+ijthsfwd = 0.01    ijthsrev = 0.001  bvs   = 10       xjbvs = 1
+jsd   = 0.0001    jswd  = 1e-011   jswgd = 1e-010   njd   = 1
+ijthdfwd = 0.01    ijthdrev = 0.001  bvd   = 10       xjbvd = 1
      +pbs   = 1        cjs   = 0.0005   mjs   = 0.5      pbsws = 1
+cjsws = 5e-010    mjsws = 0.33     pbswgs = 1       cjswgs = 5e-010
      +mjswgs = 0.33    pbd   = 1        cjd   = 0.0005   mjd   = 0.5
+pbswd = 1        cjswd = 5e-010  mjswd = 0.33     pbswgd = 1
+cjswgd = 5e-010  mjswgd = 0.33   tpb   = 0.005    tcj   = 0.001
+tpbsw = 0.005    tcjsw = 0.001   tpbswg = 0.005   tcjswg = 0.001

```

```

+xtis = 3      xtid = 3
+dmcg = 0e-006  dmci = 0e-006  dmdg = 0e-006  dmcgt = 0e-007
+dwj = 0e-008  xgw = 0e-007  xgl = 0e-008
+rshg = 0.4    gbmin = 1e-010  rbpb = 5      rbpd = 15
+rbps = 15    rbdb = 15      rbsb = 15     ngcon = 1

```

*

```

.model P_50n pmos level = 54
+binunit = 1      paramchk = 1      mobmod = 0
+capmod = 2      igcmmod = 1      igbmod = 1      geomod = 0
+diomod = 1      rdsmod = 0      rbodymod = 1    rgatemod = 1
+permod = 1      acnqsmod = 0      trnqsmod = 0
+tnom = 27      toxex = 1.4e-009  toxp = 7e-010  toxm = 1.4e-009
+epsrox = 3.9    wint = 5e-009    lint = 1.2e-008
+ll = 0          wl = 0          lln = 1         wln = 1
+lw = 0          ww = 0          lwn = 1         wwn = 1
+lw1 = 0         ww1 = 0         xpart = 0       toxref = 1.4e-009
+vth0 = -0.22    k1 = 0.39       k2 = 0.05       k3 = 0
+k3b = 0         w0 = 2.5e-006  dvt0 = 3.9      dvt1 = 0.635
+dvt2 = -0.032  dvt0w = 0       dvt1w = 0       dvt2w = 0
+dsup = 0.7     minv = 0.05     voff1 = 0       dvtp0 = 0.5e-008
+dvtp1 = 0.05   lpe0 = 5.75e-008  lpeb = 2.3e-010  xj = 2e-008
+ngate = 5e+020  ndep = 2.8e+018  nsd = 1e+020    phin = 0
+cdsc = 0.000258  cdsb = 0        cdsd = 6.1e-008  cit = 0
+voff = -0.15    nfactor = 2     eta0 = 0.15     etab = 0
+vfb = 0.55     u0 = 0.0095     ua = 1.6e-009   ub = 8e-018
+uc = 4.6e-013  vsat = 90000    a0 = 1.2        ags = 1e-020

+a1 = 0          a2 = 1          b0 = -1e-020    b1 = 0
+keta = -0.047  dwg = 0         dwb = 0         pclm = 0.55
+pdiblc1 = 0.03  pdiblc2 = 0.0055  pdiblc3 = 3.4e-008  drout = 0.56
+pvag = 1e-020  delta = 0.014    pscbe1 = 8.14e+008  pscbe2 = 9.58e-007
+fprout = 0.2   pdits = 0.2     pditsd = 0.23    pditsl = 2.3e+006
+rsh = 3        rdsw = 250      rsw = 160        rdw = 160
+rdswmin = 0    rdwmin = 0      rswmin = 0       prwg = 3.22e-008
+prwb = 6.8e-011  wr = 1         alpha0 = 0.074   alpha1 = 0.005
+beta0 = 30     agidl = 0.0002  bgidl = 2.1e+009  cgidl = 0.0002
+egidl = 0.8

+aigbacc = 0.012  bigbacc = 0.0028  cigbacc = 0.002
+nigbacc = 1     aigbinv = 0.014  bigbinv = 0.004  cigbinv = 0.004
+eigbinv = 1.1   nigbinv = 3      aigc = 0.69     bigc = 0.0012
+cigc = 0.0008   aigsd = 0.0087  bigsd = 0.0012  cigsd = 0.0008
+nigc = 1        poxedge = 1     pigcd = 1       ntox = 1
+xrcrg1 = 12     xrcrg2 = 5

+cgso = 7.43e-010  cgdo = 7.43e-010  cgbo = 2.56e-011  cgdl = 1e-014
+cgsl = 1e-014    ckappas = 0.5    ckappad = 0.5    acde = 1
+moin = 15       noff = 0.9      voffcv = 0.02
+kt1 = -0.19     kt1l = 0        kt2 = -0.052    ute = -1.5
+ua1 = -1e-009   ub1 = 2e-018    uc1 = 0         prt = 0
+at = 33000


+fnoimod = 1     tnoimod = 0
+jss = 0.0001    jsws = 1e-011   jswgs = 1e-010  njs = 1
+ijunswd = 0.01  ijunrev = 0.001  bvs = 10        xjovs = 1

```

+jsd = 0.0001	jswd = 1e-011	jswgd = 1e-010	njd = 1
+ijthdfwd= 0.01	ijthdrev= 0.001	bvd = 10	xjbvd = 1
+pbs = 1	cjs = 0.0005	mjs = 0.5	pbsws = 1
+cjsws = 5e-010	mjsws = 0.33	pbswgs = 1	cjswgs = 5e-010
+mjswgs = 0.33	pbd = 1	cjd = 0.0005	mjd = 0.5
pbswd = 1	cjswd = 5e-010	mjswd = 0.33	pbswgd = 1
+cjswgd = 5e-010	mjswgd = 0.33	tpb = 0.005	tcj = 0.001
+tpbsw = 0.005	tcjsw = 0.001	tpbswg = 0.005	tcjswg = 0.001
	+xtis = 3	xtid = 3	
+dmcg = 0e-006	dmci = 0e-006	dmdg = 0e-006	dmcgt = 0e-007
+dwj = 0e-008	xgw = 0e-007	xgl = 0e-008	
rshg = 0.4	gbmin = 1e-010	rbpb = 5	rbpd = 15
+rbps = 15	rbdb = 15	rbsb = 15	ngcon = 1


ELECTRIC VLSI DESIGN EDA TOOL

 1. Start Electric: The following window will appear.



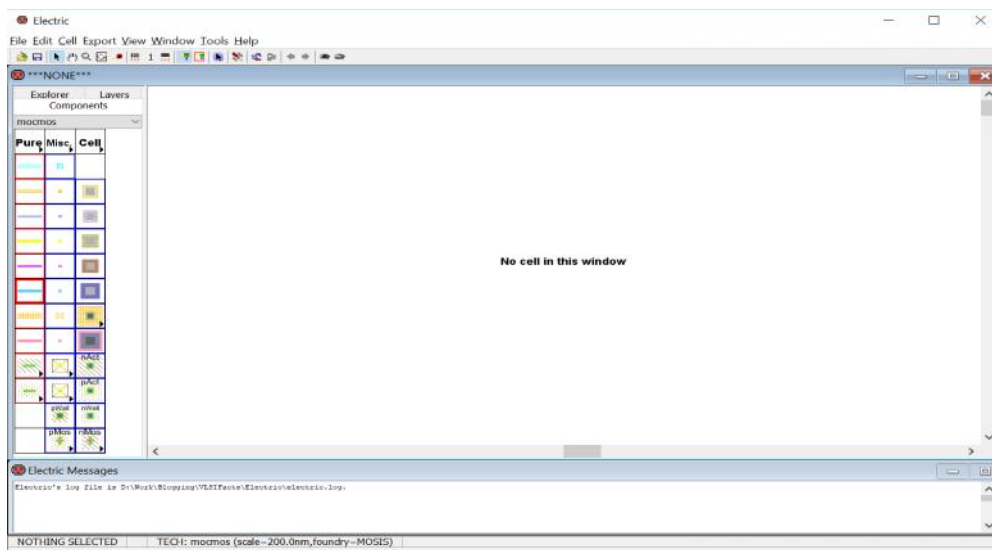
2. Towards the bottom of the window, Electric Messages Window will be found where different messages can be found throughout any design.
3. The background color of the window can change as follows

Window → Color Schemes → White Background Colors



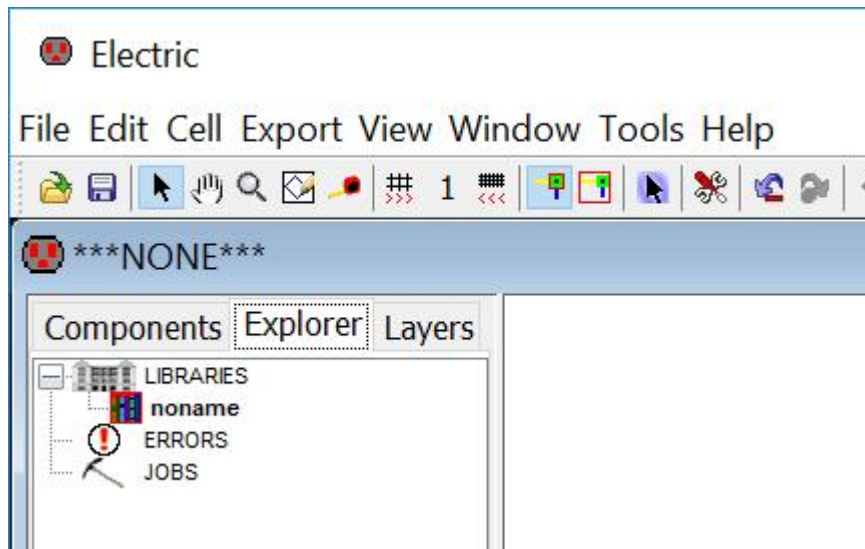4. **Let's create a Library**

Go to **Explorer** (beside the **Components** view); you will find **LIBRARIES** name as no name




5. **File -> Save Library As**

Go to the location where design have to be save. (eg: $\$PATH/Electric/Designs$)

Name the design (library name) eg. design_1.jelib

We would create our schematic and layout under this library

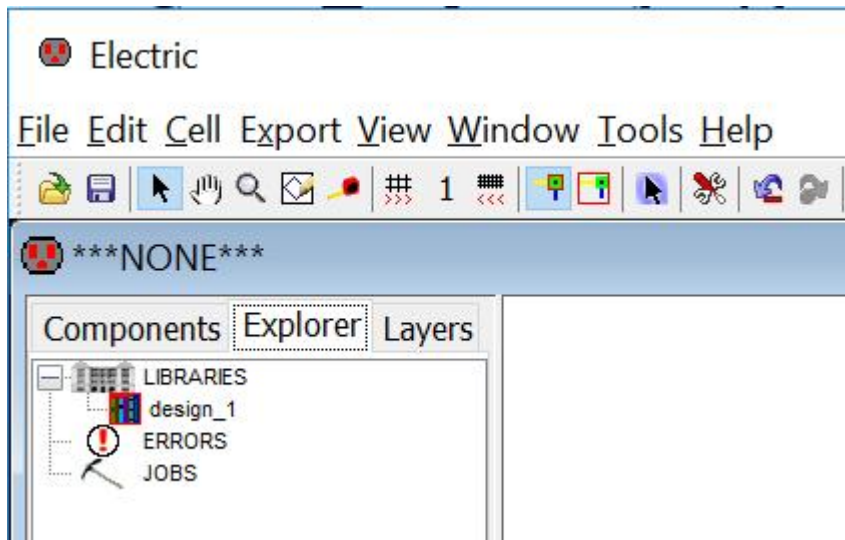Now you will see design_1.jelib under LIBRARIES name in Explorer




6. **Go to Preferences by clicking the following button or executing File -> Preferences...**
7. Then you have to set the following.

Preferences -> Categories -> Technology -> Technology

mocmos Technology -> Metal layers -> 3 Layers


Keep submicron rules and Second Polysilicon Layer checked

Click the Analog checkbox.

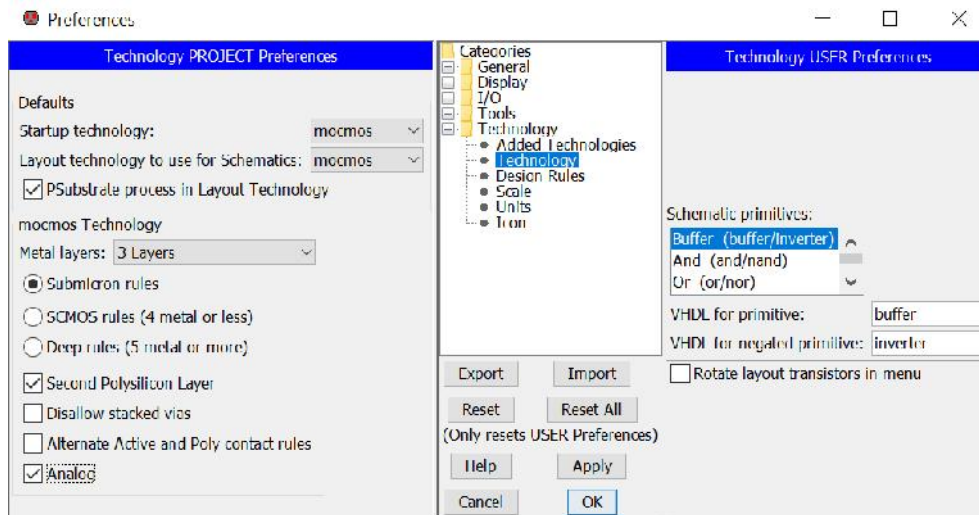

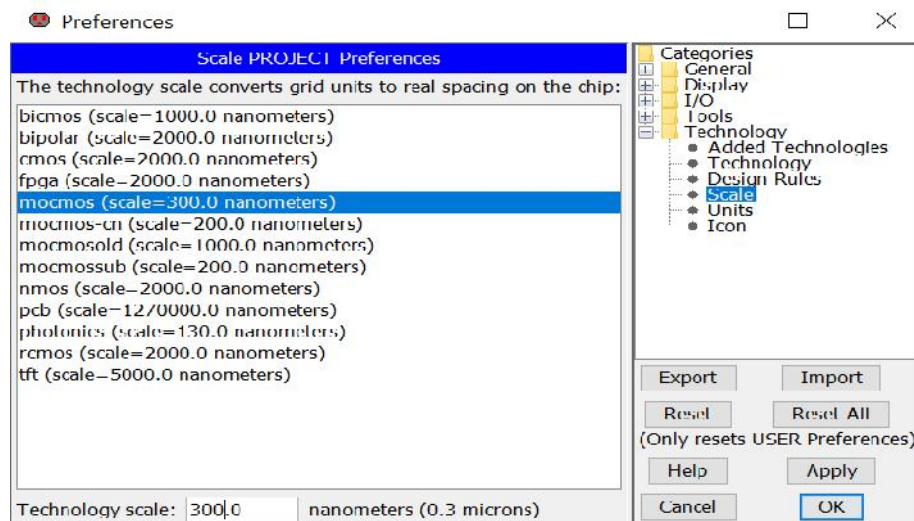
8. To set the scale go to

File -> Preferences -> Technology -> Scale and set mocmos scale to 300 nm



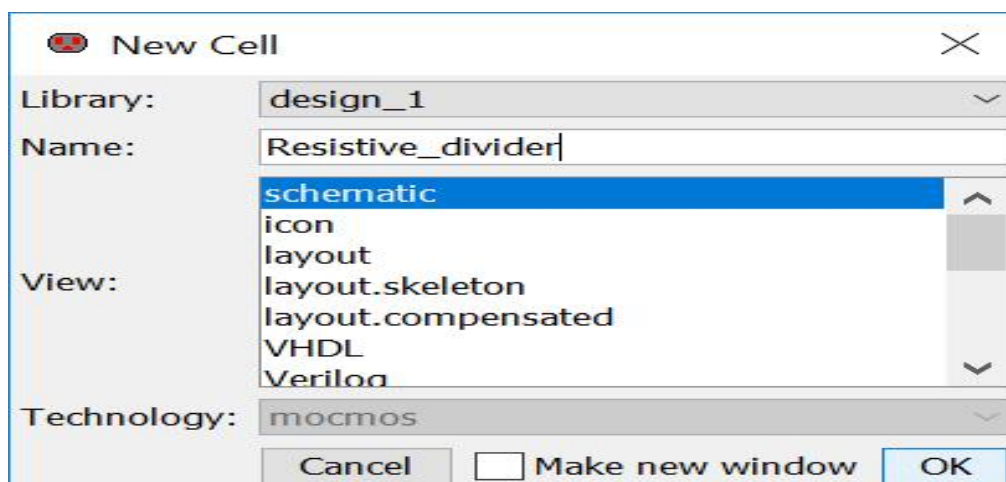9. **Creating a new cell**


Go to **cell -> New Cell** (or you can press **ctrl + N**). You will find a window like following.




Enter the **name** of the cell {----- } and click the **view** as {schematic}.

Press **ok**.

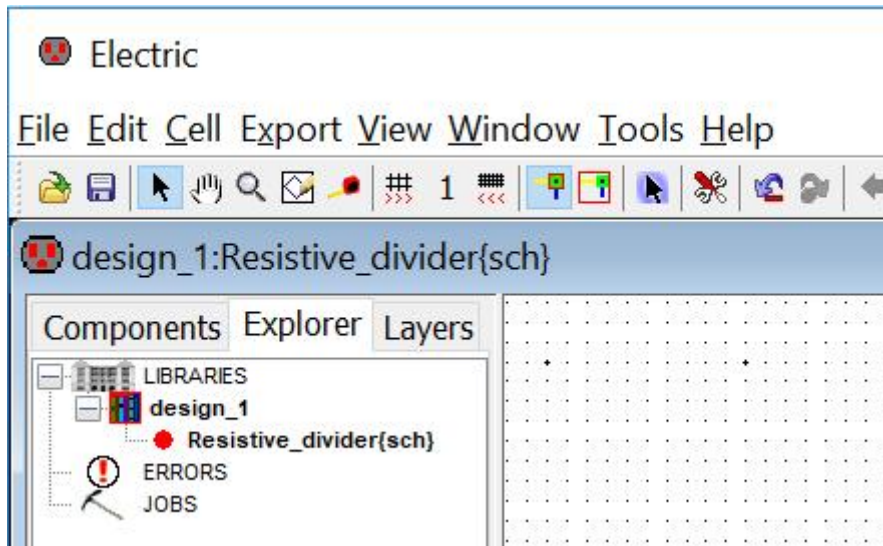Now under the **library design_1.jelib** you can find a **schematic cell** named as ----- {sch} with a **red indicator** as follows.



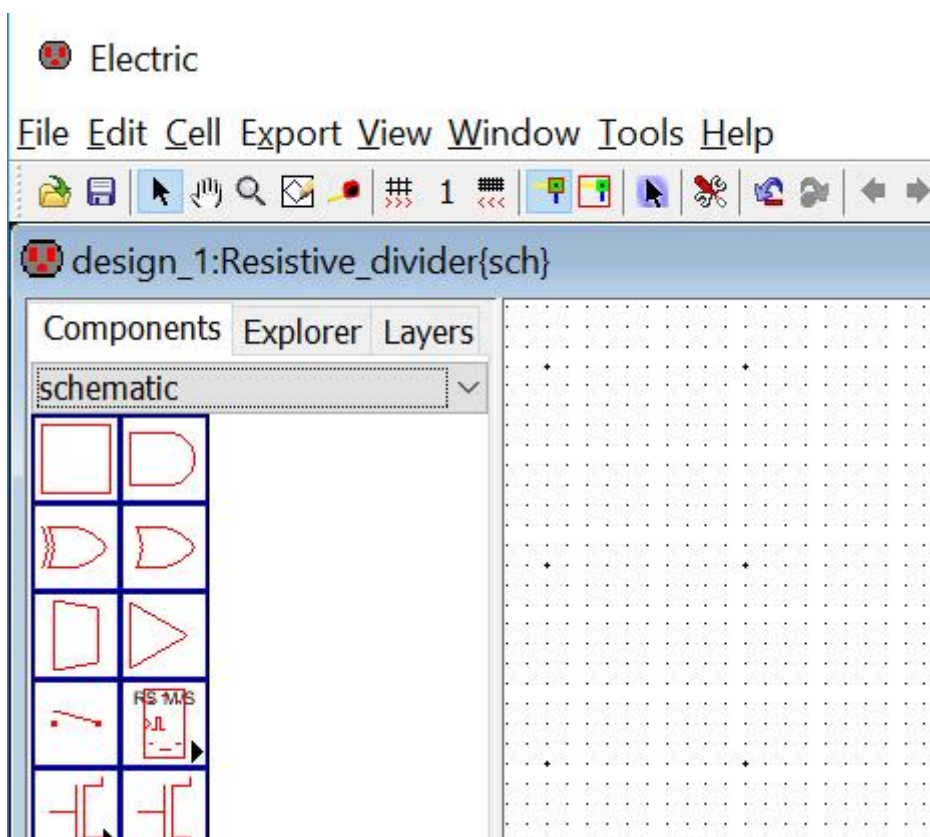
10. Now Press the **Components**. You will find the schematic components unlike the layout components in the startup window.



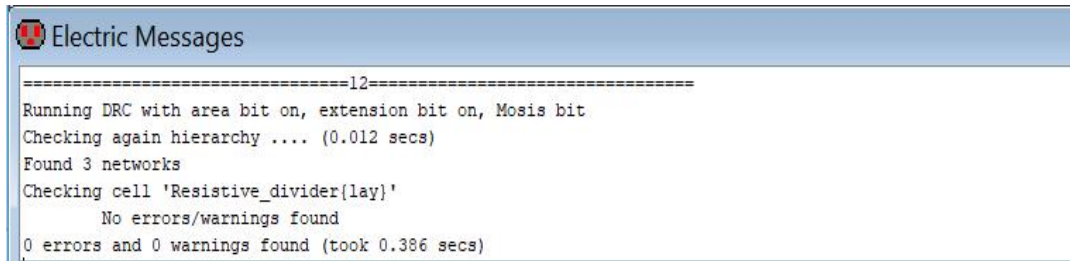11. Now we are finished with the setup and ready to fabricate a chip in the C5 process via MOSIS
12. Checking of DRC (Design Rule Check)

To check DRC you can execute **Tools -> DRC -> Check Hierarchically** or you can press **F5**.


Once DRC is checked, you can see result in the **message window** as follows:



```
=====12=====
Running DRC with area bit on, extension bit on, Mosis bit
Checking again hierarchy .... (0.012 secs)
Found 3 networks
Checking cell 'Resistive_divider{lay}'
    No errors/warnings found
0 errors and 0 warnings found (took 0.386 secs)
```

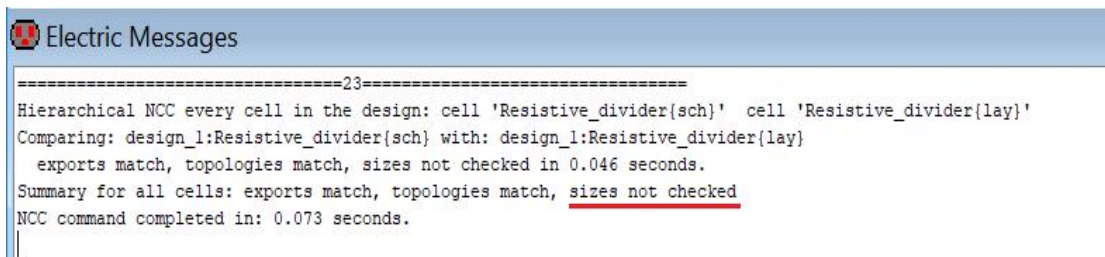13. Layout vs. Schematic (LVS) in Electric is checked using Network Consistency Checking (NCC)

To check this, execute **Tools -> NCC -> Schematic and Layout views of Cell in Current Window**. You can run this command being in any design window (schematic / layout).




```
=====23=====
Hierarchical NCC every cell in the design: cell 'Resistive_divider{sch}' cell 'Resistive_divider{lay}'
Comparing: design_1:Resistive_divider{sch} with: design_1:Resistive_divider{lay}
    exports match, topologies match, sizes not checked in 0.046 seconds.
Summary for all cells: exports match, topologies match, sizes not checked
NCC command completed in: 0.073 seconds.
```

We found a message like **sizes not checked**.

For this we have to take care of the following

Go to **File -> Preferences -> Categories -> Tools -> NCC -> Check transistor sizes**

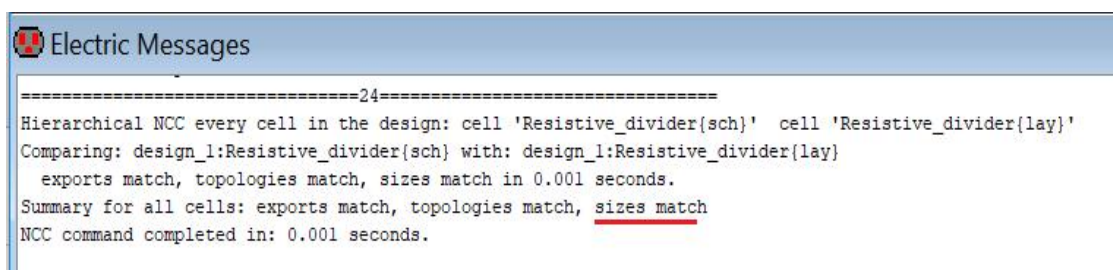Once again execute the NCC, now you will find the following message.



```
=====24=====
Hierarchical NCC every cell in the design: cell 'Resistive_divider{sch}' cell 'Resistive_divider{lay}'
Comparing: design_1:Resistive_divider{sch} with: design_1:Resistive_divider{lay}
    exports match, topologies match, sizes match in 0.001 seconds.
Summary for all cells: exports match, topologies match, sizes match
NCC command completed in: 0.001 seconds.
```

14. Checking ERC (Well Check)


This process checks the connection of the n-well and p-substrate.

The C5 process used here is an n-well process. The p-type substrate is common to all NMOS devices and should be grounded.

One of the **electrical rule checks** (ERCs) is to verify that the **p-well** (in this case p-substrate) is always connected to **ground**.

Further, in this n-well process, if the design contains only **digital circuits** then the **n-well** should be connected to V_{DD} .

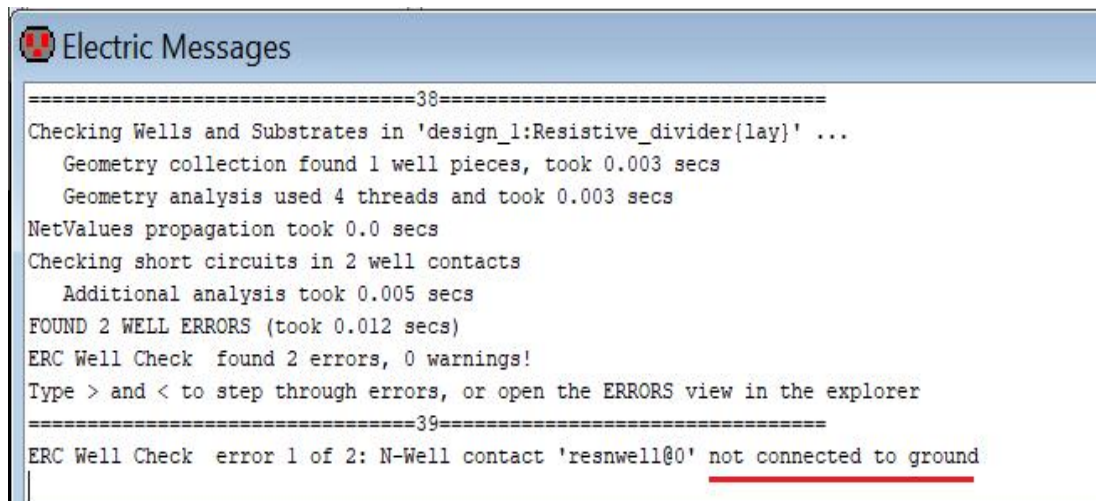For Well Check execute **Tools -> ERC -> Check Wells** or press **W** (as we have bounded this key to Well Check).



```
=====38=====
Checking Wells and Substrates in 'design_1:Resistive_divider{lay}' ...
  Geometry collection found 1 well pieces, took 0.003 secs
  Geometry analysis used 4 threads and took 0.003 secs
NetValues propagation took 0.0 secs
Checking short circuits in 2 well contacts
  Additional analysis took 0.005 secs
FOUND 2 WELL ERRORS (took 0.012 secs)
ERC Well Check found 2 errors, 0 warnings!
Type > and < to step through errors, or open the ERRORS view in the explorer
=====39=====
ERC Well Check error 1 of 2: N-Well contact 'resnwell@0' not connected to ground
```

The reason is as below:

In Digital Design all the N-Wells to be connected to V_{DD} and all the P-Wells to be connected to Ground.

Here we can see For N-Well, **Must connect to Power** is checked.

But this Resistive_divider is not a digital design. Here the N-Well is used as a resister which is an **analog design**.


So **uncheck** “Must connect to Power” under “For N-Well”. You will find zero Well Check error.

15. Schematic Simulation

Now we would **simulate** the resistive divider circuit which has been built, and would observe the output voltage w.r.t. a particular input voltage.

For this we need to write a **SPICE code** which would give the description of the input voltage and would indicate the type of simulation we want to perform.

Writing SPICE Code

 

Go to the **Components** menu. Click on the arrowhead in the **Misc** box to add **SPICE** code to the schematic as seen in the figure.

Place the SPICE code in the **schematic** and use Ctrl+I to edit its properties.

Ensure, in the SPICE code property box, that the **Multi-line Text** box is checked.


Add the code shown in the figure for specifying a **SPICE transient analysis** and an **input voltage source**. The code indicates an input voltage of 1 V DC is applied to the circuit. The analysis would be a transient one for 1 second.

Press F5 to check the schematic.

16. Simulation of the Schematic

Go to **Tools -> Simulation (Spice) -> Write Spice Deck**.

The following LTspice window will open.

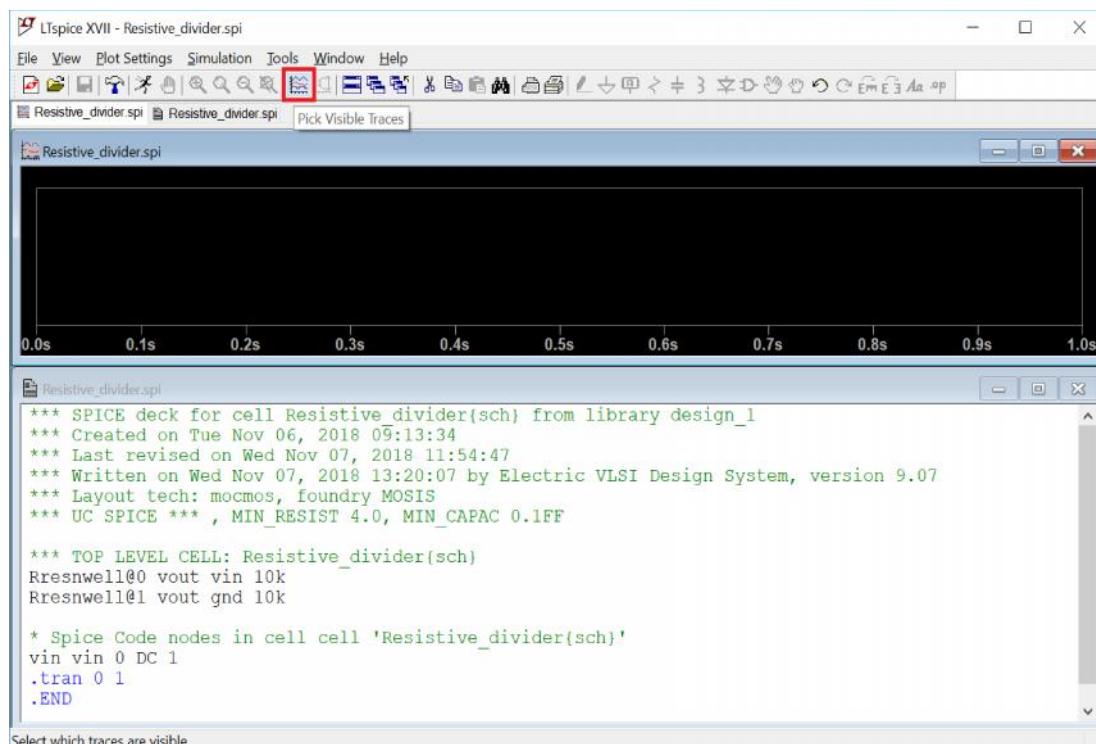



17. Resistive Divider Layout


Open the layout view of the Resistive_divider cell and then copy/paste (Ctrl+C/Ctrl+V) an **additional resistor**.

Running a **DRC** (pressing F5) on the above layout results in the following **error**.

By pressing > we see that there is **too little space between the N-wells**.

 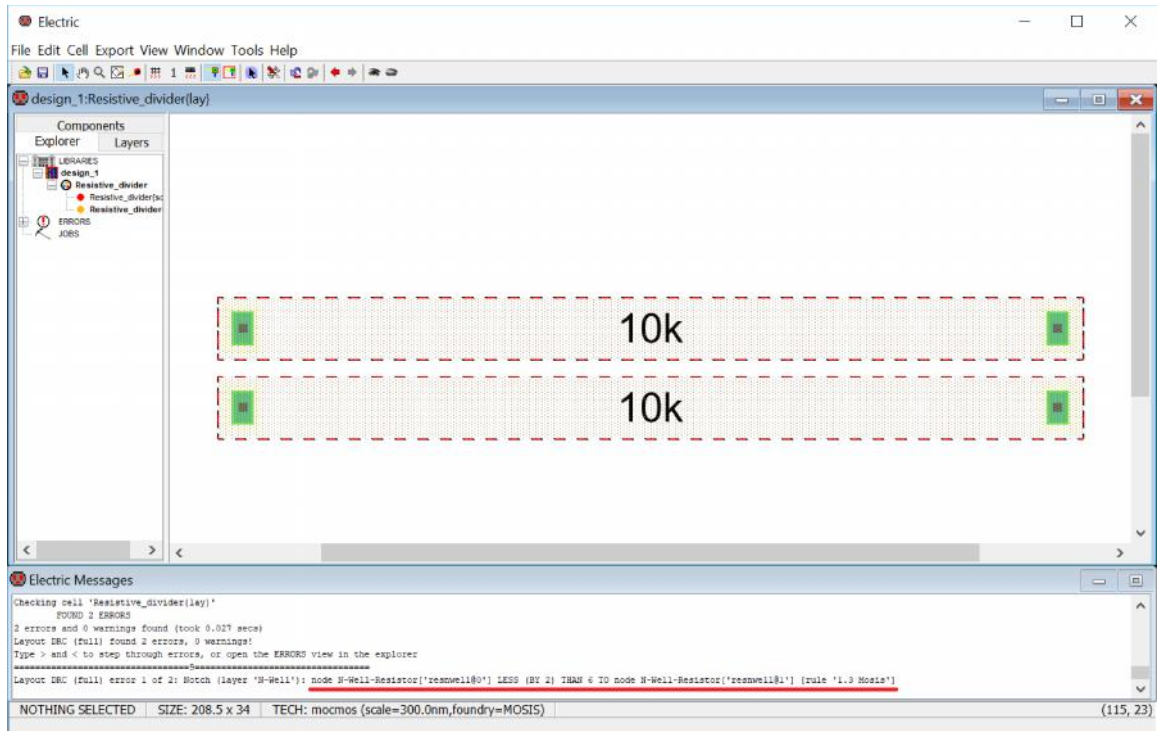Move the Nodes apart until the layout passes the DRCs. Of-course the error will not appear if you have initially placed both the resistors apart enough, which would **satisfy the MOSIS rule** for space between N-wells.



 


Run DRC to check the design is free of error or not.

This layout cell should match the schematic cell. Verify this by running the NCC (aka LVS check).

The following figure shows the Electric Messages for **DRC of layout** and **NCC of both layout and schematic (LVS)**.

 18. Layout Simulation

The following figure shows the visible spice code.




Run a DRC, NCC, and a Well Check to ensure that there aren't any errors.

This cell can be simulated following the same steps used for simulating the schematic view above.

Simulate this cell using LTspice now.

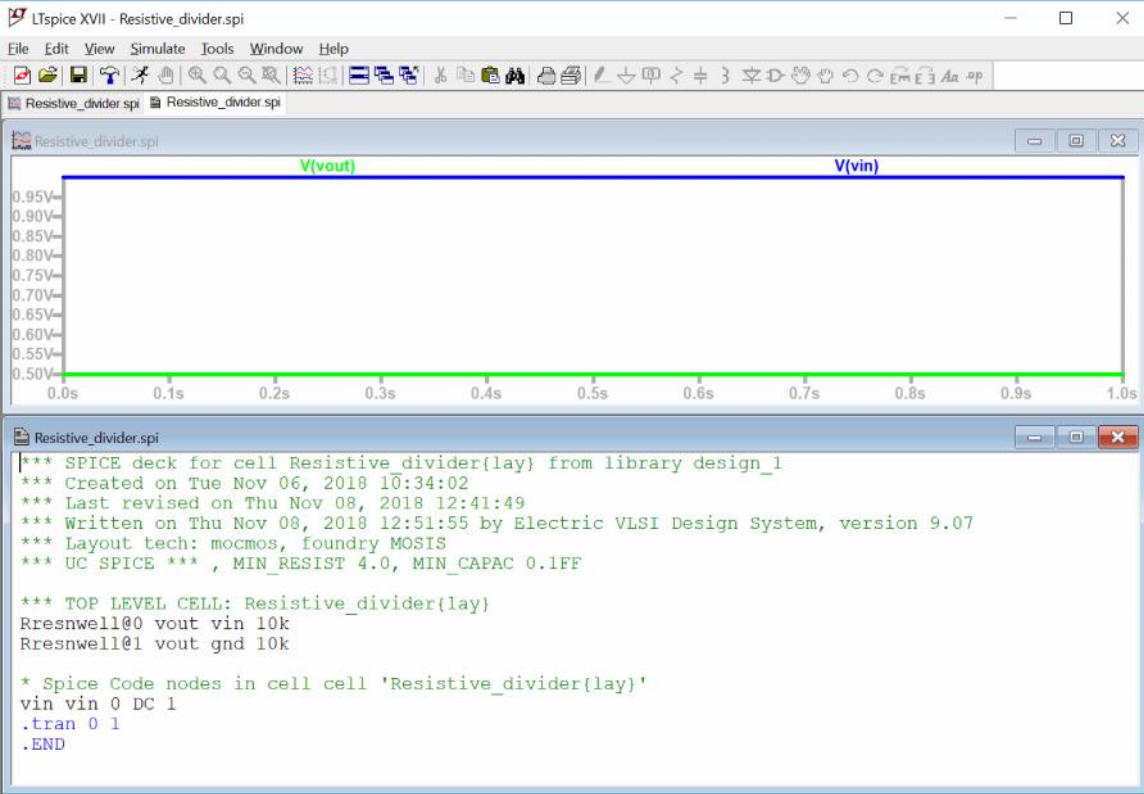The following figure shows the simulation output from LTspice for the Resistive_divider layout.



- * BSIM3 models for AMI Semiconductor's C5 process
- *
- * Don't forget the .options scale=300nm if using drawn lengths
- * and the MOSIS SUBM design rules
- *
- * $2 < L_{drawn} < 500$ $10 < W_{drawn} < 10000$ $V_{dd} = 5V$
- * Note minimum L is 0.6 um while minimum W is 3 um
- * Change to level=49 when using HSPICE or SmartSpice

```
.MODEL NMOS NMOS (          LEVEL = 8
+VERSION = 3.1      TNOM = 27      TOX = 1.39E-8
+XJ = 1.5E-7      NCH = 1.7E17      VTH0 = 0.6696061
+K1 = 0.8351612    K2 = -0.0839158  K3 = 23.1023856
+K3B = -7.6841108  W0 = 1E-8      NLX = 1E-9
+DVT0W = 0        DVT1W = 0        DVT2W = 0
+DVT0 = 2.9047241  DVT1 = 0.4302695  DVT2 = -0.134857
+U0 = 458.439679   UA = 1E-13      UB = 1.485499E-18
+UC = 1.629939E-11 VSAT = 1.643993E5  A0 = 0.6103537
+AGS = 0.1194608   B0 = 2.674756E-6  B1 = 5E-6
+KETA = -2.640681E-3  A1 = 8.219585E-5  A2 = 0.3564792
+RDSW = 1.387108E3  PRWG = 0.0299916  PRWB = 0.0363981
+WR = 1           WINT = 2.472348E-7  LINT = 3.597605E-8
+XL = 0          XW = 0           DWG = -1.287163E-8
+DWB = 5.306586E-8  VOFF = 0          NFACTOR = 0.8365585
+CIT = 0         CDSC = 2.4E-4      CDSCD = 0

+CDSCB = 0       ETA0 = 0.0246738  ETAB = -1.406123E-3
+DSUB = 0.2543458  PCLM = 2.5945188  PDIBLC1 = -0.4282336
+PDIBLC2 = 2.311743E-3  PDIBLCB = -0.0272914  DROUT = 0.7283566
+PSCBE1 = 5.598623E8  PSCBE2 = 5.461645E-5  PVAG = 0
+DELTA = 0.01      RSH = 81.8      MOBMOD = 1
+PRT = 8.621      UTE = -1       KT1 = -0.2501
+KT1L = -2.58E-9   KT2 = 0        UA1 = 5.4E-10
```

```

+UB1 = -4.8E-19 UC1 = -7.5E-11 AT = 1E5
+WL = 0 WLN = 1 WW = 0
+WVN = 1 WWL = 0 LL = 0
+LLN = 1 LW = 0 LWN = 1
+LWL = 0 CAPMOD = 2 XPART = 0.5
+CGDO = 2E-10 CGSO = 2E-10 CGBO = 1E-9
+CJ = 4.197772E-4 PB = 0.99 MJ = 0.4515044
+CJSW = 3.242724E-10 PBSW = 0.1 MJSW = 0.1153991
+CJSWG = 1.64E-10 PBSWG = 0.1 MJSWG = 0.1153991
+CF = 0 PVTH0 = 0.0585501 PRDSW = 133.285505
+PK2 = -0.0299638 WKETA = -0.0248758 LKETA = 1.173187E-3
+AF = 1 KF = 0)
*
.MODEL PMOS PMOS ( LEVEL = 8
+VERSION = 3.1 TNOM = 27 TOX = 1.39E-8
+XJ = 1.5E-7 NCH = 1.7E17 VTH0 = -0.9214347
K1 = 0.5553722 K2 = 8.763328E-3 K3 = 6.3063558
+K3B = -0.6487362 W0 = 1.280703E-8 NLX = 2.593997E-8
+DVT0W = 0 DVT1W = 0 DVT2W = 0
+DVT0 = 2.5131165 DVT1 = 0.5480536 DVT2 = -0.1186489

+U0 = 212.0166131 UA = 2.807115E-9 UB = 1E-21
+UC = -5.82128E-11 VSAT = 1.713601E5 A0 = 0.8430019
+AGS = 0.1328608 B0 = 7.117912E-7 B1 = 5E-6
KETA = -3.674859E-3 A1 = 4.77502E-5 A2 = 0.3
+RDSW = 2.837206E3 PRWG = -0.0363908 PRWB = -1.016722E-5
+WR = 1 WINT = 2.838038E-7 LINT = 5.528807E-8
+XL = 0 XW = 0 DWG = -1.606385E-8
+DWB = 2.266386E-8 VOFF = -0.0558512 NFACTOR = 0.9342488
+CIT = 0 CDSC = 2.4E-4 CDSCD = 0
+CDSCB = 0 ETA0 = 0.3251882 ETAB = -0.0580325
DSUB = 1 PCLM = 2.2409567 PDIBLC1 = 0.0411445
+PDIBLC2 = 3.355575E-3 PDIBLCB = -0.0551797 DROUT = 0.2036901

```

+PSCBE1 = 6.44809E9 PSCBE2 = 6.300848E-10 PVAG = 0
+DELTA = 0.01 RSH = 101.6 MOBMOD = 1
+PRT = 59.494 UTE = -1 KT1 = -0.2942
+KT1L = 1.68E-9 KT2 = 0 UA1 = 4.5E-9
+UB1 = -6.3E-18 UC1 = -1E-10 AT = 1E3
+WL = 0 WLN = 1 WW = 0
+WWN = 1 WWL = 0 LL = 0
+LLN = 1 LW = 0 LWN = 1
+LWL = 0 CAPMOD = 2 XPART = 0.5
+CGDO = 2.9E-10 CGSO = 2.9E-10 CGBO = 1E-9
+CJ = 7.235528E-4 PB = 0.9527355 MJ = 0.4955293
+CJSW = 2.692786E-10 PBSW = 0.99 MJSW = 0.2958392
+CJSWG = 6.4E-11 PBSWG = 0.99 MJSWG = 0.2958392
+CF = 0 PVTH0 = 5.98016E-3 PRDSW = 14.8598424
+PK2 = 3.73981E-3 WKETA = 5.292165E-3 LKETA = -4.205905E-3
AF = 1 KF = 0)

EXP NO: 7

Date:

Ring Oscillator

AIM:

To design, analyze and simulate the ring oscillator using LT-SPICE.

APPARATUS REQUIRED:


S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	LT-SPLICE	1

PROCEDURE:


1. Start "LTSpice XVII" (or earlier version)
2. Start a new Project under the File -> New Schematic
3. Make sure , files are saved in a convenient directory. The root directory (C:\) or Desktop are probably not good choices. I would suggest creating a directory "C:\Circuits" and saving your work there
4. Double click on LTspice XVII item → Select the file menu → double click save button
5. Click on component button → click type nmos → click on nmos4 item → select ok → click left in screen → press cntl+E for required number of nmos
6. Follow step 5 for selecting pmos4 device.
7. Click on wire button and give connection in circuit diagram
8. Click the ground button and place in screen and give connection using wire.
9. Click voltage in component list and place in screen. Give connection using wire.
10. Click on spice directive button and type ".include level 3 and 54.txt" then click ok
11. Click File menu → select save as and select desktop item outline item and select the file name and type the name of file then give ok.
12. Click on run button.
13. Obtain the Transient analysis of Ring oscillator

Circuit Diagram:


3 stage ring oscillator

 


3 stage ring oscillator using CMOS

 

SCHEMATIC:

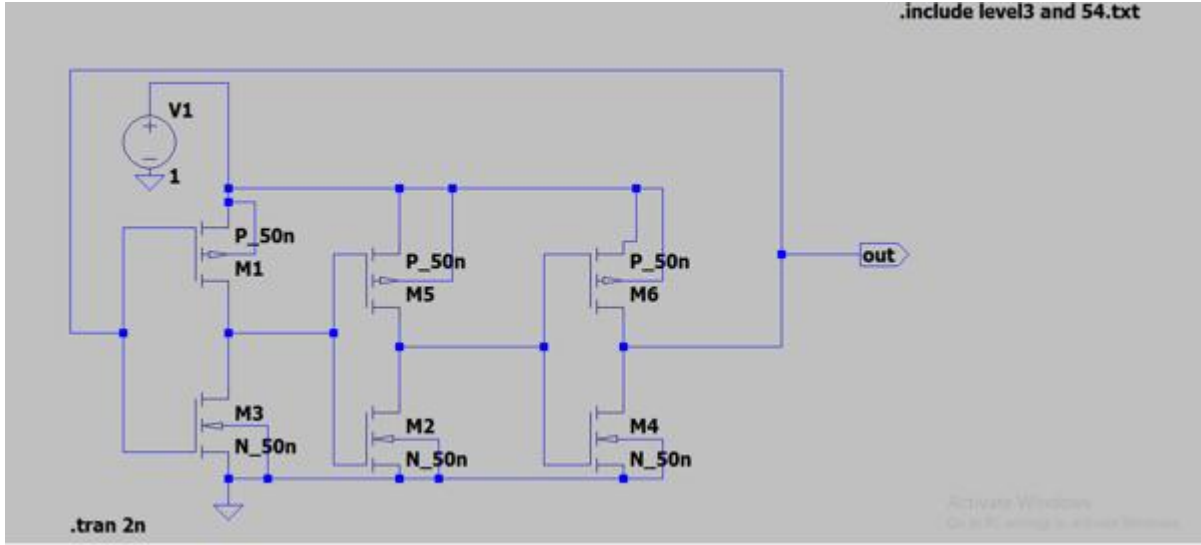

SIMULATION OUTPUT:

 

Calculation:

The frequency of oscillation formula for ring oscillator is

$$f = \frac{1}{2nT}$$

Here T = time delay for single inverter

n = number of inverters in the oscillator

RESULT:

Thus the Ring oscillator is simulated using LT-SPICE.

EXP NO: 8

Date:

Differential Amplifier

AIM:

To design, analyze and simulate the Differential Amplifier using LT-SPICE.

APPARATUS REQUIRED:


S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	LT-SPLICE	1

PROCEDURE:


1. Start "LTSpice XVII" (or earlier version)
2. Start a new Project under the File -> New Schematic
3. Make sure , files are saved in a convenient directory. The root directory (C:\) or Desktop are probably not good choices. I would suggest creating a directory "C:\Circuits" and saving your work there
4. Double click on LTspice XVII item → Select the file menu → double click save button
5. Click on component button → click type nmos → click on nmos4 item → select ok → click left in screen → press cntl+E for required number of nmos
6. Follow step 5 for selecting pmos4 device.
7. Connect the Circuit as schematic.
8. Click on spice directive button and type ".include BISM4_models.txt" then click ok
9. Click File menu → select save as and select desktop item outline item and select the file name and type the name of file then give ok.
10. .To Obtain the AC analysis, Click on spice directive button and type ".ac oct 20 7 150" then click ok
11. To Obtain the DC analysis, Click on spice directive button and type ".dc V1 -5 5 1m" then click ok
12. To Obtain the Transient analysis,Click on spice directive button and type ".tran 4m" then click ok

SCHEMATIC:


Symbol:

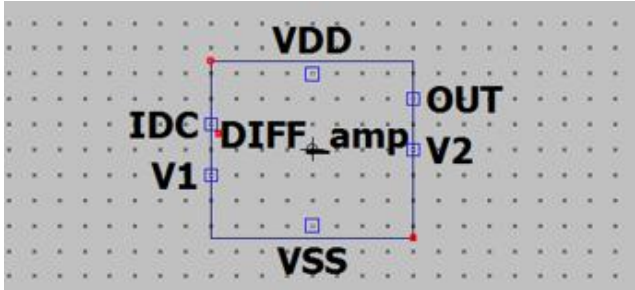


Circuit:

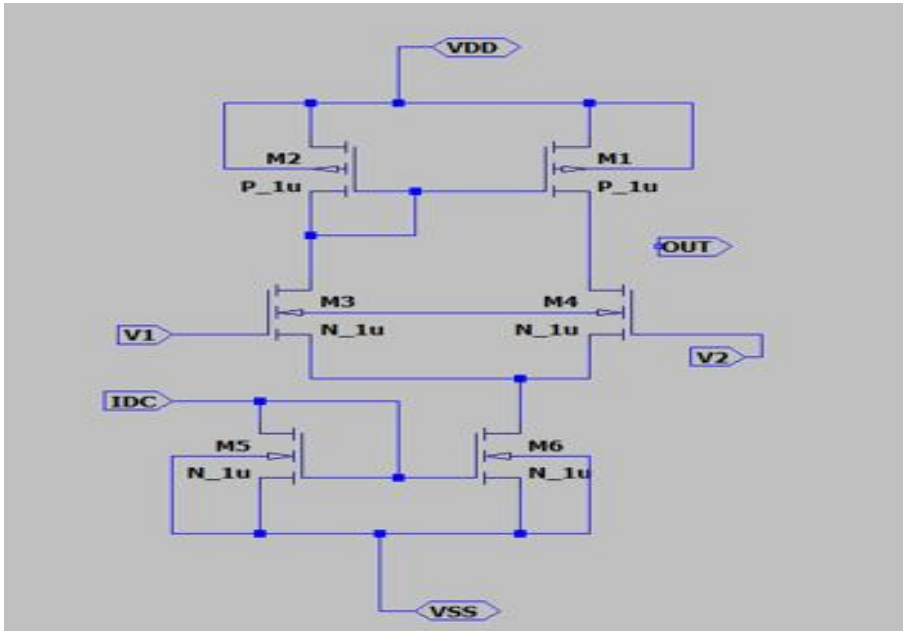


AC ANALYSIS:

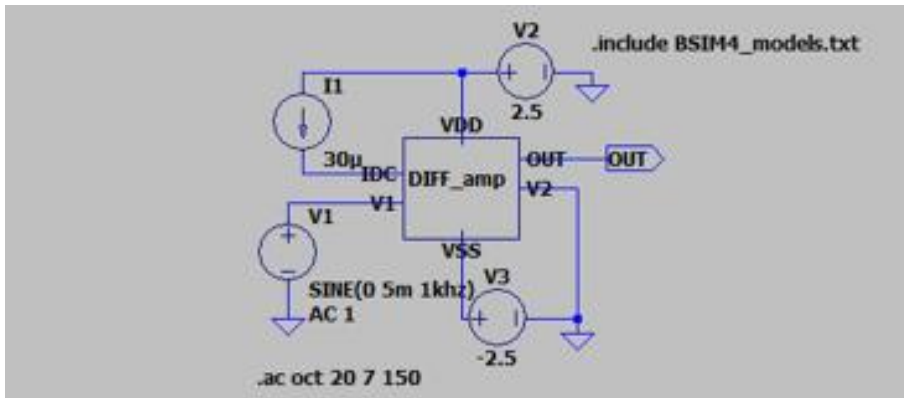


SIMULATION OUTPUT:

 


DC ANALYSIS

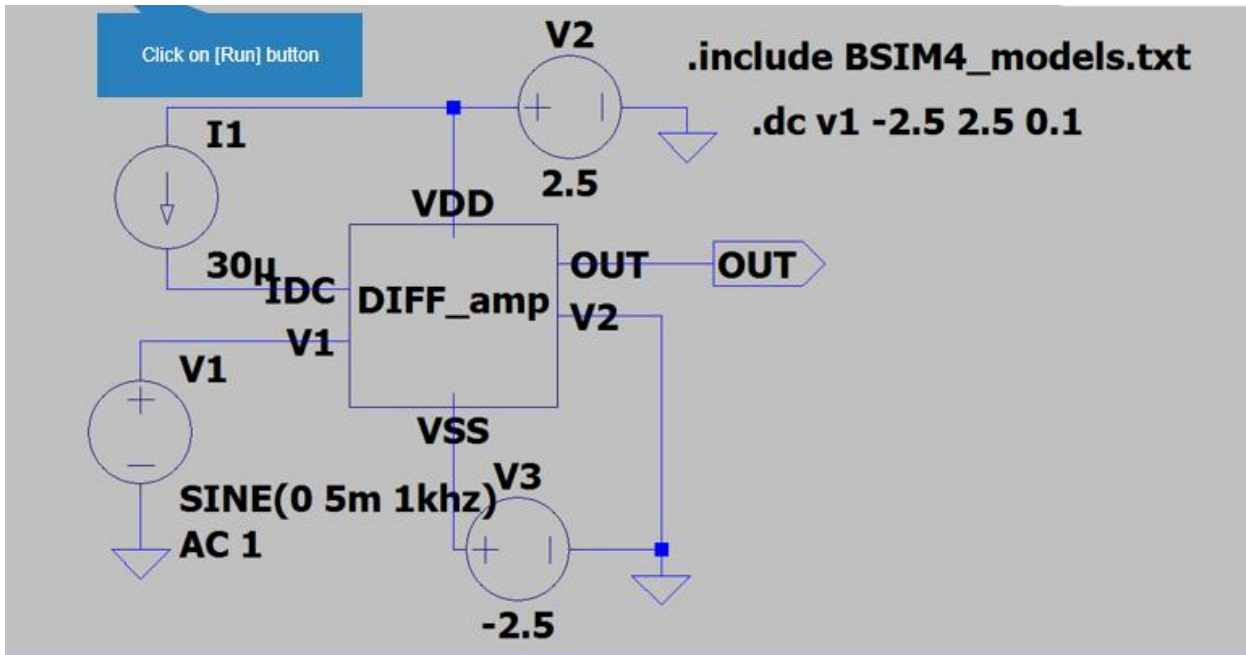


SIMULATION OUTPUT:

 



Transient Analysis:

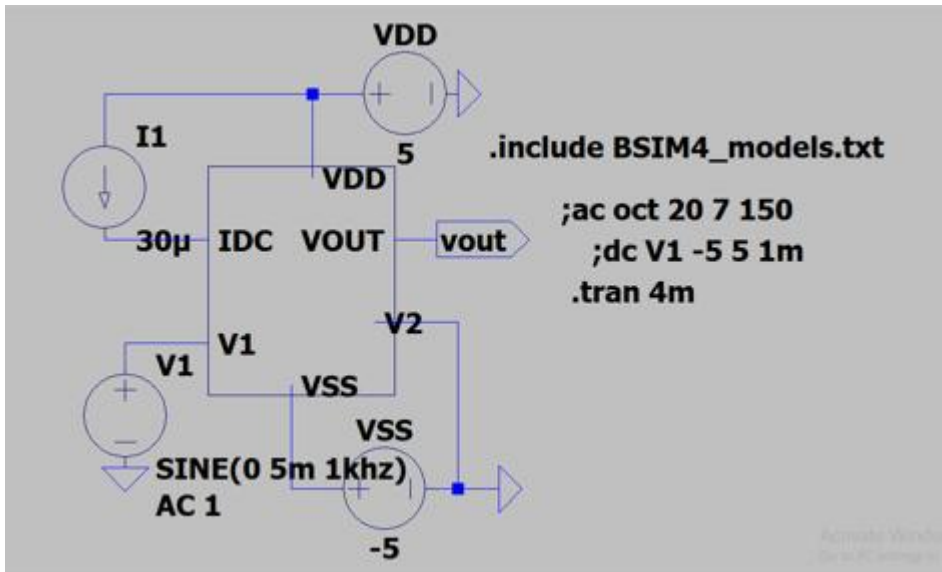



SIMULATION OUTPUT:

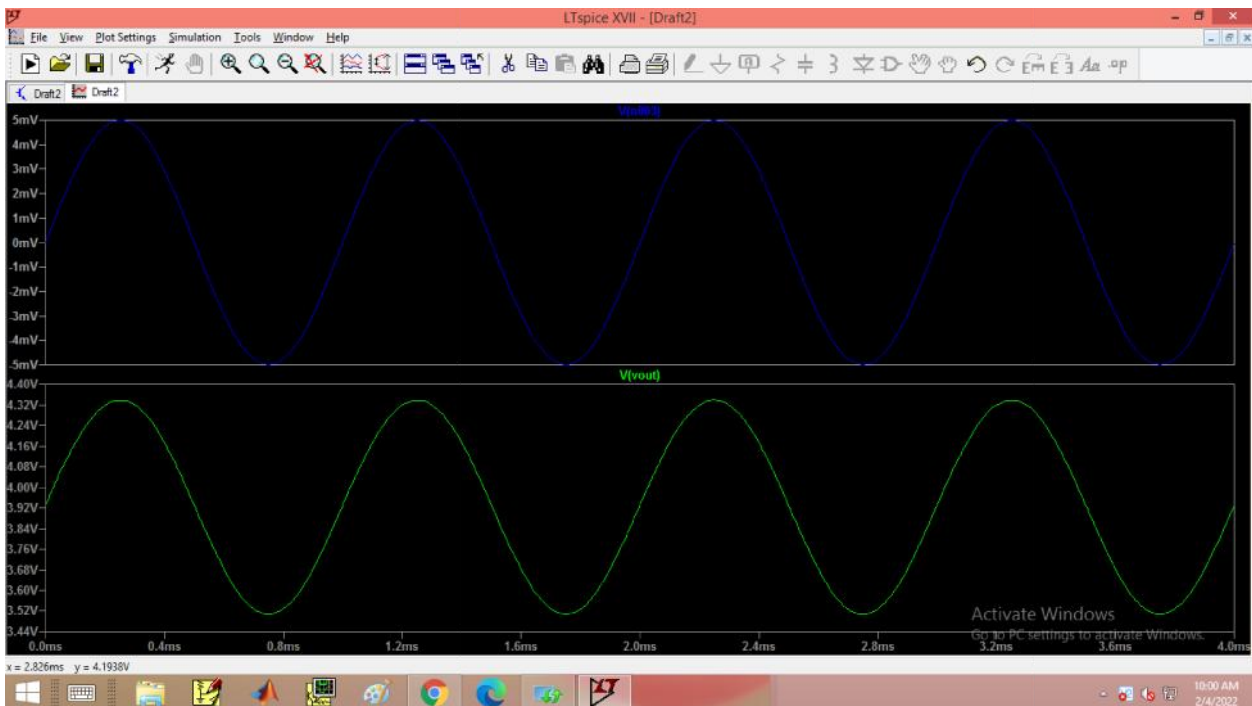

Differential Mode Gain:

 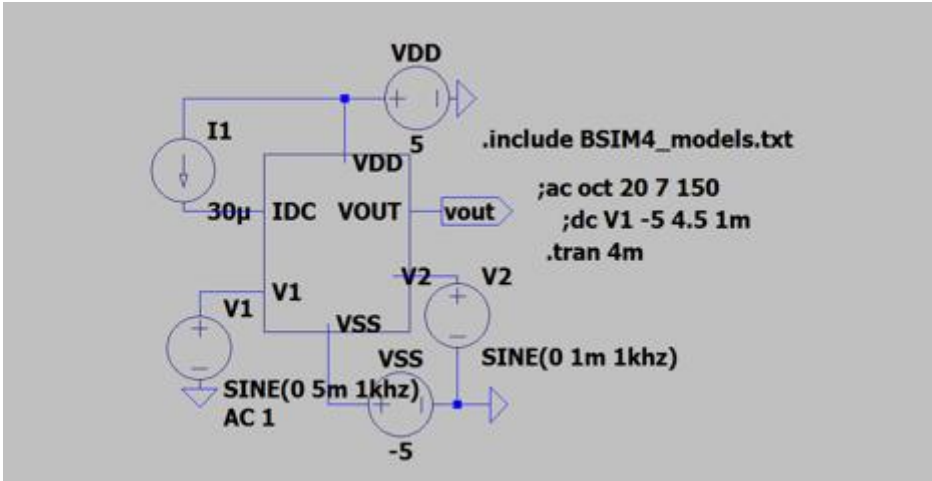

Common Mode Gain:

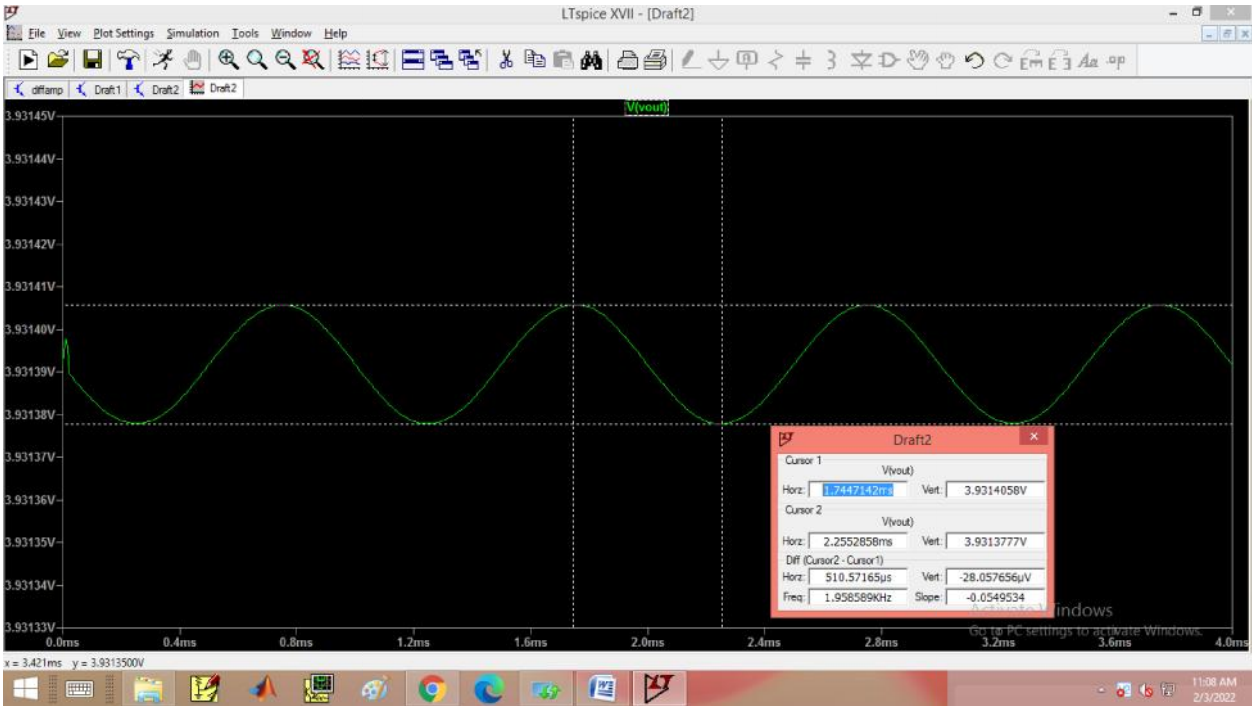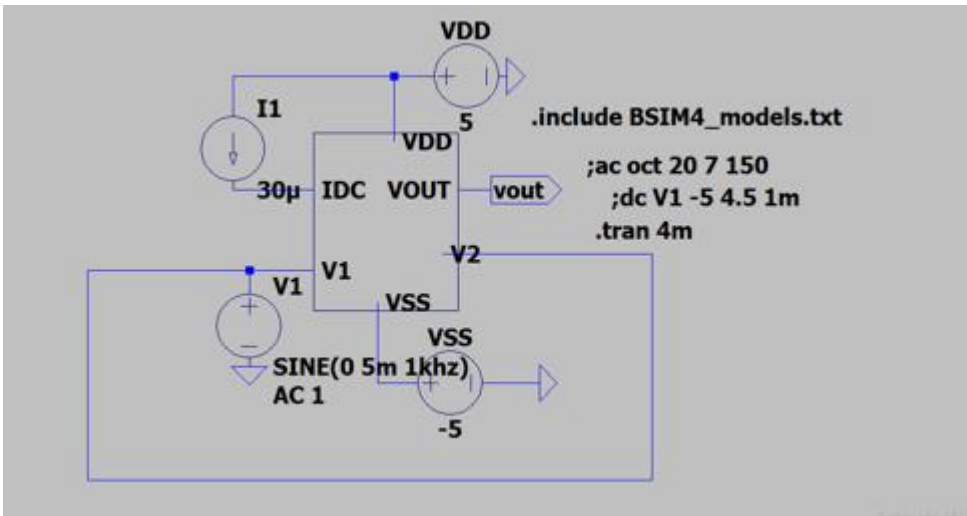

Calculation:

$$C = \frac{A_D}{A_C}$$

$$C_{in} = 20 \mu \frac{A_D}{A_C}$$

$$A_D = D \quad V \quad G$$

$$A_D = \frac{V_o}{V_1 - V_2}$$

V1= 5mv V2= 1mv Vout =

$$A_C = C \mu \quad m \quad V \quad G$$

$$A_C = \frac{V_o}{(V_1 + V_2)/2}$$

V1= 5mv V2= 5mv Vout =

RESULT:

Thus the Differential Amplifier is simulated and CMRR is determined using LT-SPICE.

EXP NO: 9

Date:

CMOS Inverter

AIM:

To design a CMOS inverter using the Schematic entry tool - Electric and verify its functioning.

APPARATUS REQUIRED:



S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	ELECTRIC-EDA Tool	1

PROCEDURE:


1. Start Electric VLSI system Design tool.
2. Start a new Project under the File -> New Schematic
3. Make sure, files are saved in a convenient directory. Save as filename.jelib under LIBRARIES name in Explorer
4. Go to Preferences by clicking the following button or executing File -> Preferences Then set the following.
 - a. Preferences -> Categories -> Technology -> Technology
5. Go to cell -> New Cell → Schematic
6. Go to **Components**. The schematic components will appear unlike the layout components in the startup window.
7. Connect the Circuit as shown in Figure
8. To check DRC ,execute Tools -> DRC -> Check Hierarchically
9. To check NCC, execute Tools -> NCC -> Schematic and Layout views of Cell in Current Window.
10. **For Well Check** execute Tools -> ERC -> Check Wells
11. Go to the **Components menu**. Click on the arrowhead in the **Misc box** to add **SPICE code** to the schematic . Place the SPICE code in the **schematic**
12. Go to Tools -> Simulation (Spice) -> Write Spice Deck.
13. Obtain the output waveform of CMOS Inverter.

SCHEMATIC

Symbol:

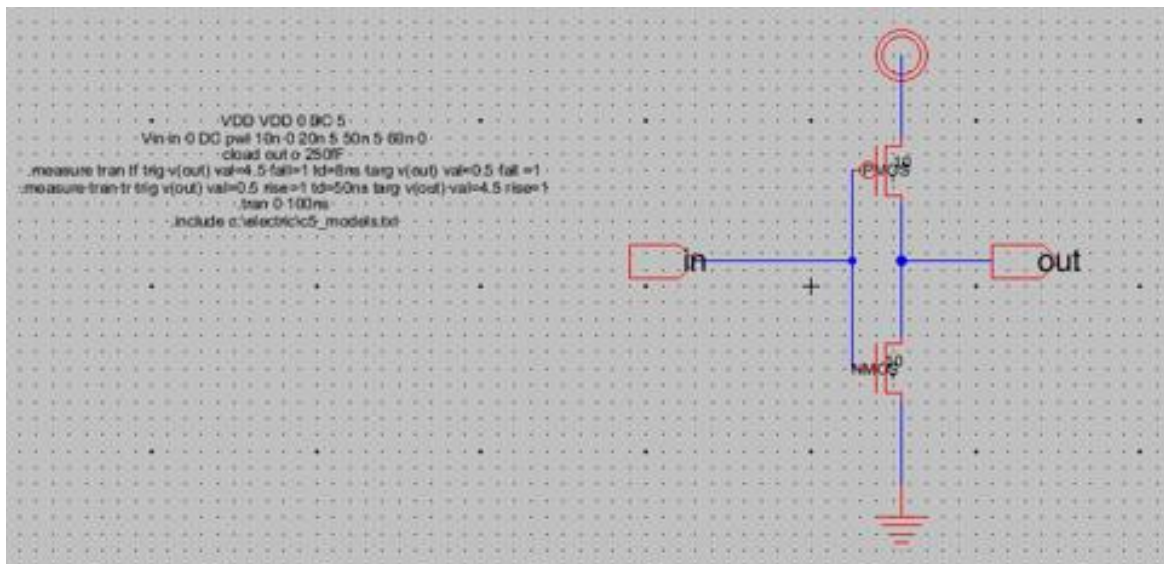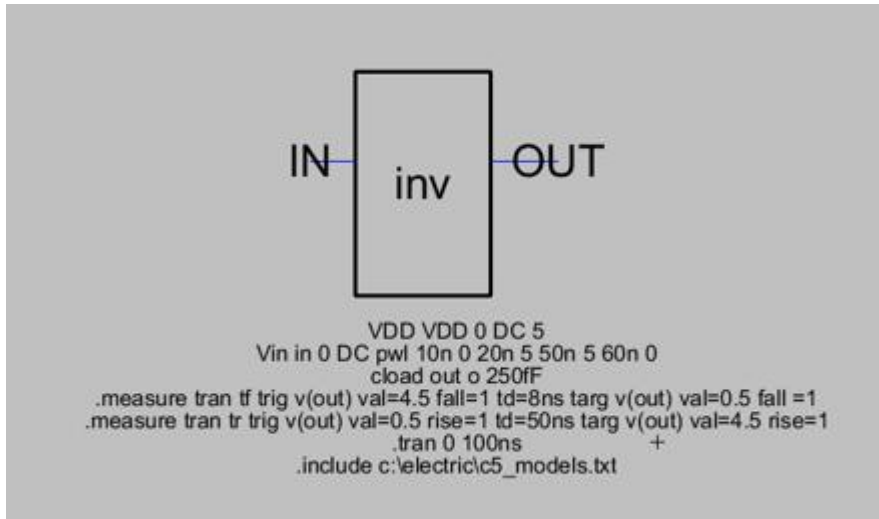

SIMULATION OUTPUT:

 

RESULT

Thus the design & simulation of a CMOS inverter has been carried out using schematic of Electric EDA Tools.

EXP NO: 10
Date:

Layout CMOS Inverter

AIM:

To draw the layout of CMOS Inverter using Electric EDA tool and extract the SPICE code.


APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	ELECTRIC-EDA Tool	1


PROCEDURE:

1. Start Electric VLSI system Design tool.
2. Start a new Project under the File -> New Schematic
3. Make sure, files are saved in a convenient directory. Save as filename.jelib under LIBRARIES name in Explorer
4. Go to Preferences by clicking the following button or executing File -> Preferences Then set the following.
 - a. Preferences -> Categories -> Technology -> Technology
5. Go to cell -> New Cell -> Schematic
6. Go to **Layers**. The Layer components will appear unlike the schematic components in the components window.
7. Connect the Layout as shown in Figure
8. To check DRC ,execute Tools -> DRC -> Check Hierarchically
9. To check NCC, execute Tools -> NCC -> Schematic and Layout views of Cell in Current Window.
10. **For Well Check** execute Tools -> ERC -> Check Wells
11. Go to the **Components menu**. Click on the arrowhead in the **Misc box** to add **SPICE code** to the schematic . Place the SPICE code in the **layout**
12. Go to Tools -> Simulation (Spice) -> Write Spice Deck.
13. Obtain the output waveform of CMOS Inverter.

LAYOUT:

 

3D VIEW:

 

SPICE Code:


```
*** SUBCIRCUIT inverter1__inv FROM CELL inverter1:inv(lay)
.SUBCKT inverter1__inv gnd IN out vdd
Mnm0s@0 gnd IN out gnd NMOS L=0.4U W=2U AS=3.2P AD=8.2P PS=7.2U PD=19.2U
Mpm0s@0 vdd IN out vdd PMOS L=0.4U W=2U AS=3.2P AD=8.84P PS=7.2U PD=19.6U

* Spice Code nodes in cell cell 'inverter1:inv(lay)'
vdd vdd 0 DC 5
vin in 0 DC pwl 10n 0 20n 5 50n 5 60n 0
cload out 0 250fF
.measure tran tf trig v(out) val=4.5 fall=1 td=8ns targ v(out) val=0.5 fall=1
.measure tran tf trig v(out) val=0.5 rise=1 td=50ns targ v(out) val=4.5 fall=1
.tran 0 100ns
.include c:\electric\c5_models.txt
.ENDS inverter1__inv

*** TOP LEVEL CELL: inv_sym(lay)
Xinv@0 gnd IN OUT vdd inverter1__inv

* Spice Code nodes in cell cell 'inv_sym(lay)'
vdd vdd 0 DC 5
vin in 0 DC pwl 10n 0 20n 5 50n 5 60n 0
cload out 0 250fF
.measure tran tf trig v(out) val=4.5 fall=1 td=8ns targ v(out) val=0.5 fall=1
.measure tran tf trig v(out) val=0.5 rise=1 td=50ns targ v(out) val=4.5 fall=1
.tran 0 100ns
.include c:\electric\c5_models.txt
.END
```

SIMULATION OUTPUT:

 

RESULT:

Thus the layout of CMOS Inverter was verified through Electric EDA tool

EXP NO: 11
Date:

CMOS Inverter – Place and Route

AIM:

To design placement and routing, and post placement and routing parameters and observe logical effort for CMOS Inverter using Electric EDA tools.


APPARATUS REQUIRED:

S.No	Name of the equipment/ software	Quantity
1.	PC with Windows	1
2.	ELECTRIC-EDA Tool	1


PROCEDURE:

1. Start Electric VLSI system Design tool.
2. Start a new Project under the File -> New Schematic
3. Make sure, files are saved in a convenient directory. Save as filename.jelib under LIBRARIES name in Explorer
4. Go to Preferences by clicking the following button or executing File -> Preferences Then set the following.
 - a. Preferences -> Categories -> Technology -> Technology
5. Go to cell -> New Cell -> Schematic
6. Go to **Components**. The schematic components will appear unlike the layout components in the startup window.
7. Connect the Circuit as shown in Figure
8. To check DRC ,execute Tools -> DRC -> Check Hierarchically
9. To check NCC, execute Tools -> NCC -> Schematic and Layout views of Cell in Current Window.
10. **For Well Check** execute Tools -> ERC -> Check Wells
11. Go to the **Components menu**. Click on the arrowhead in the **Misc box** to add **SPICE code** to the schematic . Place the SPICE code in the **schematic**
12. Go to Tools -> Simulation (Spice) -> Write Spice Deck.
13. Go to Tools -> Placement -> FloorPlanning to obtain place and route of Inverter
14. Go to Tools -> Logic effort -> Logic Effort libraries to obtain logic effort of Inverter.

Floor Planning:

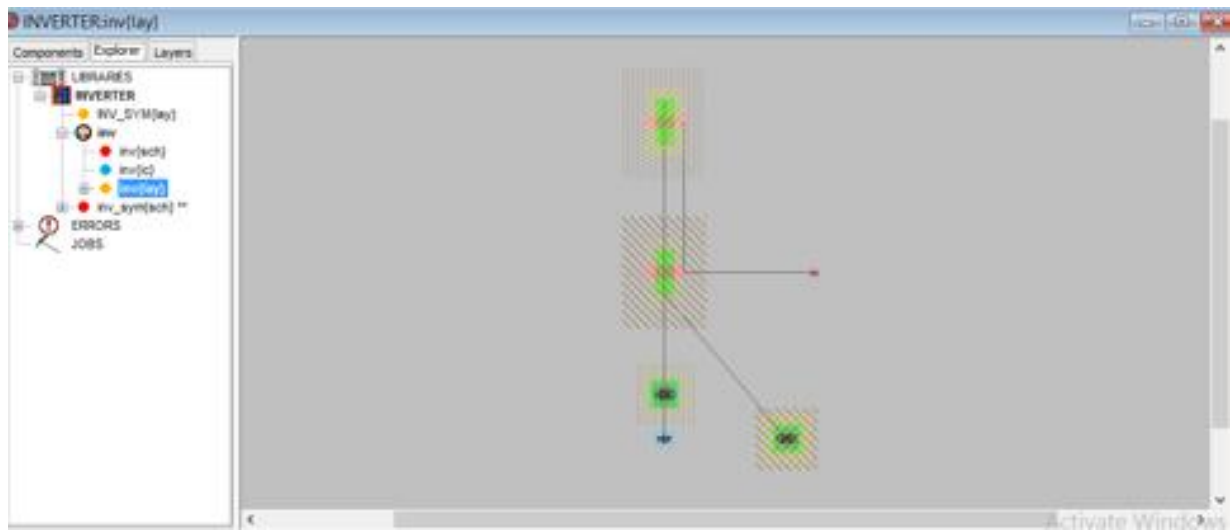

Place and Route:

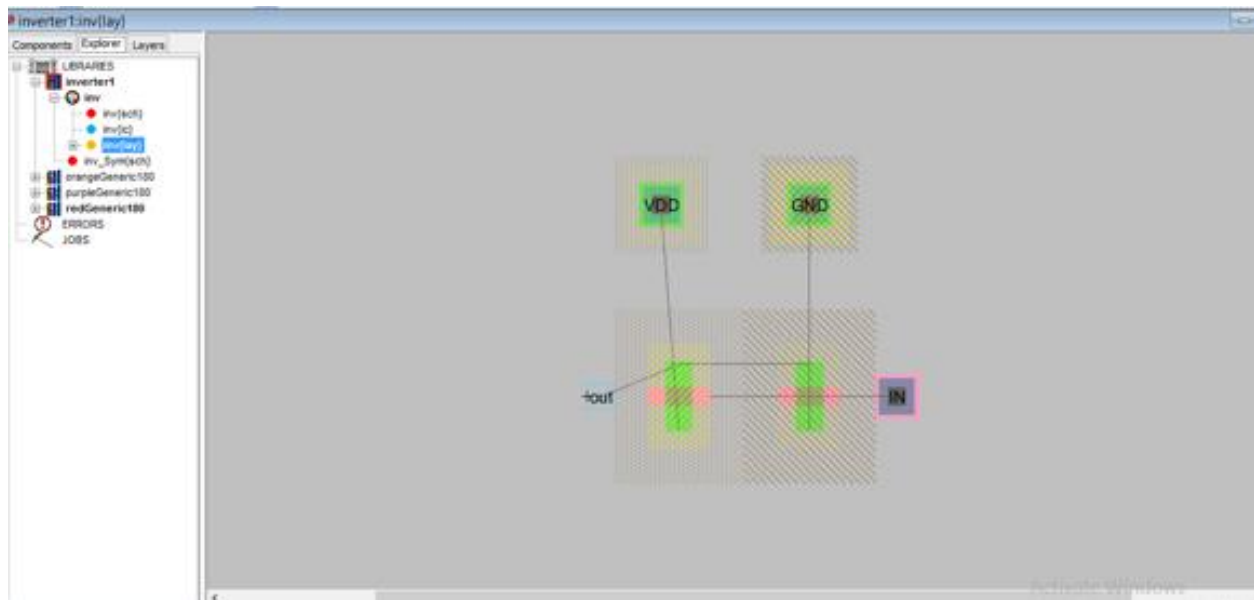


Report:


```
File Edit Cell Export View Window Tools Help
Electric Messages
Electric's log file is C:\Users\ECE_CASDI\Desktop\electric.log.
-----
Library /C:/Users/ECE_CASDI/Documents/inverter1.yellib read, took 0.018 secs
Checking library 'inverter1' for repair... library checked
No errors found
-----
Delay estimation for each network is a ratio of the following:
Numerator is the sum of these layers on the network:
  Transistor widths
  Diffusion half-perimeter, weighted by 0.7
  Poly silicon half-perimeter, weighted by 0.25
  Metal half-perimeter, weighted by 0.25
Denominator is the width of transistors on the network
Separate results are computed for N and P transistors, as well as their sum
-----
Network 'in' ratio computation:
N Gate width = 10.0, P Gate width = 10.0
Layer 1to half-perimeter is 0 x 0.25 = 0
Numerator is the sum of these factors (20)
N denominator = 10.0, ratio = 2
P denominator = 10.0, ratio = 2
N+P Denominator = 20.0, ratio = 1
```

Activate Windows

RC MODEL:

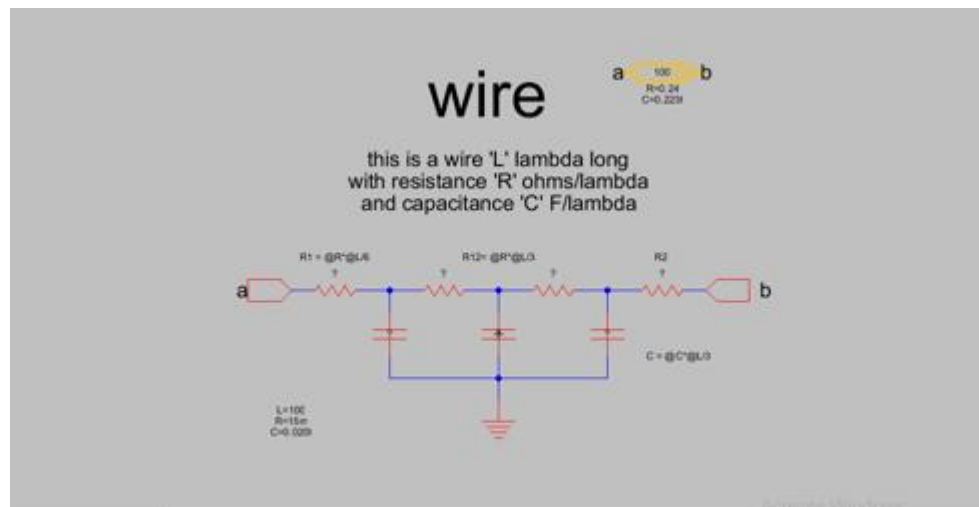

LOGIC EFFORT:

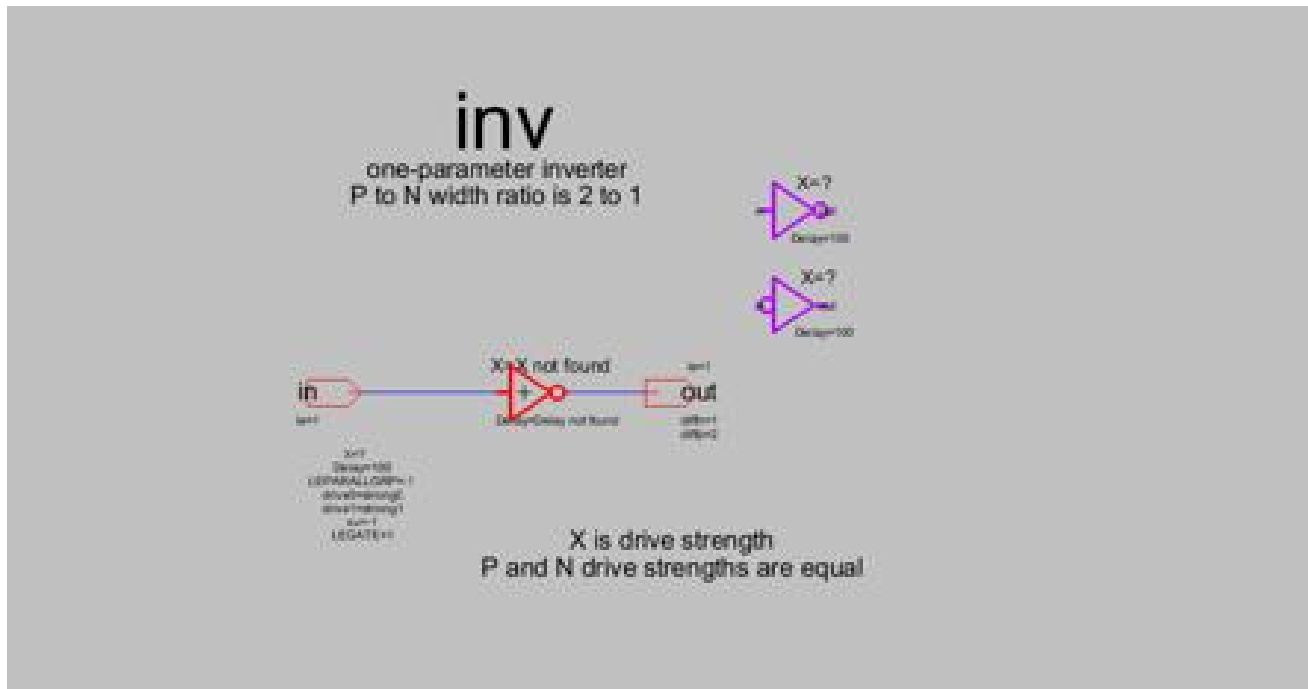

RESULT:

Thus the post placement and routing parameters and logical effort of CMOS Inverter are observed using Electric EDA tools.

EXP NO: 12
Date:

Layout CMOS NAND Gate

AIM:

To draw the layout of CMOS NAND using Electric EDA tool and extract the SPICE code.


APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	ELECTRIC-EDA Tool	1


PROCEDURE:

1. Start Electric VLSI system Design tool.
2. Start a new Project under the File -> New Schematic
3. Make sure, files are saved in a convenient directory. Save as filename.jelib under LIBRARIES name in Explorer
4. Go to Preferences by clicking the following button or executing File -> Preferences Then set the following.
 - a. Preferences -> Categories -> Technology -> Technology
5. Go to cell -> New Cell -> Schematic
6. Go to **Layers**. The Layer components will appear unlike the schematic components in the components window.
7. Connect the Layout as shown in Figure
8. To check DRC ,execute Tools -> DRC -> Check Hierarchically
9. To check NCC, execute Tools -> NCC -> Schematic and Layout views of Cell in Current Window.
10. **For Well Check** execute Tools -> ERC -> Check Wells
11. Go to the **Components menu**. Click on the arrowhead in the **Misc box** to add **SPICE code** to the schematic . Place the SPICE code in the **layout**
12. Go to Tools -> Simulation (Spice) -> Write Spice Deck.
13. Obtain the output waveform of CMOS NAND.


SCHEMATIC:

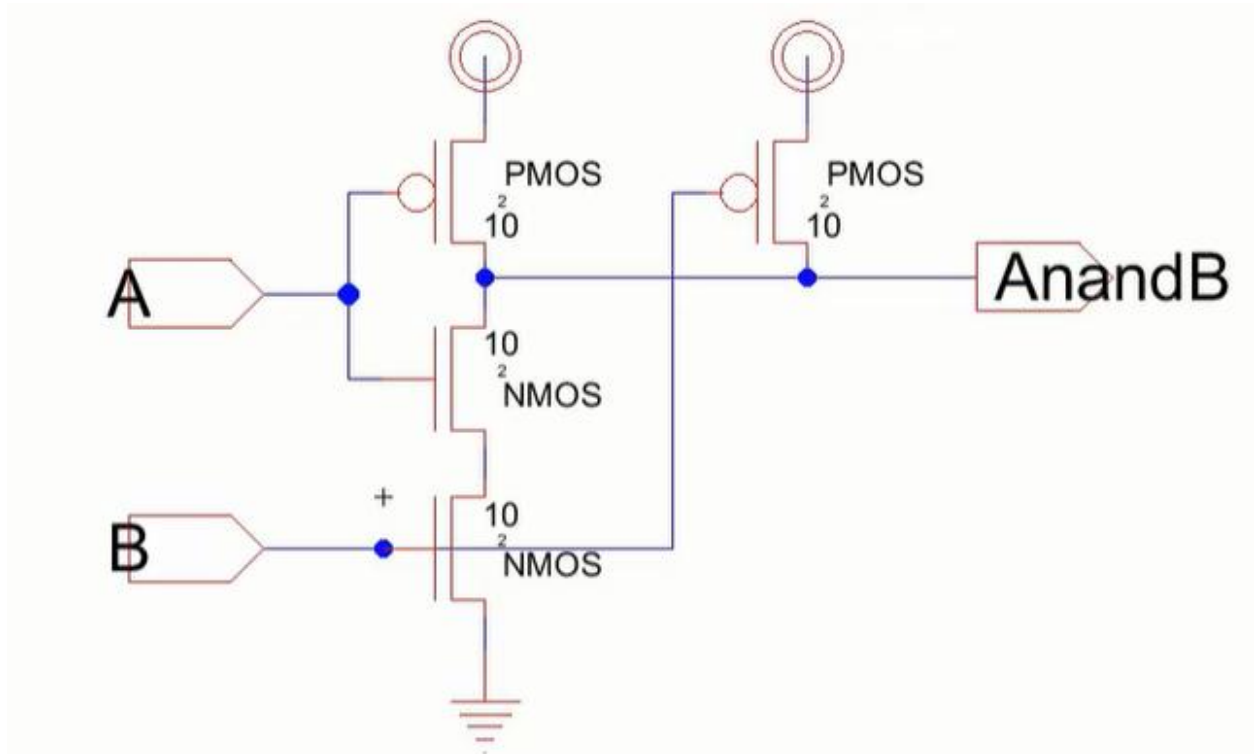


SYMBOL:

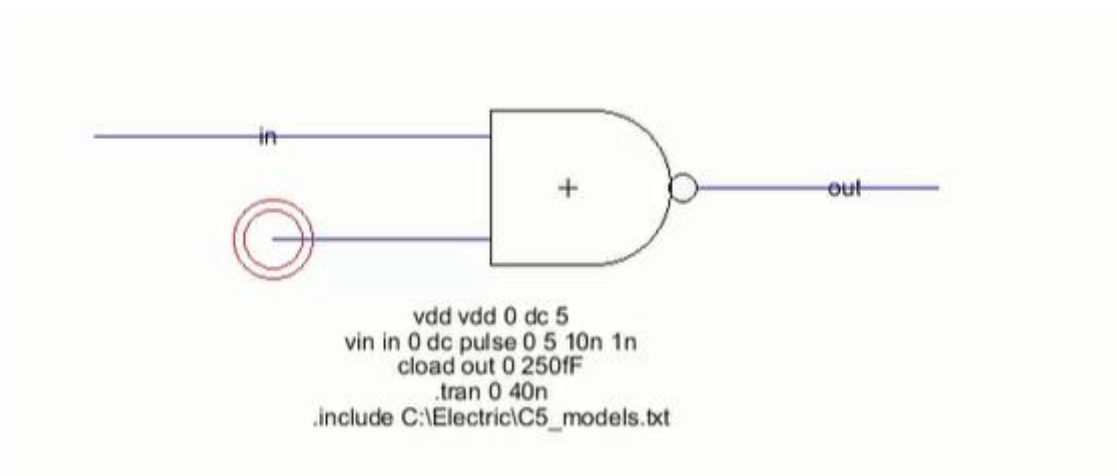


LAYOUT:

 

3D VIEW:

 

Simulation Output:

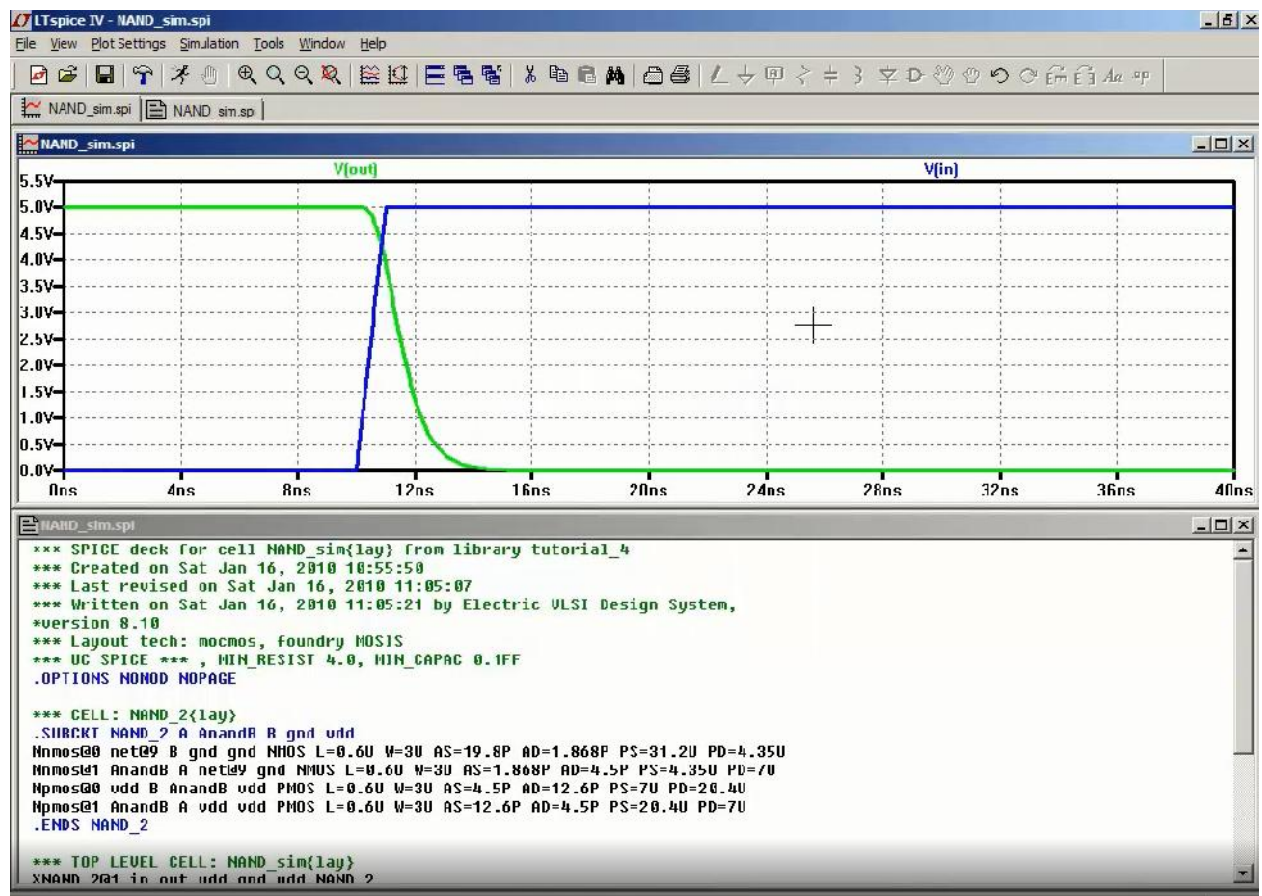

RESULT:

Thus the layout of CMOS NAND was verified through Electric EDA tool

EXP NO: 13

Date:

Static Timing Analysis

AIM:

To study the given circuit and perform static timing analysis using Synopsys - PrimeTime STA tools.

APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	Synopsys - PrimeTime STA tool	1

PROCEDURE:

Invoke PrimeTime STA tool

To invoke PrimeTime, choose either options

pt_shell (command mode)

primetime &(GUI mode)

Command mode is preferred because:

- The command mode helps you to keep a record of what you have done.
- The command mode runs more efficiently than GUI mode.
- The command mode helps you to lookup the manual/reference quickly.

In spite of the above advantages, command mode sometimes is not as good as GUI mode in terms of debugging the schematic problem.

Start Operating PrimeTime STA tool

STA Environment Setting for TSMC 0.13um Technology:

1. Set search path (*If it has not been set up yet*)

```
set search_path "/home/raid2_2/course/cvsd/CBDK_IC_Contest/CIC/SynopsysDC/db"
```

2. Set link library

```
set link_path "* typical.db fast.db slow.db"
```

```
~/Desktop/synopsys_example/DesignCompiler/dc
~/Desktop/synopsys_example/DesignCompiler/dc$ pt_shell
hell

PrimeTime (R)
Version J-2014.12-SP2 for RHEL64 -- Feb 26, 2015
Copyright (c) 1988-2015 Synopsys, Inc.
ALL RIGHTS RESERVED

This program is proprietary and confidential information of Synopsys, Inc.
and may be used and disclosed only as authorized in a license agreement
controlling such use and disclosure.

pt_shell> set link
link_allow_design_mismatch link_library
link_create_black_boxes link_path
link_force_case link_path_per_instance
pt_shell> set link_library {* re
ref/ results/
pt_shell> set link_library {* ref/models/saed
saed90nm_typ_ht.db saed90nm_typ_ht.lib
pt_shell> set link_library {* ref/models/saed90nm_typ_ht.db }
```

Read Gate level Netlist Files and Link design:

1. Type these lines to read in CIC .18 library and your gate level netlist.

```
read_verilog ./Counter_syn.v
```

2. Link all designs

```
link_design Counter
```

Note, to check the search path and include library, if the error message occurred after step 2.

Read Timing and RC information:


Reads leaf cell and net timing and RC information from a file in SPEF Format and uses that information to annotate the current design.

```
read_parasitics counter.spef
```

Note: The file can be get during synthesis with “write_parasitics” comment.

Set Operating Conditions:
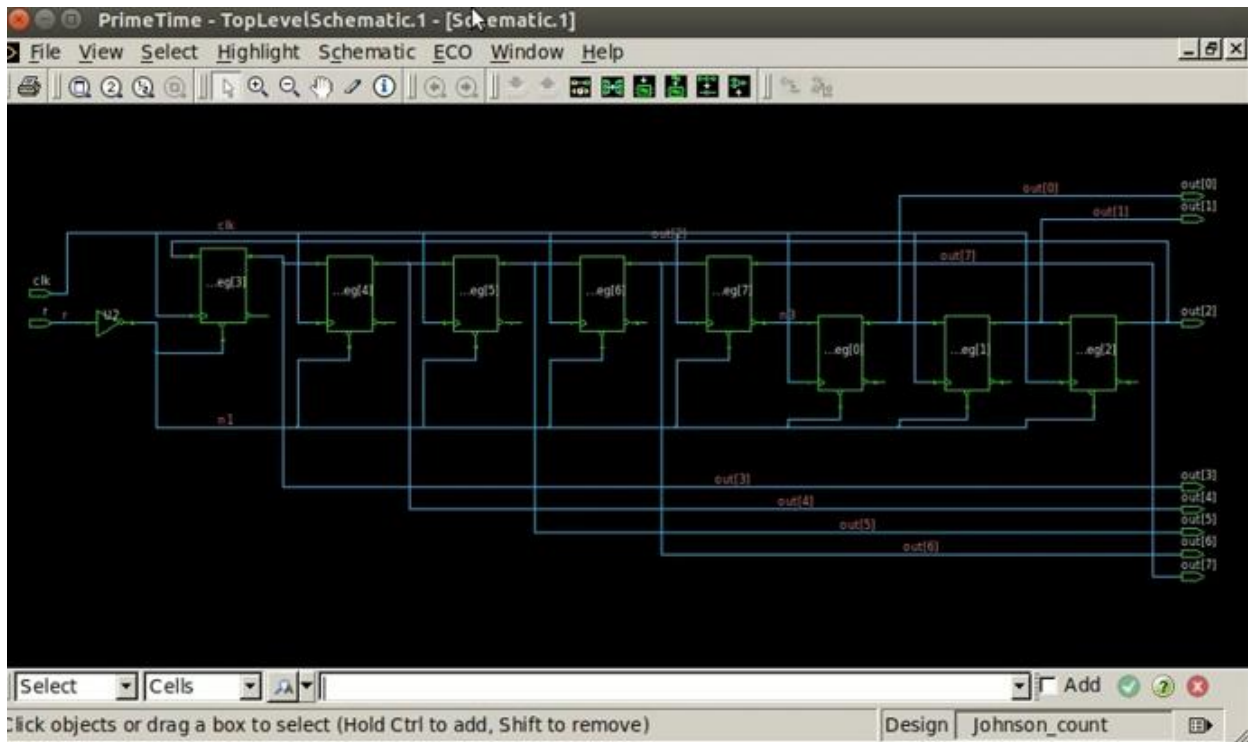
```
set_operating_conditions typical -library typical
```



Set Design Constraints:

This step tells the Dft Compiler how many scan chains are needed. specify the names of scan related pins (scan_enable, scan_in, scan_out).

```

1. Specify the clock name, period, and clock characteristic
create_clock -period 10 -waveform {0 5} [get_ports clk]
set_design_clock [get_clock clk]
set_clock_uncertainty 0.5 $design_clock
set_clock_latency -min 1.5 $design_clock
set_clock_latency -max 2.5 $design_clock
set_clock_transition -min 0.25 $design_clock
set_clock_transition -max 0.30 $design_clock
set_propagated_clock $design_clock

```

```

2. Set wire load model
set_wire_load_model -name "ForQA" -library "typical"

```

```

3. Set wire load mode
set_wire_load_mode top

```

```

4. Report
report_design
report_reference

```

```

~/Desktop/synopsys_example/DesignCompiler/dc
clock clock (rise edge)          70.000    70.000
clock network delay (ideal)      0.000    70.000
out_reg[7]/CLK (DFFARX1)        0.000    70.000 r
out_reg[7]/QN (DFFARX1)        0.224    70.224 r
U1/Z (AOBUF2)                   0.129    70.353 r
out_reg[0]/D (DFFARX1)         0.032    70.385 r
data arrival time                70.385

clock clock (rise edge)          190.000   190.000
clock network delay (ideal)      0.000   190.000
clock reconvergence pessimism    0.000   190.000
out_reg[0]/CLK (DFFARX1)        190.000 r
library setup time              -0.161   189.839
data required time               189.839
-----
data required time                189.839
data arrival time                 -70.385
-----
slack (MET)                       119.454

pt_shell> write_changes -format text -output eco
1
pt_shell> pt_shell>

```

Timing analysis and report possible problems:

This step checks your scan specification for consistency. Please type the following commands to set the input/output delay:

```

set_input_delay 1.5 [get_ports inputA] -clock $design_clock
set_input_delay 1.5 [get_ports inputB] -clock $design_clock
set_input_delay 1.5 [get_ports instruction] -clock $design_clock
set_input_delay 1.5 [get_ports reset] -clock $design_clock
set_output_delay 1.5 [get_ports alu_out] -clock $design_clock

```

And then check the timing:

```

check_timing
set true_delay_prove_true_backtrack_limit 20000
report_timing -true
report_bottleneck

```

RESULT:

Thus the static timing analysis of the given circuit has been studied.

EXP NO: 14

Date:

DfT – Scan Chain Insertion

AIM:

To study the given circuit and perform DfT-Scan chain insertion using Synopsys -TetraMaxtools.

APPARATUS REQUIRED:

S.No	Nameofthe equipment/ software	Quantity
1.	PC with Windows	1
2.	Synopsys - TetraMax tool	1

PROCEDURE:

Invoke DftCompiler

Dft Compiler is actually embedded in the Design Compiler.

To invoke Dft Compiler, choose either options.

dc_shell (command mode)

dv &(GUI mode)

Command mode is preferred because:

- a. Command mode helps you to keep a record of what you have done.
- b. Command mode runs more efficiently than GUI mode.
- c. Command mode helps you to lookup the manual/reference quickly.

In spite of the above advantages, command mode sometimes is not as good as GUI mode in terms of debugging the schematic problem.

NOTE: maybe occurrence of some error message like “Error: current design notdefined.” just ignore it for now.

STEP 1: Read Input Files

1. Please check there is no error message when starting the “dc_shell”. If there are errors in the windows, please check the .synopsys_dc.setup. Type either one of these lines to read your gate level netlist (The circuit after synthesis).

read_verilog ALU_syn.v

read_file ALU_syn.v -format Verilog

2. Set the working design to you top design. In this case, set ALU as the working design.

current_design ALU

3. Resolve the design references and check if there is any errors.

Link check_design

4. Set the design constraints and check if the designs have any violations. The constraints.tcl is based on the constraints that you used in the synthesis lab.

```
source constraints.tcl  
report_constraint -all_violators
```

5. To obtain a timing/area/power report of your original design, type (where ALU is your top design)

```
report_area > ALU_syn.area_rpt  
report_timing > ALU_syn.timing_rpt  
report_power > ALU_syn.power_rpt
```

STEP 2: Select scan style

Define the default scan style for the insert_dft command if a scanstyle is not specified with the set_scan_style command. This variable must identify one of the following supported scan styles: multiplexed_flip_flop, clocked_scan, lssd, aux_clock_lssd, combinational, or none. You can skip this step because the default is multiplexed_flip_flop.

```
set test_default_scan_style multiplexed_flip_flop
```

STEP 3: Set ATE configuration and create test protocol

The timing of the test clock is based on the test_default_period, test_default_delay, test_default_strobe, and test_default_strobe_width variables.

```
set test_default_delay 0  
set test_default_bidir_delay 0  
set test_default_strobe 40  
set test_default_period 100
```

To create a test protocol for a non-scan design, you can just type


```
create_test_protocol -infer_asynch -infer_clock
```

When -infer_asynch is specified, create_test_protocol infers asynchronous set and reset signals in the design, and places them at offstate during scan shifting. When -infer_clock is specified, create_test_protocol infers test clock pins from the design, and pulses them during scan shifting.

STEP 4: Pre-scan Check

Check if there is any design constraint violations before scan insertion.
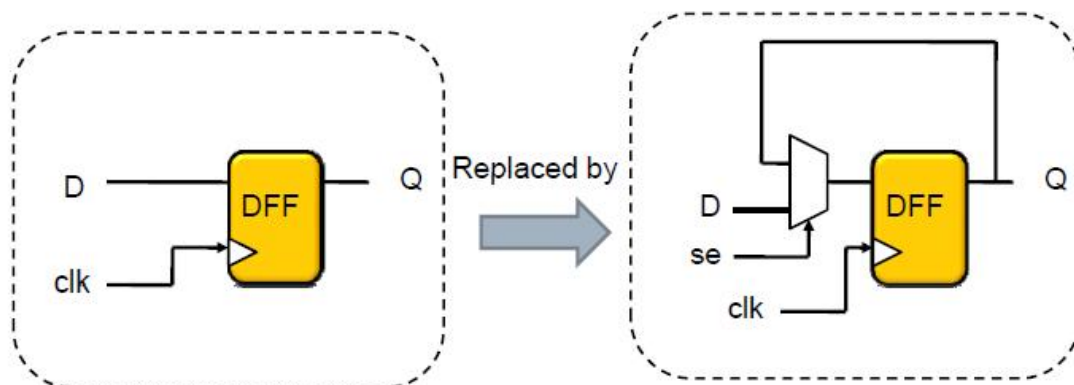
```
report_constraint -all_violators  
Perform pre-scan test design rule checking.  
dft_drc
```



STEP 5: Scan specification

This step tells the Dft Compiler how many scan chains needed. This allows to specify the names of scan related pins (scan_enable, scan_in,scan_out).

set_scan_configuration -chain_count 1

STEP 6: Scan preview

This step checks your scan specification for consistency. Please type **preview_dft**

STEP 7: scan chain synthesis

Stitch your scan cells into a chain. And do some more optimizations.

insert_dft

STEP8: Post-scan check

Check if there is any design constraint violations after scan insertion.

report_constraint -all_violators

Perform post-scan test design rule checking.

dft_drc

```
Resetting current test mode
Beginning Mapping Optimizations

In mode: Internal scan...
Design has scan chains in this mode
Design is scan routed
Post-DFT DRC enabled

Information: Starting test design rule checking. [TRST-222]
Loading test protocol
..basic checks...
..basic sequential cell checks...
..checking vector rules...
..checking clock rules...
..checking scan chain rules...
..checking scan compression rules...
..checking X-state rules...
..checking tristate rules...
..extracting scan details...
..saving simulation value info...

-----
Begin Modeling violations...
```

Pattern Summary Report		
#internal patterns		0

Uncollapsed Stuck Fault Summary Report		
fault class	code	#faults
Detected	DT	2164
Possibly detected	PT	0
Undetectable	UD	90
ATPG untestable	AU	150
Not detected	ND	0

total faults		2404
test coverage		93.52%

Information: The test coverage above may be inferior than the real test coverage with customized protocol and test simulation library.		

STEP 9: Reports


Report the scan cells and the scan paths

report_scan_path -view existing -chain all > ALU_syn_dft.scan_path

report_scan_path -view existing -cell all > ALU_syn_dft.scan_cell

To obtain a timing/area report of your scan_inserted design, type

report_timing > ALU_syn_dft.timing_rpt

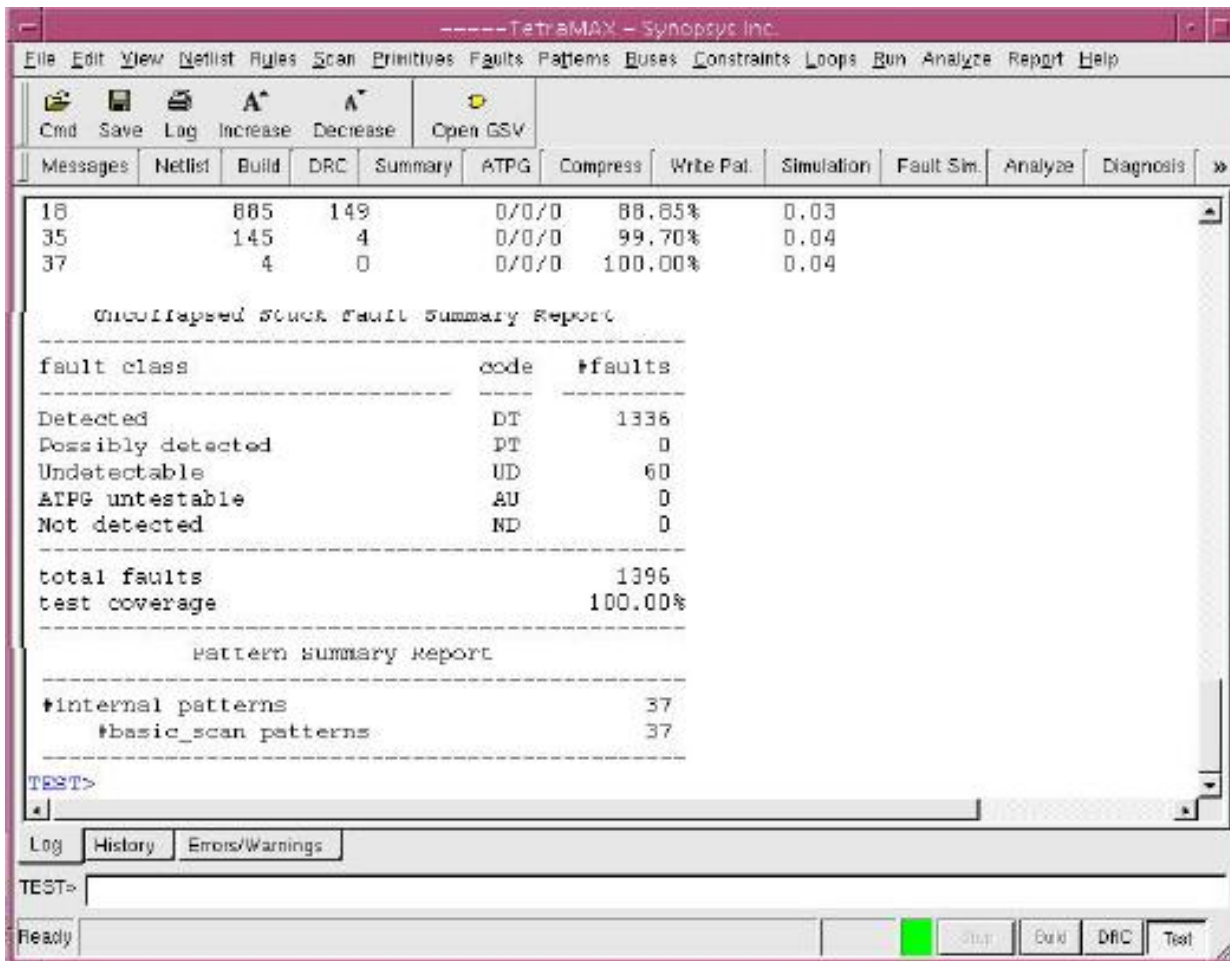

RESULT:

Thus the DfT-Scan chain insertion of the given circuit has been studied.

