



श्रीचन्द्रशेखरेन्द्रसरस्वतीविश्वमहाविद्यालयः  
**SRI CHANDRASEKHARENDRASARASWATHI VISWA MAHAVIDYALAYA**

Deemed to be University u/s 3 of UGC Act 1956 | Accredited with "A" grade by NAAC  
Enathur, Kanchipuram - 631 561, Tamilnadu, India | [www.kanchiuniv.ac.in](http://www.kanchiuniv.ac.in)  
Sponsored and run by Sri Kanchi Kamakoti Peetam Charitable Trust



**LABORATORY MANUAL**  
of  
**COMPUTER AIDED SYSTEM DESIGN LABORATORY**  
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

Prepared by: Dr.M.Vinoth  
Assistant Professor

# Computer Aided System Design Laboratory Manual

B.E (ECE) – FULL TIME

V SEMESTER



DEPARTMENT OF ELECTRONICS & COMMUNICATION  
ENGINEERING

SRI CHANDRASEKHARENDRASARASWATHI VISWA  
MAHAVIDYALAYA

(A University U/S 3 of UGC Act 1956)

Enathur, Kanchipuram 631561

## LIST OF EXPERIMENTS

1. Verify the characteristics (AC and Transient Analysis) of RLC Circuits by using the PSPICE Software.
2. Verify the characteristics Positive and Negative clamper by using the PSPICE Software.
3. Verify the characteristics Half Wave Rectifier and Full Wave Rectifier (Bridge rectifier) by using the PSPICE Software.
4. Verify the Input and Output characteristics of BJT by using the PSPICE Software.
5. Verify the characteristics Transient analysis of Common Emitter Amplifier by using the PSPICE Software.
6. Verify the Input and Output characteristics of CMOS by using the PSPICE Software
7. Verify the Truth Table for the concept of 4:1 Multiplexer using the PSPICE software.
8. Verify the Truth Table for the concept of Counter Circuit using the PSPICE software.
9. Verify the Truth Table for the concept of Flip-flop Circuit using the PSPICE software.
10. Write the VHDL code for the concept of Basic Logic Gates, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
11. Write the VHDL code for the concept of Full Adder, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
12. Write the VHDL code for the concept of Full Subtractor, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
13. Write the VHDL code for the concept of Multiplexer and Demultiplexer, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
14. Write the Verilog code for the concept of 8 bit Adder (Ripple Carry Adder), simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
15. Write the Verilog code for the concept of Flip-Flops, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.
16. Write the Verilog code for the concept of Ripple Counter, Simulate it by using the Xilinx ISE Simulator and implement it with the available FPGA device.

Exp:-1

## AC AND TRANSIENT ANALYSIS OF RC CIRCUITS

### Aim :

To verify the AC AND TRANSIENT ANALYSIS of a Low Pass and High Pass filter circuits by using the PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed



### COMPONENTS:

sno	component	Range	quantity
1	AC source(vac)	5v	1
2	resistor	1k	1
3	capacitor	1n	1
4	ground	-	1
5	Voltage probe	-	1
6	vsin	0,5v,1khz	1


### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For ac analysis choose vsin 0,5v,1khz.
- For transient analysis choose vdc and 5v.
- Give the ac analysis the default values
- For transient analysis give the 0-10ms time.
- Simulate the circuit.


**CIRCUIT DIAGRAM:**

  

## LOW PASS CIRCUIT:

 


Ac analysis

 


transient analysis

## HIGH PASS CIRCUIT:

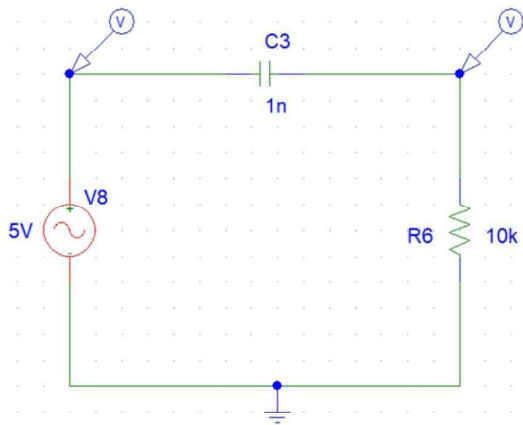


Ac analysis

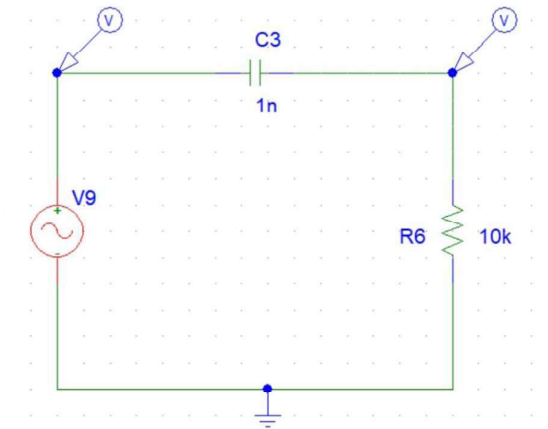


transient analysis

## Ac Analysis

 


High pass filter

 


Low pass filter

## Transient Analysis

 

HIGH PASS FILTER

 

Low pass filter

Low pass filter code:-

**\*\* Analysis setup \*\***

**.ac LIN 101 10 1.00K**

**.tran 0ns 10m 0 0.01ms**

**.OP**

**\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:**

**.lib "nom.lib"**

**.INC "low pass filter.net"**



**\*\*\*\* INCLUDING "low pass filter.net" \*\*\*\***

**\* Schematics Netlist \***

**R\_R1      \$N\_0002 \$N\_0001 1k**  
**C\_C1      0 \$N\_0001 1n**  
**V\_V4      \$N\_0002 0 DC 0V AC 5V 0**

**\*\*\*\* RESUMING "low pass filter.cir" \*\*\*\***

**.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)**

**.END**

**High pass filter code:-**

**\*\* Analysis setup \*\***

**.tran 0ns 10m 0 0.01ms**

**.ac LIN 101 10 1.00K**

**.OP**

**.STMLIB "low pass filter.stl"**

**\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:**

**.lib "nom.lib"**

**.INC "high pass filter.net"**

**\*\*\*\* INCLUDING "high pass filter.net" \*\*\*\***

**\* Schematics Netlist \***

**C\_C3      \$N\_0001 \$N\_0002 1n**  
**R\_R6      0 \$N\_0002 10k**

```
V_V9    $N_0001 0
+SIN 0 5 1khz 0 0 0
```

```
**** RESUMING "high pass filter.cir" ****
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.END
```

**RESULT:**

Thus the characteristics of Low Pass and High Pass filter circuit have been verified .

## Exp : 2

### POSITIVE AND NEGATIVE CLAMPER

#### Aim:

To verify the characteristics of a POSITIVE AND NEGATIVE CLAMPER circuits by using PSPICE software.

#### Apparatus:

PC with PSPICE VERSION 9.1 installed

#### COMPONENTS:-


sno	component	Range	quantity
1	vsin	0,5v,1khz	1
2	resistor	10k	1
3	capacitor	1u	1
4	ground	-	1
5	Voltage probe	-	1
6	diode	D1n4002	1
7	vdc	5v	1

#### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For transient analysis choose vac and 5v.
- For transient analysis give the 0-10ms time.
- Simulate the circuit.


#### CIRCUIT DIAGRAMS:

positive clamper

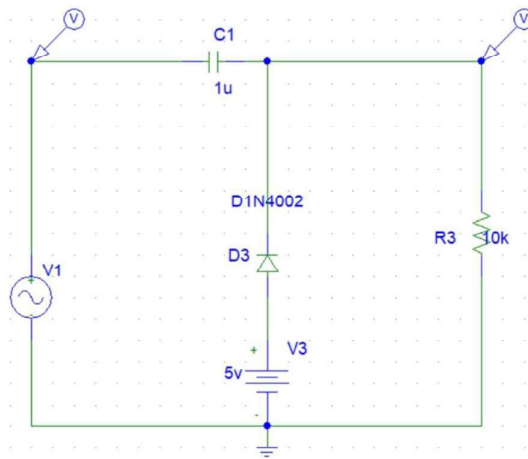


AM:

POSITIVE CLAMPER

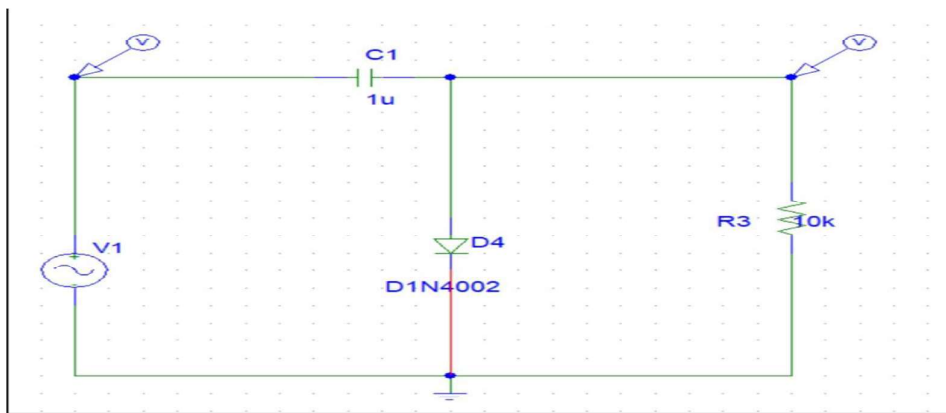


NEGATIVE CLAMPER

WAVEFORMS:

 

POSITIVE CLAMPRER

 

NEGATIVE CLAMPER

Positive clamper code:-

**\*\* Analysis setup \*\***

.tran 0ns 10ms

.OP

\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:

.lib "nom.lib"

.INC "1628574735364\_positive clamper.1.net"

**\*\*\*\* INCLUDING "1628574735364\_positive clamper.1.net" \*\*\*\***

\* Schematics Netlist \*

D\_D3      \$N\_0001 \$N\_0002 D1N4002

C\_C1      \$N\_0003 \$N\_0002 1u

V\_V3      \$N\_0001 0 5v

V\_V1      \$N\_0003 0

+SIN 0v 5v 1khz 0 0 0

R\_R3      0 \$N\_0002 10k

**\*\*\*\* RESUMING "1628574735364\_positive clamper.1.cir" \*\*\*\***

.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)

.END

Negative clamper code:-

```
** Analysis setup **
```

```
.tran 0ns 10ms
```

```
.OP
```

```
* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:
```

```
.lib "nom.lib"
```

```
.INC "1628574735364_negative clamper.1.net"
```

```
**** INCLUDING "1628574735364_negative clamper.1.net" ****
```

```
* Schematics Netlist *
```

```
C_C1      $N_0001 $N_0002 1u
```

```
V_V1      $N_0001 0
```

```
+SIN 0v 5v 1khz 0 0 0
```

```
R_R3      0 $N_0002 10k
```

```
D_D4      $N_0002 0 D1N4002
```

```
**** RESUMING "1628574735364_positive clamper.1.cir" ****
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.END
```

## RESULT:

Thus the characteristics of positive and negative clamper have been verified .

### Exp : 3

## HALF WAVE ANF FULL WAVE RECTIFIER

### Aim:

To verify the characteristics of a HALF WAVE ANF FULL WAVE RECTIFIER (BRIDGE RECTIFIER) circuits by using PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed


### COMPONENTS:-

sno	component	Range	quantity
1	vsin	0,5v,1khz	1
2	resistor	10k,1k	1 each
3	capacitor	1u	1
4	ground	-	1
5	Voltage probe	-	1
6	diode	D1n4002	4


### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For transient analysis choose vdc and 5v.
- For transient analysis give the 0-10ms time.
- Simulate the circuit.

### CIRCUIT DIAGRAMS:

 


HALF WAVE RECTIFIER

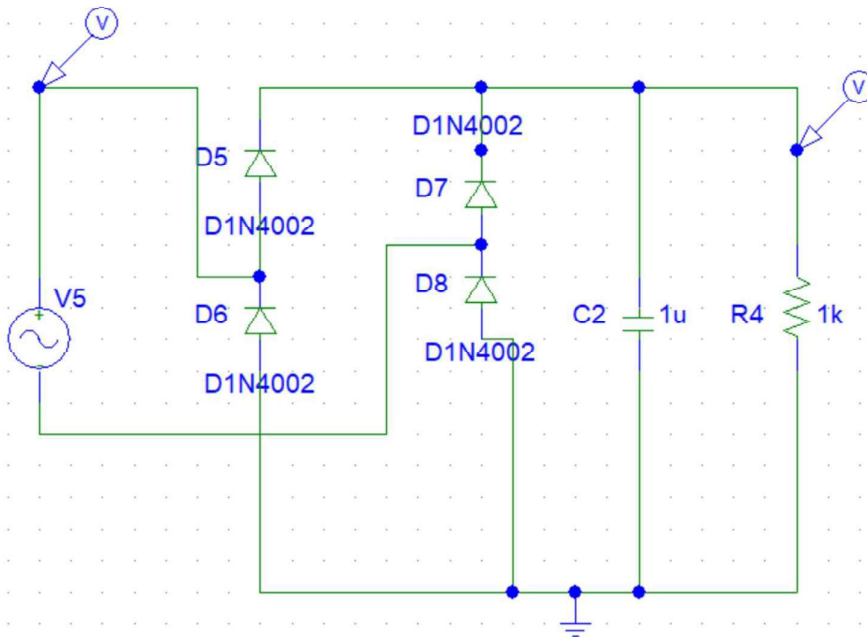


FULL WAVE RECTIFIER

**WAVEFORMS:**



 

HALF WAVE RECTIFIER

 

FULL WAVE BRIDGE RECTIFIER

Halfwave rectifier code:-

```

** Analysis setup **
.tran 0ns 10ms
.OP

* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:
.lib "nom.lib"

.INC "half wave rectifier (1).net"

```

```
**** INCLUDING "half wave rectifier (1).net" ****
```

```
* Schematics Netlist *
```

```
D_D5      $N_0001 $N_0002 D1N4002
```

```
V_V1      $N_0001 0
```

```
+SIN 0v 5v 1khz 0 0 0
```

```
R_R2      0 $N_0002 10k
```

```
**** RESUMING "half wave rectifier (1).cir" ****
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.END
```

Full wave rectifier code:-

```
** Analysis setup **
```

```
.tran 0ms 10ms
```

```
.OP
```

```
* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:
```

```
.lib "nom.lib"
```

```
.INC "bridge rectifier.net"
```

```
**** INCLUDING "bridge rectifier.net" ****
```

```
* Schematics Netlist *
```

```
V_V5      $N_0001 $N_0002
```

```
+SIN 0V 5V 1KHZ 0 0 0
```

```
D_D6      0 $N_0001 D1N4002
```

```
D_D5      $N_0001 $N_0003 D1N4002
```

```
R_R4      0 $N_0003 1k
```

```
C_C2      0 $N_0003 1u
D_D7      $N_0002 $N_0003 D1N4002
D_D8      0 $N_0002 D1N4002
```

```
**** RESUMING "positive clamper.cir" ****
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.END
```

## **RESULT:**

Thus the characteristics of half wave and fullwave rectifier have been verified .

## Exp : 4

### WEIN BRIDGE OSCILLATOR

#### Aim:

To verify the characteristics of a WEIN BRIDGE OSCILLATOR circuit by using PSPICE software.

#### Apparatus:

PC with PSPICE VERSION 9.1 installed


#### COMPONENTS:-

sno	component	Range	quantity
1	resistor	10k,20k	3,1
2	capacitor	33nf	2
3	ground	-	1
4	Voltage probe	-	1
5	amplifier	Ua741	1
6	vdc	15v	2


#### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For transient analysis choose vdc and 5v.
- For transient analysis give the 0-10ms time.
- Set to skip the initial conditions in transient setup.
- Simulate the circuit.

#### CIRCUIT DIAGRAMS:

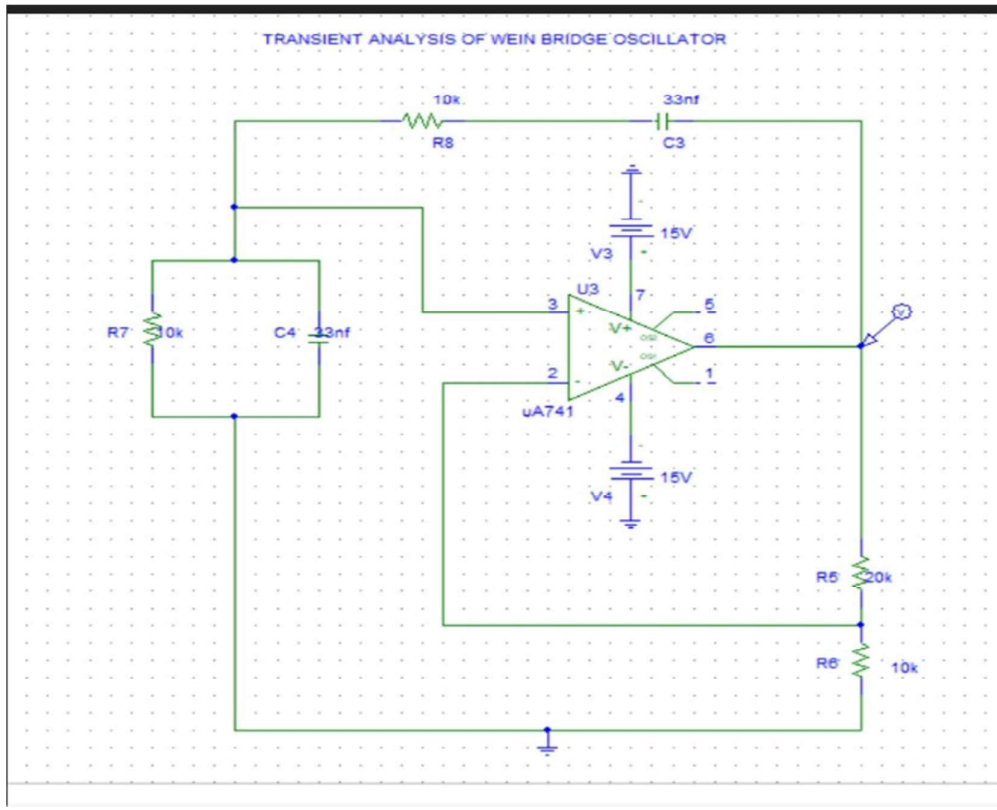

**Wave forms:-**

 

**Code:-**

```
** Analysis setup **
.tran 0ns 10ms 0 0.01ms SKIPBP
.OP
```

\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:  
.lib "nom.lib"

.INC "wein bridge oscillator.net"

\*\*\*\* INCLUDING "wein bridge oscillator.net" \*\*\*\*

\* Schematics Netlist \*

C\_C2      \$N\_0001 \$N\_0002 33nf  
R\_R3      \$N\_0003 \$N\_0001 20k  
R\_R2      0 \$N\_0003 10k  
C\_C1      0 \$N\_0004 33nf  
R\_R1      0 \$N\_0004 10k  
X\_U2      \$N\_0004 \$N\_0003 \$N\_0005 \$N\_0006 \$N\_0001 uA741  
R\_R4      \$N\_0002 \$N\_0004 10k  
V\_V1      \$N\_0005 0 15V  
V\_V2      0 \$N\_0006 15V

\*\*\*\* RESUMING "wein bridge oscillator.cir" \*\*\*\*

.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)

.END

### RESULT:

Thus the characteristics of wein bridge oscillator  
have been verified

## Exp : 5

### INVERTING & NON-INVERTING AMPLIFIER

#### Aim:

To verify the characteristics of a Inverting & Non Inverting Amplifier circuits by using PSPICE software.

#### Apparatus:

PC with PSPICE VERSION 9.1 installed


#### COMPONENTS:-

sno	component	Range	quantity
1	AC source(vac)	5v	1
2	resistor	10k	5
3	capacitor	1u	2
4	ground	-	1
5	Voltage probe	-	1
6	amplifier	Ua741	1
7	vdc	12v	2
6	vsin	0,5v,1khz	1


#### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For transient analysis choose vdc and 5v.
- For ac analysis choose vsin 0,5v,1khz.
- He ac analysis is for voltage and in decade mode and settings shown in figure.
- For transient analysis give the 0-10ms time.
- Simulate the circuit.

## Circuit diagrams:-

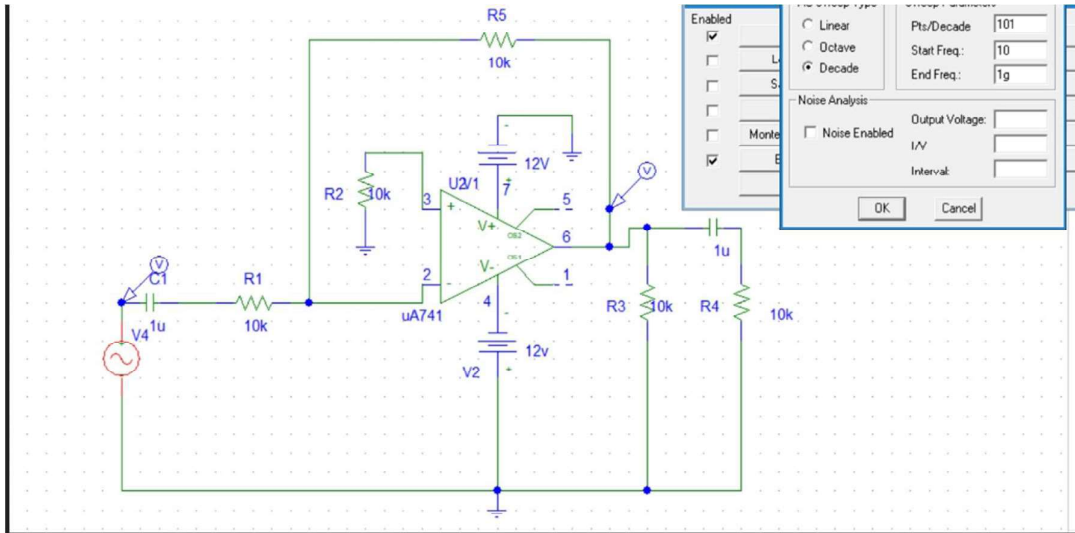

**INVERTING AMPLIFIER CIRCUIT**

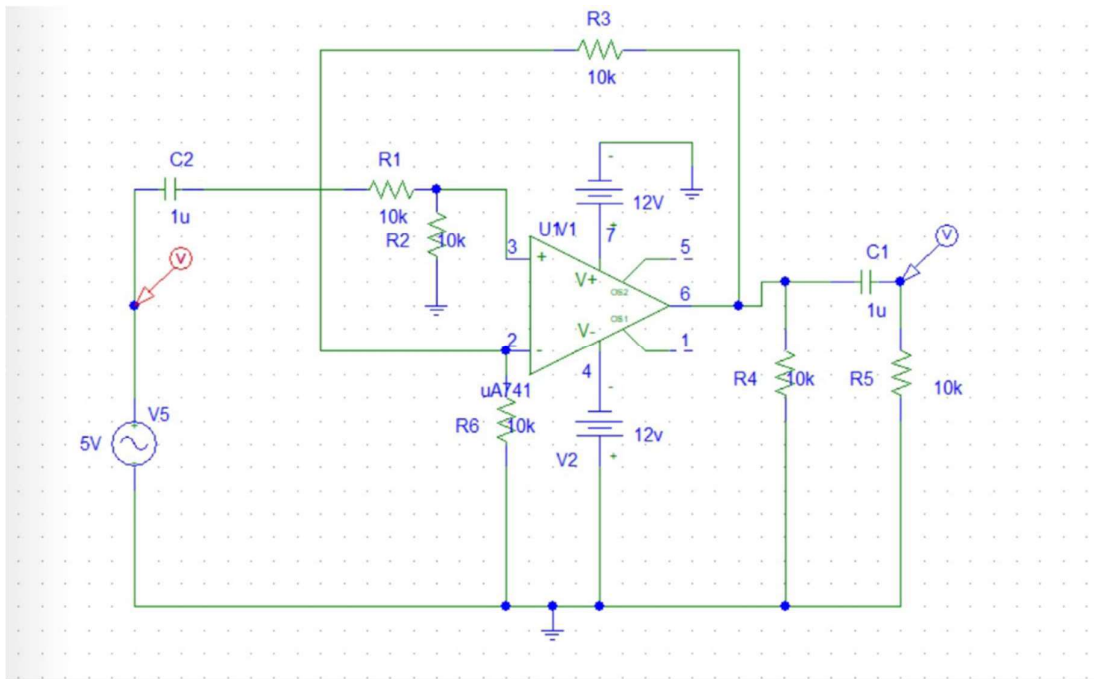


**NON-INVERTING AMPLIFIER**


## OUTPUT OF INVERTING AMPLIFIER:-

Ac analysis



 


 Transient analysis for inverting amplifier :-




**NON INVERTING AMPLIFIER:-**

**Ac analysis**

 

**Transient analysis:-**

 

## CIRCUIT FILE:

INV OP (AC & TRANSIENT)

VIN 1 0 AC 1.5V PWL(0 0 1NS -1V 1MS -1V 1.0001MS 1V 2MS 1V 2.0001MS -1V 3MS -  
1V 3.0001MS 1V 4MS 1V)

R1 1 2 2.5K

RF2310K

RL 3 0 100K

XA1 2 0 3 0 OPAMP

.SUBCKT OPAMP 1 2 7 4

RI 1 2 2.0E6

GB43120.1M

R13410K

C1 3 4 1.5619UF

EA45342E+5

RO5775

.ENDS

.PROBE

.AC DEC 50 100 1E9

.PLOT AC VP(3) VM(3) 0,250

.TRAN 5e-005 4MS 0

.TEMP 27

.PLOT

TRAN V(3) V(1) -10,15

.END

**RESULT**: Thus the characteristics of Inverting and Non - inverting circuit have been verified.

Exp:-6

## INPUT AND OUTPUT CHARACTERISTICS OF BJT

### Aim :

To verify the input and output characteristics of BJT by using the PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed


### COMPONENTS:-

sno	component	Range	quantity
1	ground	-	1
2	bjt	Q2n222	1
3	vdc	5v,20v	1 each

### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- Perform dc sweep in the bjt and nested sweep for input and output values.
- For input characteristics set the trace to IB(q1).
- For output characteristics set the trace to IC(q1).
- The dc sweep values are in figure.
- Simulate the circuit.

### CIRCUIT DIAGRAMS:

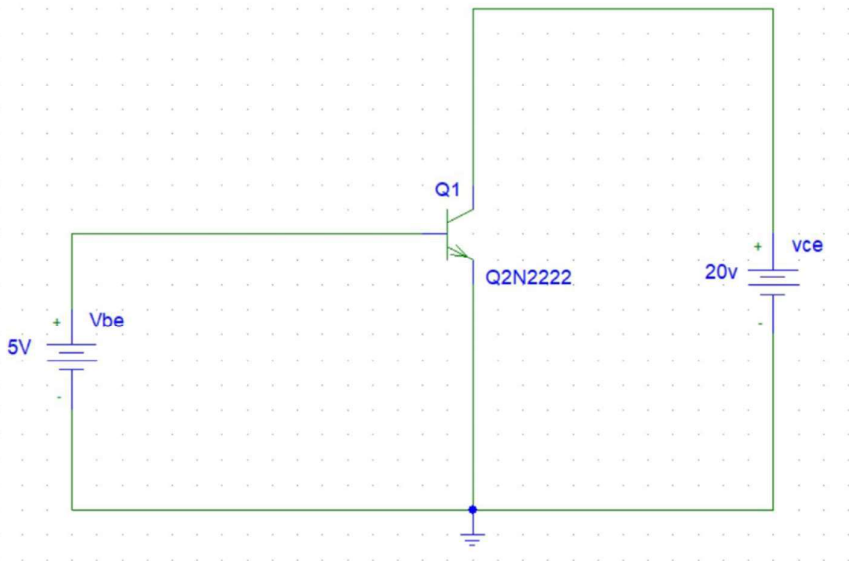

**BJT INPUT DC SWEEP VALUES**

**DC Sweep**

Swept Var. Type  
 Voltage Source  
 Temperature  
 Current Source  
 Model Parameter  
 Global Parameter

Name:   
 Model Type:   
 Model Name:   
 Param. Name:

Sweep Type  
 Linear  
 Octave  
 Decade  
 Value List

Start Value:   
 End Value:   
 Increment:   
 Values:

Nested Sweep... OK Cancel

**DC Nested Sweep**

Swept Var. Type  
 Voltage Source  
 Temperature  
 Current Source  
 Model Parameter  
 Global Parameter

Name:   
 Model Type:   
 Model Name:   
 Param. Name:



Sweep Type  
 Linear  
 Octave  
 Decad  
 Value List

Start Value:   
 End Value:   
 Increment:   
 Values:

Main Sweep...  Enable Nested Sweep  
 OK Cancel



**Output characteristics:-**

 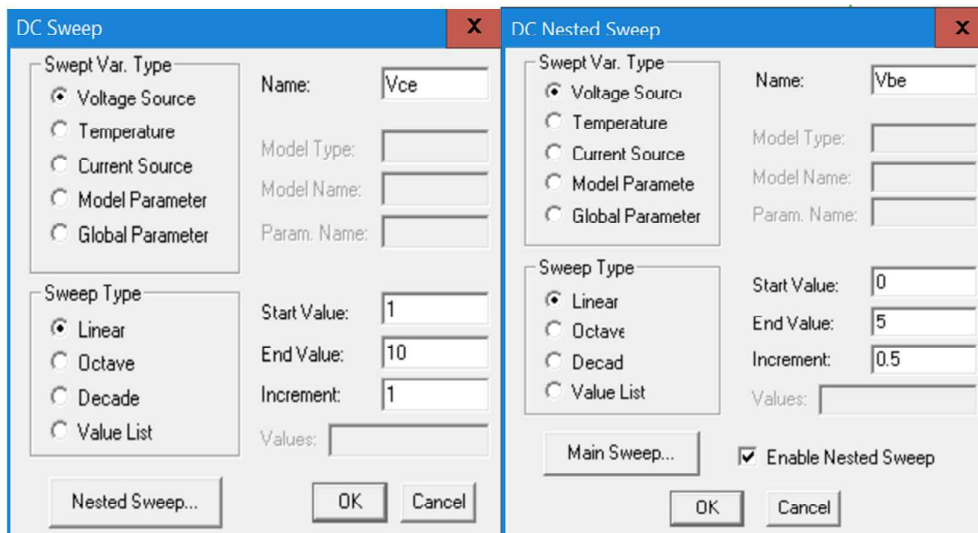

Code:-

**\*\* Analysis setup \*\***

**.tran 0ns 2ms**

**.OP**

**\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:**

**.lib "nom.lib"**

**.INC "bjt input.net"**

**.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)**

**.END**

**Output code:-**

**\*\* Analysis setup \*\***

**.DC LIN V\_VCE 1 10 1**

**+ LIN V\_VBE 0 5 0.5**

**.DC LIN V\_VBE 0 5 0.5**

**+ LIN V\_VCE 1 10 1**

**.OP**

**\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:**

**.lib "nom.lib"**

**.INC "BJT output characteristics.net"**

**.PROBE V(\*) I(\*) W(\*) D(\*) NOISE(\*)**

**.END**

**Result:-** Thus the input and output characteristics of BJT have been verified.

Exp:-7

## TRANSIENT ANALYSIS OF COMMON EMITTER PNP AMPLIFIER

### Aim :

To verify the transient analysis of common emitter pnp amplifier by using the PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed

#### COMPONENTS:-


sno	component	Range	quantity
1	vsin	0,5v,1khz	1
2	resistor	500,47k,20k,10k,5k	1,1,1,1,2
3	capacitor	10uf	3
4	ground	-	1
6	bjt	Q2N2907	1
7	vdc	15v	1

### PROCEDURE:


- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- Perform the transient analysis on common emitter pnp transistor with 0-2ms.
- Simulate the circuit.

Circuit diagram:-



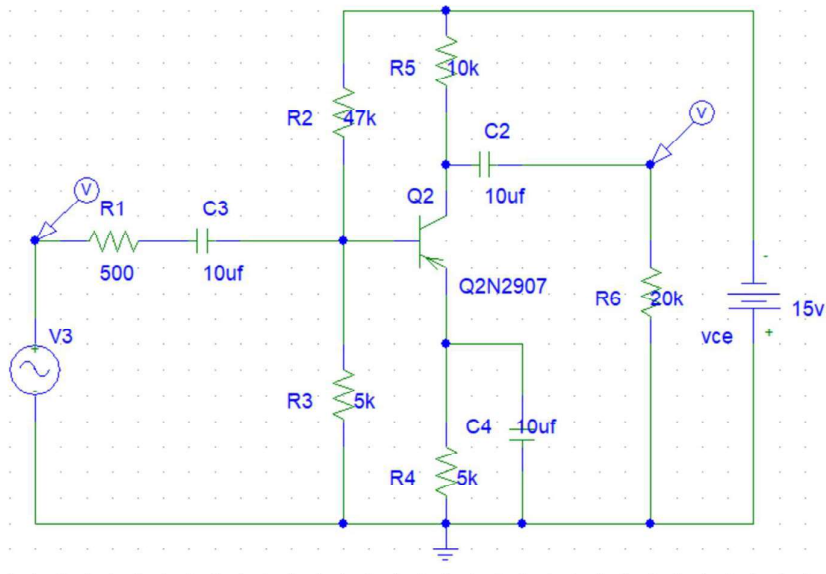

Waveform :-

 

Code:-

```
.AC DEC 10 1hz 10khz;
```

```
VIN 1 0 AC 10mv sin(0 10mv 1khz);
```

```
VCC 0 7 DC 15v;
```

```
Rs 1 2 500;
```

```
R1 7 3 47k;
```

```
R2 3 0 5k;
```

```
RC 7 4 10k;
```

```
RE 5 0 2k;
```

```
RI 6 0 20k;
```

```
C1 2 3 10uF;
C2 4 6 10uF;
CE 5 0 10uF;
Q1 4 3 5 0 Q2n2907;
.model Q2N2907 PNP(Is = 650.6E-18 Xti=3 Eg=1.11 Vaf=115.7 Bf=231.7 Ne=1.829
+Ise =54.81f Ikf=1.079 Xtb=1.5 Br=3.563 Nc=2 Isc=0 Ikr=0 Rc=.715
+Cjc=14.76p Mjc=.5383 Vjc=.75 Fc=.5 Cje=19.82p Mje=.3357 Vje=.75
+Tr=111.3m Tf=603.7p Itf=.65 Vtf=5 Xtf=1.7 Rb=10)
* National pid=63 case=TO18
* 88-09-09 bam creation
.tran 50us 2ms;
.plot tran V(4) V(6) V(1);
.plot AC VM(6) VP(6);
.probe;
.end;
```

**Result:-**

Thus the transient analysis of common emitter pnp amplifier have been verified.

Exp:-8

## INPUT AND OUTPUT CHARACTERISTICS OF MOSFET

### Aim :

To verify the input and output characteristics of MOSFET by using the PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed


### COMPONENTS:-

sno	component	Range	quantity
1	ground	-	1
2	bjt	MbreakN	1
3	vdc	10v	2

### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- Perform dc sweep in the mosfet and nested sweep for input and output values.
- For input characteristics set the trace to IG(M1).
- For output characteristics set the trace to ID(M1).
- The dc sweep values are in figure.
- Simulate the circuit.

### CIRCUIT DIAGRAMS:

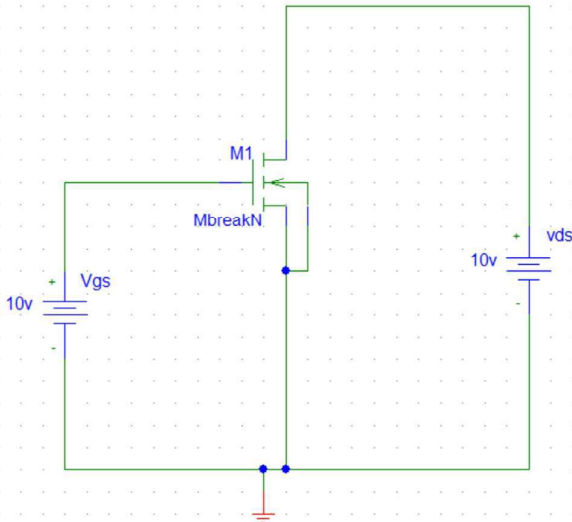

### Mosfet INPUT DC SWEEP VALUES

#### DC Sweep

**Swept Var. Type**

- Voltage Source
- Temperature
- Current Source
- Model Parameter
- Global Parameter

Name:

Model Type:

Model Name:

Param. Name:

**Sweep Type**

- Linear
- Octave
- Decade
- Value List

Start Value:

End Value:

Increment:

Values:

#### DC Nested Sweep

**Swept Var. Type**

- Voltage Source
- Temperature
- Current Source
- Model Parameter
- Global Parameter

Name:

Model Type:

Model Name:

Param. Name:

**Sweep Type**

- Linear
- Octave
- Decad
- Value List


Start Value:

End Value:

Increment:


Values:

Enable Nested Sweep

 

## Output characteristics:-

DC Sweep		DC Nested Sweep	
Swept Var. Type	Name: vds	Swept Var. Type	Name: vgs
<input checked="" type="radio"/> Voltage Source	Model Type:	<input checked="" type="radio"/> Voltage Source	Model Type:
<input type="radio"/> Temperature	Model Name:	<input type="radio"/> Temperature	Model Name:
<input type="radio"/> Current Source	Param. Name:	<input type="radio"/> Current Source	Param. Name:
<input type="radio"/> Model Parameter		<input type="radio"/> Model Parameter	
<input type="radio"/> Global Parameter		<input type="radio"/> Global Parameter	
Sweep Type	Start Value: 0	Sweep Type	Start Value: 0
<input checked="" type="radio"/> Linear	End Value: 5	<input checked="" type="radio"/> Linear	End Value: 10
<input type="radio"/> Octave	Increment: 100mv	<input type="radio"/> Octave	Increment: 1
<input type="radio"/> Decade	Values:	<input type="radio"/> Decad	Values:
<input type="radio"/> Value List		<input type="radio"/> Value List	
Nested Sweep...	OK Cancel	Main Sweep... <input checked="" type="checkbox"/> Enable Nested Sweep	OK Cancel

 

code:-

**\*\* Analysis setup \*\***

```
.DC LIN V_Vgs 0 10 0.5
```

```
+ LIN V_vds 0 10 1
```

```
.DC LIN V_vds 0 10 1
```

```
+ LIN V_Vgs 0 10 0.5
```

```
.OP
```

\* From [PSPICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:

```
.lib "nom.lib"
```

```
.INC "mosfet char.net"
```

```
**** INCLUDING "mosfet char.net" ****
```

```
* Schematics Netlist *
```

```
V_Vgs    $N_0001 0 10v
```

```
M_M1     $N_0002 $N_0001 0 0 MbreakN
```

```
V_vds    $N_0002 0 10v
```

```
**** RESUMING "mosfet char.cir" ****
```

```
.PROBE V(*) I(*) W(*) D(*) NOISE(*)
```

```
.END
```

**Result:-**

Thus the input and output characteristics of BJT have been verified.

Exp:-9

## DC AND TRANSIENT ANALYSIS OF CMOS INVERTER

### Aim :

To verify the DC AND TRANSIENT ANALYSIS OF CMOS INVERTER circuits by using the PSPICE software.

### Apparatus:

PC with PSPICE VERSION 9.1 installed


### COMPONENTS:-

sno	component	Range	quantity
1	ground	-	1
2	mosfet	MbreakN,MbreakP	1 each
3	vsrc	5v	2
4	vpulse	-	1

### PROCEDURE:

- Get the components from the library
- Choose wire to join them
- Give appropriate names and values to elements
- For mbreakp  $L = 2\mu, W = 4\mu$ ;
- For mbreakn  $L = 2\mu, W = 2\mu$ ;
- For DC analysis choose vsrc and set to 5v.
- Add trace to v\_v1 and v(m1:d).
- For transient analysis choose vpulse and 5v.
- Add trace to v(m1:g) and v(m1:d).
- Give the ac analysis the default values
- For transient analysis give the 0-10ms time.
- Simulate the circuit.

### Circuit diagram:-

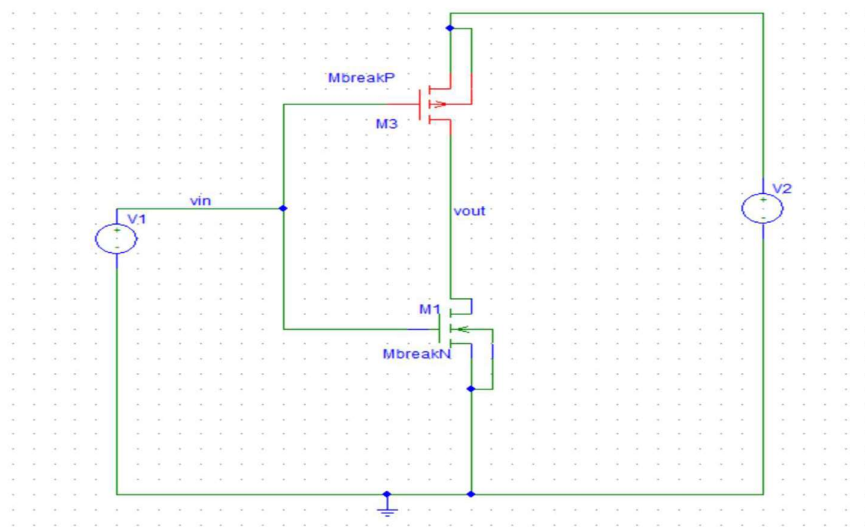

### Output for dc sweep:-

**DC Sweep** [X]

Swept Var. Type

- Voltage Source
- Temperature
- Current Source
- Model Parameter
- Global Parameter

Name: v1

Model Type: [ ]

Model Name: [ ]

Param. Name: [ ]

Sweep Type

- Linear
- Octave
- Decade
- Value List

Start Value: 0

End Value: 5

Increment: 0.0001

Values: [ ]

Nested Sweep... [OK] [Cancel]


**Transfer Function** [X]

Output Variable: v(vout)

Input Source: v1

[OK] [Cancel]



 


Output of transient analysis:-

V5 PartName: VPULSE

Name	Value
REFDES	= V5
V1=0	
V2=5	
TD=0	
TR=1n	
TF=1n	
PW=1s	
PER=2	

Include Non-changeable Attributes  
 Include System-defined Attributes

 Buttons: Save Attr, Change Display, Delete, OK, Cancel



Code:-

**\*\* Analysis setup \*\***

**.tran 0ns 10s**

**.OP**

**\* From [PSPIICE NETLIST] section of d:\pspice\PSpice\PSpice.ini:**

**.lib "nom.lib"**

**.INC "cmos inverter.net"**

**\*\*\*\* INCLUDING "cmos inverter.net" \*\*\*\***

**\* Schematics Netlist \***

**V\_V2     \$N\_0001 0 DC 5v**

**M\_M1     vout vin 0 0 MbreakN**

**+ L=2u**

**+ W=2u**

**M\_M3     vout vin \$N\_0001 \$N\_0001 MbreakP**

```
+ L=2u
+ W=4u
V_V5    vin 0 DC 5v
+PULSE 0 5 0 1n 1n 1s 2

**** RESUMING "cmos inverter.cir" ****
.PROBE V(*) I(*) W(*) D(*) NOISE(*)

.END
```

**Result:-**

Thus the DC and transient analysis of cmos inverter have been verified.

---

**Experiment Number:**

---

**Title of the Experiment:    BASIC LOGIC GATES**

---

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the Basic Logic Gates with the tools available in Xilinx Project Navigator using VHDL.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**

c) Xilinx (ISE) simulator 9.1


d) FPGA KIT

**Procedure for doing the experiment:**

<b>S.No</b>	<b>Details of the step</b>
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

## CIRCUIT DIAGRAM:

AND GATE:

 


2 Input AND gate		
A	B	A.B
0	0	0
0	1	0
1	0	0
1	1	1

OR GATE:



2 Input OR gate		
A	B	A+B
0	0	0
0	1	1
1	0	1
1	1	1

NOT GATE:

 

NOT gate	
A	A-bar
0	1
1	0

XOR GATE:



2 Input EXOR gate		
A	B	A⊕B
0	0	0
0	1	1
1	0	1
1	1	0

NAND GATE:



2 Input NAND gate		
A	B	$\overline{AB}$
0	0	1
0	1	1
1	0	1
1	1	0

NOR GATE:




2 Input NOR gate		
A	B	$\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

## VHDL CODE:

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity logic_gates is
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        AND1 : out STD_LOGIC;
        OR1 : out STD_LOGIC;
        NOT1 : out STD_LOGIC;
        XOR1 : out STD_LOGIC;
        NAND1 : out STD_LOGIC;
        NOR1 : out STD_LOGIC);
end logic_gates;
architecture Behavioral of logic_gates is
begin
AND1<=A AND B;
OR1<=A OR B;
NOT1<=NOT A;
XOR1<=A XOR B;
NAND1<= A NAND B;
NOR1<=A NOR B;
end Behavioral;
```

## OUTPUT:

 

## RESULT:

Thus the Basic Logic Gates have been simulated with the Truth Table by using Xilinx ISE Simulator.



---

**Experiment Number:**

---

**Title of the Experiment: FULL ADDER**

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the Full Adder with the tools available in Xilinx Project Navigator using VHDL.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**


c) Xilinx (ISE) simulator 9.1

d) FPGA KIT

**Procedure for doing the experiment:**

<b>S.No</b>	<b>Details of the step</b>
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

**LOGIC DIAGRAM:**

 

**TRUTH TABLE:**

A	B	C	SUM	CARRY
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## **FULL ADDER USING STRUCTURAL MODELLING:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity or_gate is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end or_gate;
architecture Behavioral of or_gate is
begin
    c<=a or b;
end Behavioral;
```

-----VHDL Code for and Gate----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity and_g is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end and_g;
architecture Behavioral of and_g is
begin
    c<=a and b;
end Behavioral;
```

-----VHDL Code for XOr Gate----

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity xor_g is
    Port ( a : in STD_LOGIC;
          b : in STD_LOGIC;
          c : out STD_LOGIC);
end xor_g;
architecture Behavioral of xor_g is
begin
    c<=a xor b;
```

```

end Behavioral;
-----VHDL Code for Full Adder----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity fulladder_structural is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          SUM : out STD_LOGIC;
          Cout : out STD_LOGIC);
end fulladder_structural;
architecture Behavioral of fulladder_structural is
    component or_gate is
        port(a,b:in std_logic;
             c:out std_logic);
    end component;
    component and_g is
        port(a,b:in std_logic;
             c:out std_logic);
    end component;
    component xor_g is
        port(a,b:in std_logic;
             c:out std_logic);
    end component;
    signal y1,y2,y3:std_logic;
begin
    x1:xor_g port map(A,B,y1);
    a1:and_g port map(A,B,y2);
    x2:xor_g port map(y1,Cin,sum);
    a2:and_g port map(y1,Cin,y3);
    r1:or_gate port map(y2,y3,Cout);
end Behavioral;

```

## **VHDL CODE:**


### **FULL ADDER USING DATAFLOW MODELLING:**

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity Full_Adder_Dataflow is
    Port ( A : in STD_LOGIC;
          B : in STD_LOGIC;
          Cin : in STD_LOGIC;
          Sum : out STD_LOGIC;
          Cout : out STD_LOGIC);
end Full_Adder_Dataflow;

architecture Dataflow of Full_Adder_Dataflow is
    signal X: STD_LOGIC;
begin
    X<= (A xor B) and Cin;
    Sum<= A xor B xor Cin;
    Cout<=X or (A and B);
end Dataflow;
```

**OUTPUT:**

 

**RESULT:**

Thus the Full adder Circuit has been simulated with the truth table by using Xilinx ISE Simulator.

---

**Experiment Number:**

---

**Title of the Experiment:** FULL SUBTRACTOR

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the Full Subtractor with the tools available in Xilinx Project Navigator using VHDL.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**

c) Xilinx (ISE) simulator 9.1

d) FPGA KIT

**Procedure for doing the experiment:**

S.No	Details of the step
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

### **VHDL CODE:**


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity full_subs is
  port (a : in STD_LOGIC_VECTOR (0 to 2);
        s : out STD_LOGIC_VECTOR (0 to
1)); end full_subs;
architecture behavioral of full_subs
is begin
  process
  (a) begin
  case a is
  when "000"=> s<="00";
  when "001"=> s<="11";
  when "010"=> s<="11";
  when "011"=> s<="01";
  when "100"=> s<="10";
  when "101"=> s<="00";
  when "110"=> s<="00";
  when      others
=>s<="11"; end case;
  end process;
end behavioral;
```

### **TRUTH TABLE:**

<b>A</b>	<b>B</b>	<b>C</b>	<b>Diff</b>	<b>Borrow</b>
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



## OUTPUT:

 

## RESULT:

Thus the Full Subtractor Circuit has been simulated with the truth table by using Xilinx ISE Simulator

---

**Experiment Number:**

---

**Title of the Experiment: MULTIPLEXER & DE-MULTIPLEXER**

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the Multiplexer & De-Multiplexer with the tools available in Xilinx Project Navigator using VHDL.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**


c) Xilinx (ISE) simulator 9.1

d) FPGA KIT

**Procedure for doing the experiment:**

S.No	Details of the step
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.


**MULTIPLEXER:**

 

**TRUTH TABLE:**

SELECT INPUT		OUTPUT
S1	S0	Y
0	0	D0
0	1	D1
1	0	D2
1	1	D3

**DEMULTIPLEXER:**

 

**TRUTH TABLE:**

INPUT			OUTPUT			
A	I0	I1	D0	D1	D2	D3
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

## **VHDL CODE:**

### **MULTIPLEXER:**

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity mux4_1 is
Port ( a : in STD_LOGIC;
      b : in STD_LOGIC;
      c : in STD_LOGIC;
      d : in STD_LOGIC;
      sel : in STD_LOGIC_VECTOR(1 downto 0);
      mux_out : out STD_LOGIC);
end mux4_1;
architecture behavioral of mux4_1 is
begin
process(sel,a,b,c,d)
begin
casesel is
when "00"=>mux_out<=a;
when "01"=>mux_out<=b;
when "10"=>mux_out<=c;
when "11"=>mux_out<=d;
when others=>null;
end case;
end process;
end behavioral
```

## **DEMULTIPLEXER:**


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity demux is
  Port ( d : in STD_LOGIC;
        sel : in STD_LOGIC_VECTOR(1 downto 0);
        d_out : out STD_LOGIC_VECTOR(3 downto 0)); end demux;


architecture demux of sai is
begin
  process(d,sel)
  begin
    d_out<="0000";
    casesel is
      when"00"=>d_out(0)<=d;
      when"01"=>d_out(1)<=d;
      when"10"=>d_out(2)<=d;
      when others=>d_out(3)<=d;
    end case;
  end process;
end sai;
```

## OUTPUT:

### MULTIPLEXER:

 

### DEMULTIPLEXER:

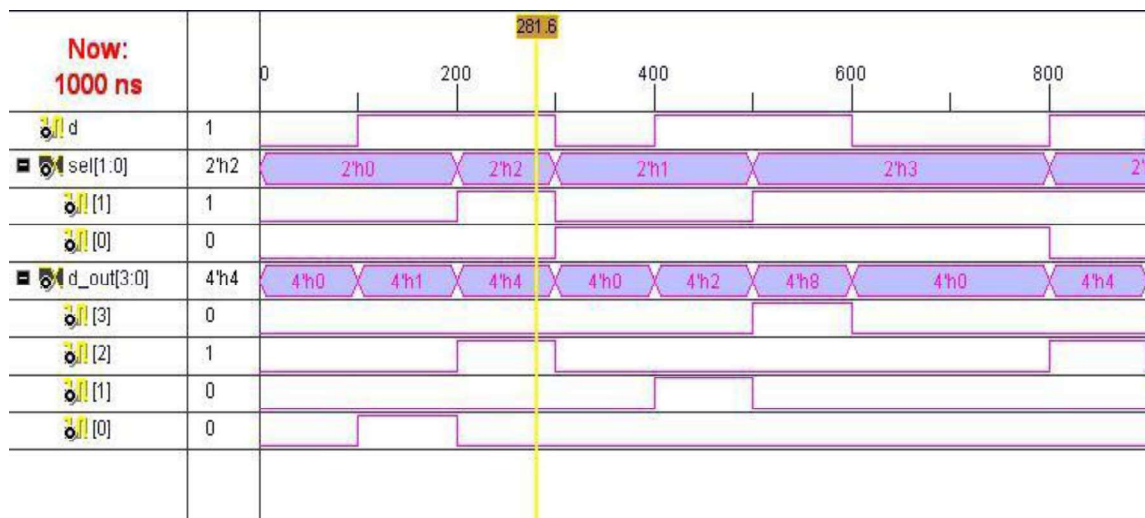

## RESULT:

Thus the Multiplexer and Demultiplexer Circuit has been simulated with the truth table by using Xilinx ISE Simulator

---

**Experiment Number:**

---

**Title of the Experiment:**    **8 BIT ADDER(RIPPLE CARRY ADDER)**

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the 8 bit Adder (RIPPLE CARRY ADDER) with the tools available in Xilinx Project Navigator using Verilog.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**


c) Xilinx (ISE) simulator 9.1

d) FPGA KIT

**Procedure for doing the experiment:**

<b>S.No</b>	<b>Details of the step</b>
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

### LOGIC DIAGRAM:

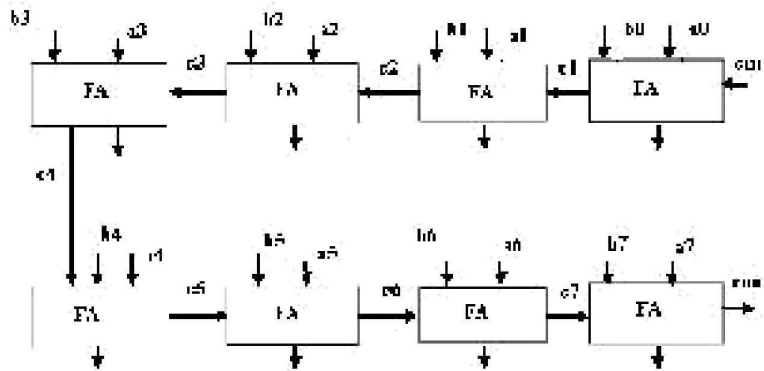


### Verilog Code:

```
module ripplecarryadder(s,cout,a,b,cin);
output[7:0]s;
output cout;
input[7:0]a,b;
input cin;
wire c1,c2,c3,c4,c5,c6,c7;
fulladd fa0(s[0],c1,a[0],b[0],cin);
fulladd fa1(s[1],c2,a[1],b[1],c1);
fulladd fa2(s[2],c3,a[2],b[2],c2);
fulladd fa3(s[3],c4,a[3],b[3],c3);
fulladd fa4(s[4],c5,a[4],b[4],c4);
fulladd fa5(s[5],c6,a[5],b[5],c5);
fulladd fa6(s[6],c7,a[6],b[6],c6);
fulladd fa7(s[7],cout,a[7],b[7],c7);
endmodule

module fulladd(s,cout,a,b,cin);
output s,cout;
input a,b,cin;
wire s1,c1,c2;
xor(s1,a,b);
xor(s,s1,cin);
and(c1,a,b);
and(c2,s1,cin);
xor(cout,c2,c1);
endmodule
```



**OUTPUT:**

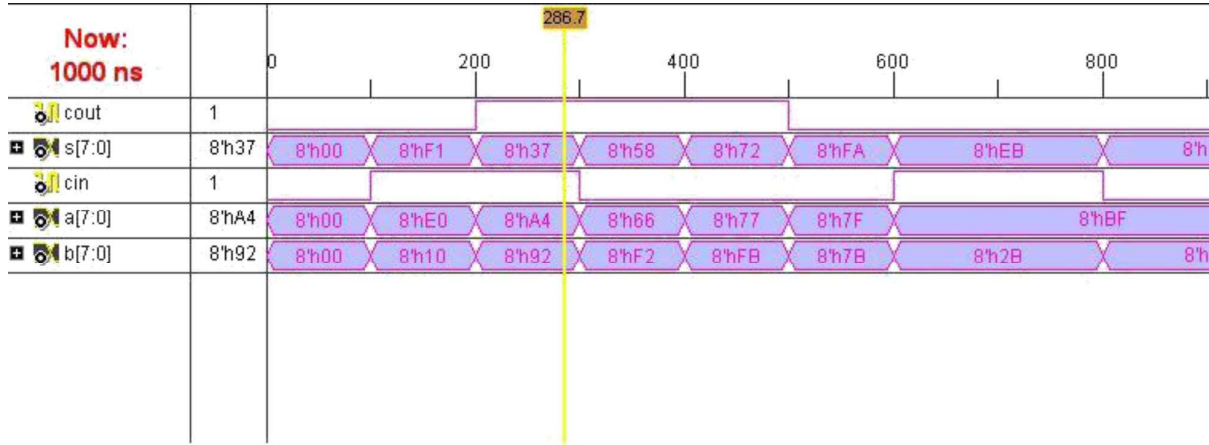

**RESULT:**

Thus the 8 Bit Adder Circuit has been simulated with the truth table by using Xilinx ISE Simulator

---

**Experiment Number:**

---

**Title of the Experiment: FLIP-FLOPS**

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the Flip-Flops with the tools available in Xilinx Project Navigator using Verilog.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**

c) Xilinx (ISE) simulator 9.1


d) FPGA KIT

**Procedure for doing the experiment:**

S.No	Details of the step
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

**LOGIC DIAGRAM:**


**JK FLIP FLOP:**

 

**TRUTH TABLE:**

Q(t)	J	K	Q(t+1)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	0


**D Flip Flop:**

 

**TRUTH TABLE:**

Q(t)	D	Q(t+1)
0	0	0
0	1	1
1	0	0
1	1	1

**T Flip Flop:**

 

**TRUTH TABLE:**

Q	T	Q(t+1)
0	0	0
0	1	1
1	0	1
1	1	0

### VERILOG SOURCE CODE: T FlipFlop

#### Behavioral Modeling:

```
+module tff(t,clk,rst, q,qb);
  input t,clk,rst;
  output q,qb;
  reg q,qb;
  reg temp=0;
  always@(posedge clk,posedge rst)
  begin
    if (rst==0) begin
      if(t==1) begin
        temp=~ temp;
      end
      temp=temp;
      q=temp;qb=~temp;
    end
    else
  end module
```

### VERILOG SOURCE CODE: JK Flip Flop

#### Behavioral Modeling:

```
module jk(q,q1,j,k,c);
  output q,q1;
  input j,k,c;
  reg q,q1;
  initial begin q=1'b0; q1=1'b1; end
  always @ (posedge c)
    begin
      case({j,k})
        {1'b0,1'b0}:begin q=q; q1=q1; end
        {1'b0,1'b1}: begin q=1'b0; q1=1'b1; end
        {1'b1,1'b0}:begin q=1'b1; q1=1'b0; end
        {1'b1,1'b1}: begin q=~q; q1=~q1; end
      endcase
    end
endmodule
```

### **VERILOG SOURCE CODE: D Flip Flop**

```
module d(q,q1,d,c);
output q,q1;
input d,c;
reg q,q1;
initial
    begin
        q=1'b0; q1=1'b1;
    end
always @(posedge c)
    begin
        q=d;
        q1= ~d;
    end
endmodule
```

### **RESULT:**

Thus the Flip Flop Circuit has been simulated with the truth table by using Xilinx ISE Simulator

---

**Experiment Number:**

---

**Title of the Experiment:    RIPPLE COUNTER**

**Date of the Experiment:**

---

**Objective :**

a) To Simulate the ripple counter with the tools available in Xilinx Project Navigator using Verilog.

b) To Implement the above with the available FPGA kit.

**Facilities Required:**

c) Xilinx (ISE) simulator 9.1


d) FPGA KIT

**Procedure for doing the experiment:**

<b>S.No</b>	<b>Details of the step</b>
1	Double click the project navigator and select the option File-New project.
2	Give the project name.
3	Select VHDL module.
4	Type your VHDL coding.
5	Check for syntax.
6	Select the new source of test bench waveform
7	Choose behavioural simulation and simulate it by Xilinx ISE simulator.
8	Verify the output.
9	Follow the instructions given to implement it with the available FPGA kit.

**LOGIC DIAGRAM:**

**4-Bit Ripple Counter:**

 

**TRUTH TABLE:**

COUNT	A0	A1	A2	A3
0	0	0	0	0
1	1	0	0	0
2	0	1	0	0
3	1	1	0	0
4	0	0	1	0
5	1	0	1	0
6	0	1	0	1
7	1	1	1	0
8	0	0	0	1
9	1	0	0	1
10	0	1	0	1
11	1	1	0	1
12	0	0	1	1
13	1	0	1	1
14	0	1	1	1
15	1	1	1	1

## VERILOG SOURCE CODE: //Structural description of Ripple Counter


```
module ripplecounter(A0,A1,A2,A3,COUNT,RESET);
  output A0,A1,A2,A3;
  input COUNT,RESET;
  //Instantiate Flip-Flop
  FF F0(A0,COUNT,RESET);
  FF F1(A1,A0,RESET);
  FF F2(A2,A1,RESET);
  FF F3(A3,A2,RESET)
endmodule

//Description of Flip-Flop

module FF(Q,CLK,RESET);

output Q;
input CLK,RESET;
reg Q;
always @(negedge CLK or negedge RESET)
if(~RESET)
Q=1'b0;
else
Q=~Q;
endmodule
```

## OUTPUT:

 

## RESULT:

Thus the 4 bit Ripple Counter Circuit has been simulated with the truth table by using Xilinx ISE Simulator