

SRI CHANDRASEKHARENDRA SARASWATHI

VISWA MAHA VIDYALAYA



DEPARTMENT OF ELECTRONICS & COMMUNICATION

ENGINEERING

COURSE MATERIAL PREPARATION

Computer Aided System Design Laboratory

Dr.R. JAYALAKSHMI

PCC20 COMPUTER AIDED SYSTEM DESIGN LABORATORY V SEMESTER

OBJECTIVES:

- To Construct RC circuits, OPAMPS, Combinational and Sequential circuits Using PSICE
- To Simulate and Implement sequential and combinational digital circuits using HDL

PSPICE: (Modelling, Design, Simulation and Analysis using Schematic / Circuit file / both)

1. Study of PSPICE
2. RC circuits – Transient and AC analysis
3. MOS Device Characterization and CMOS Inverter Characteristics – DC analysis
4. Diode based circuits (like, Rectifiers, Clampers, etc.,) – Transient, Worst-case, MC, Sensitivity, etc. analysis
5. Amplifiers and Current mirrors using BJT/MOSFET
6. Op-Amp based Wein Bridge Oscillator and DAC using sub-circuit and Analog behavioural modelling
7. Digital Circuits – Logic switches / Multiplexer / Counter HDL: (Logic Design and Simulation of Digital Circuits using VHDL / Verilog HDL / Both)
8. Study of VHDL and Verilog

9. Full Adder and Multiplexer using different Modelling / Descriptions and Concurrent and

SEQUENTIAL EXECUTION IN VHDL:

10. 8-bit Adder / Multiplier (min 4-bit) – Port Map, Generics, Technology Mapping in VHDL

11. 8-bit Counter – Bottom-up approach design and Test vector generation in Verilog HDL

12. NAND / NOR / Transmission gates using Switch level modelling in Verilog HDL

13. Design of simple sequential and combinational circuits

14. Design of ALU

15. Design of FSM and Control Unit

16. FPGA real time programming and I/O Interfacing– Waveform generation / Traffic light controller

OUTCOMES: Upon completion of the course, students will be able to:

- Construct Analog and Digital circuits and study their characteristics using PSPICE.
- Implement digital circuits using HDL TOOLS TO BE USED: LTSPICE, Mentor Graphics,

Xilinx / Equivalent

1. Study of PSPICE

INTRODUCTION TO PSPICE

Schematics are a schematic capture front-end program with a direct interface to other PSpice programs and options.

The following tasks can be performed, all in one environment, using Schematics:

- Design and draw circuits.
- Simulate circuits using PSpice.
- Analyse simulation results using the PSpice waveform viewer (Probe) Graphically characterize simulation stimuli using the fully integrated Stimulus Editor, so stimulus definitions are automatically associated with the appropriate symbols.
- Graphically characterize simulation models using the fully integrated Model Editor utility (formerly known as Parts), so model definitions are automatically associated with the appropriate symbols.
- Interface to PSpice Optimizer for analog circuit performance optimization.
- An important prerequisite for building a schematic is the availability of the necessary devices in the form of symbols. Schematic has extensive symbol libraries and include a fully integrated symbol editor for creating your own symbols or modifying existing symbols.

PROCEDURE FOR PSPICE:

SCHEMATIC File

- 1) Starting a schematic new design: Go to PSpice Students demo folder and click the SCHEMATIC icon FILE name of PSPICE students' window, select NEW and use appropriate name for PROJECT and select analog or mixed signal wizard.
- 2) Including Libraries: ADD the following libraries to the list of libraries to be used.
- 3) Selecting, Placing and editing parts: Click on the draw Menu. Select get new part on the pop up window. Select "Analog" for libraries. For example to get resistor type "R" and click Ok to place the resistor.
- 4) For Drawing Wires: Click on the draw menu and select wire and connect the circuits as per the given schematics.
- 5) For Analysis of the Schematics: Click on the Markers Menu, select the "SET UP" and select "AC SWEEP" for AC Analysis or select Transient for transient analysis, give the parameters for both analysis of timing and frequencies.
- 6) To get the output for Analysis: Click on Analysis Menu, select "Electrical Rule Check" for the net list verification and then click on Analysis Menu, select "Simulate" to see the schematics, a probe window showing the Plot of result should open-up.

PROCEDURE FOR PSPICE:

PSPICE A/D:

1) Starting a new design: Go to PSpice demo folder and click the Spice A/D. To create new Project, click the file menu and get new text file and use an appropriate value name for the text file and save as .cir in the working directory.

2) Including Libraries: Type Ctrl+G and click to add the libraries, and then click the required apparatus containing libraries for experiments then Click Ok.

3) Creating a Net List: Create a circuit in a text file with list of all the components and node connections called the Net List.

4) Simulation of PSpice A/D Run a simulation on the Net List and perform the request Analysis. Select the Type of Analysis (AC or Transient).

5) To get the Output for PSpice A/D: Open the Working directory and click the binary data file. Click the waveform icon in the PSpice A/D window. The output graph should open up.

2. RC circuits – Transient and AC analysis

AIM:

To verify the AC AND TRANSIENT ANALYSIS of a Low Pass and High Pass filter RC circuits by using the PSPICE software.

LPF AC ANALYSIS:

- Understand the characteristics of physical model of LPF and what kind of circuit needed.
- Place the resistor, capacitor, input source (AC/DC) ground source and complete the circuit by drawing wire to connect them.
- Place the voltage convertor at required place.
- Click on the set-up analysis. Choose the AC sweep option and set frequency, magnitude •

Simulate circuit and obtain graphical response curve for AC analysis.


LPF Transient Analysis:

- Understand the physical characteristics of LPF and what kind of i/p sources needed for circuit
- Using resistor, capacitor, input source (sine, pulse) etc ground source and other elements complete the circuit by connecting them with wire
- Click on setup analysis, choose transient analysis and set appropriate value for the transient parameters and click Ok
- Set the magnitude value and other parameter value for i/p source.


- Simulate the circuit and obtain the graphical curve for transient analysis.

CIRCUIT DIAGRAM

LPF Analysis

 


HPF Analysis

 


AC Analysis

Low pass filter

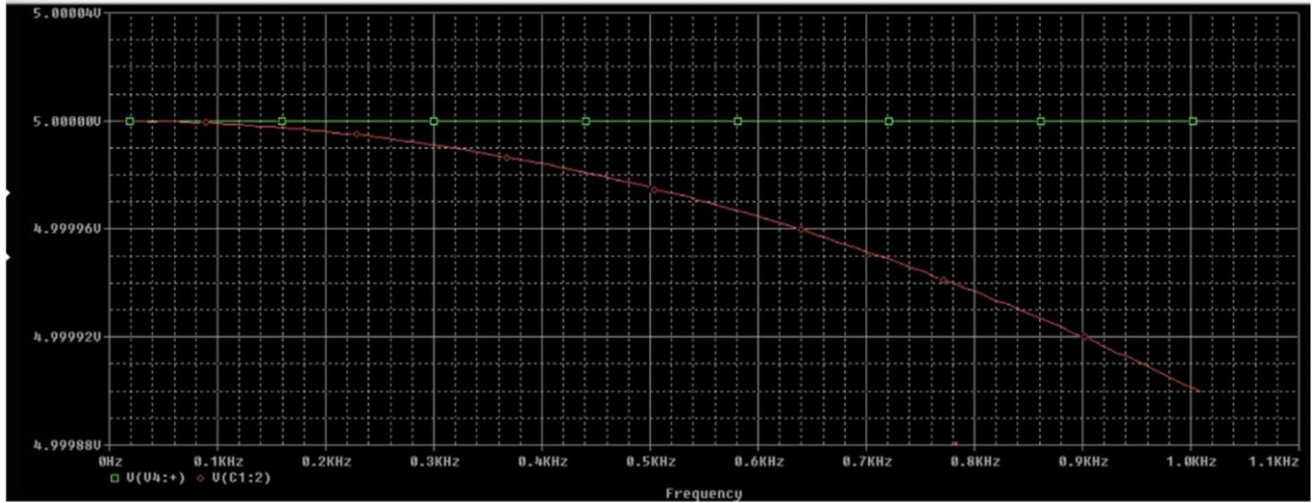


High Pass Filter

 


Transient Analysis

Low Pass Filter

 

High Pass Filter

 

Result:

Thus, the circuit for both HPF and LPF were designed and corresponding AC and transient response curves were obtained

3. CMOS Inverter Characteristics – DC analysis

Aim

To verify the DC AND TRANSIENT ANALYSIS OF CMOS INVERTER circuits by using the PSPICE software.

Procedure:

Make the connections as per the Circuit Diagram


Give appropriate names and values to elements

Set the Values for DC analysis


Set the Values for Transient Analysis

Simulate the circuit and analyse the results.


Circuit Diagram

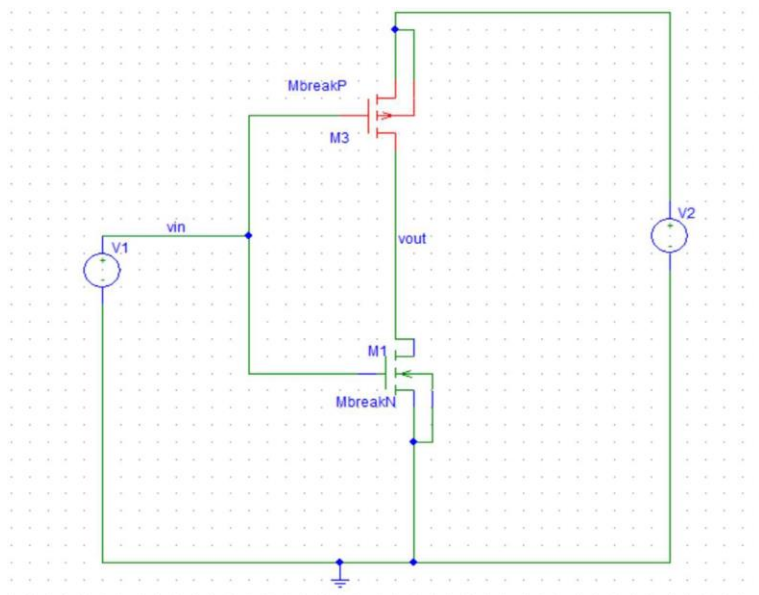

DC Sweep Analysis

 

Transient Analysis

 

Result: -

Thus, the DC and transient analysis of CMOS inverter have been verified.


4. Diode based circuits – Rectifiers and Clampers

POSITIVE AND NEGATIVE CLAMPER


Aim:

To verify the characteristics of a POSITIVE AND NEGATIVE CLAMPER circuits by using PSPICE software.


Circuit diagrams:

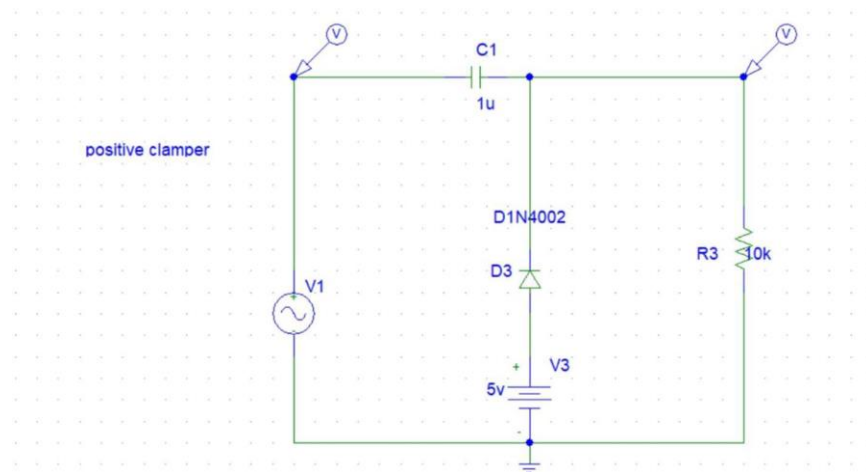


Negative Clamper

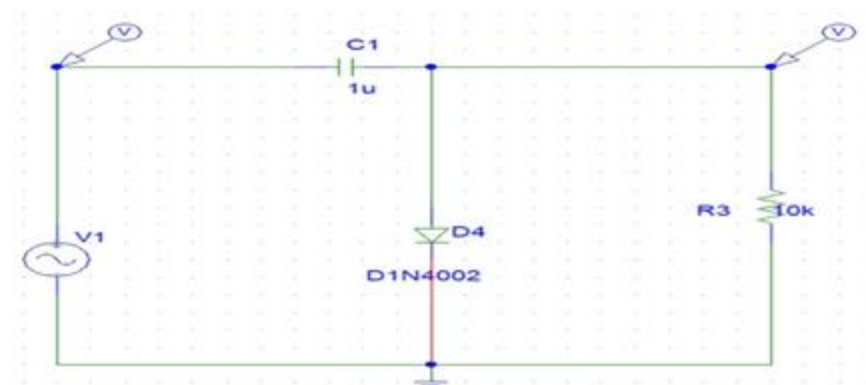

POSITIVE CLAMPER

 

NEGATIVE CLAMPER

 

Result:



Thus, the characteristics of a POSITIVE AND NEGATIVE CLAMPER circuits by using PSPICE software is verified.

Aim:



To Verify the characteristics of Half wave rectifier and Full wave Rectifier – Bridge Rectifier circuits using Pspice simulation Software.

Circuit Diagrams:

  Half wave Rectifier: Circuit and Waveform



Bridge Rectifier: Circuit and Waveform

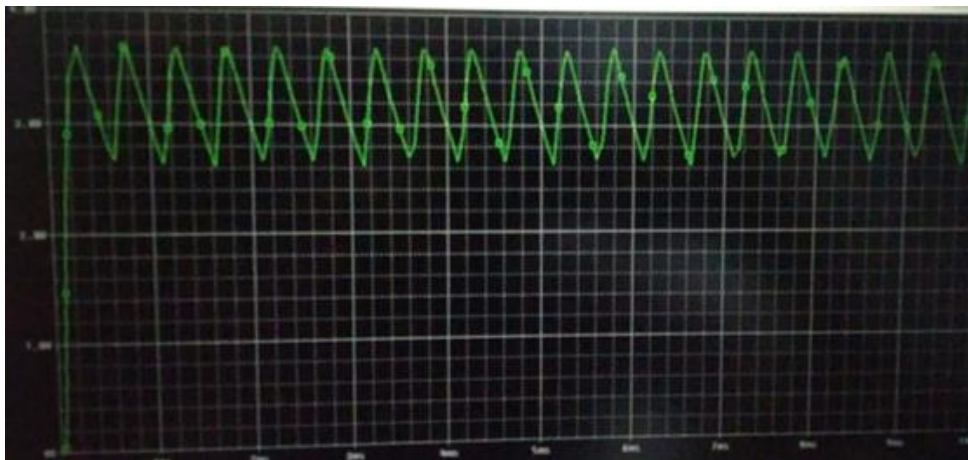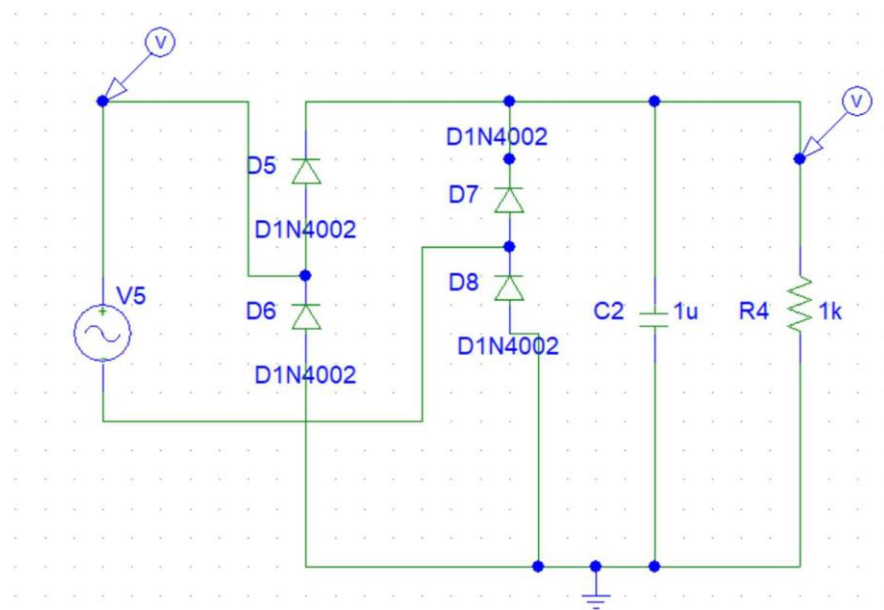

Result:

Thus, the Characteristics Of Half Wave And Full wave Rectifier has been verified using Pspice software.


5. Amplifiers and Current mirrors using BJT/MOSFET

Transient Analysis of Common Emitter PNP Amplifier


Aim:

To verify the transient analysis of common emitter PNP amplifier by using the PSPICE software.

Circuit diagram:

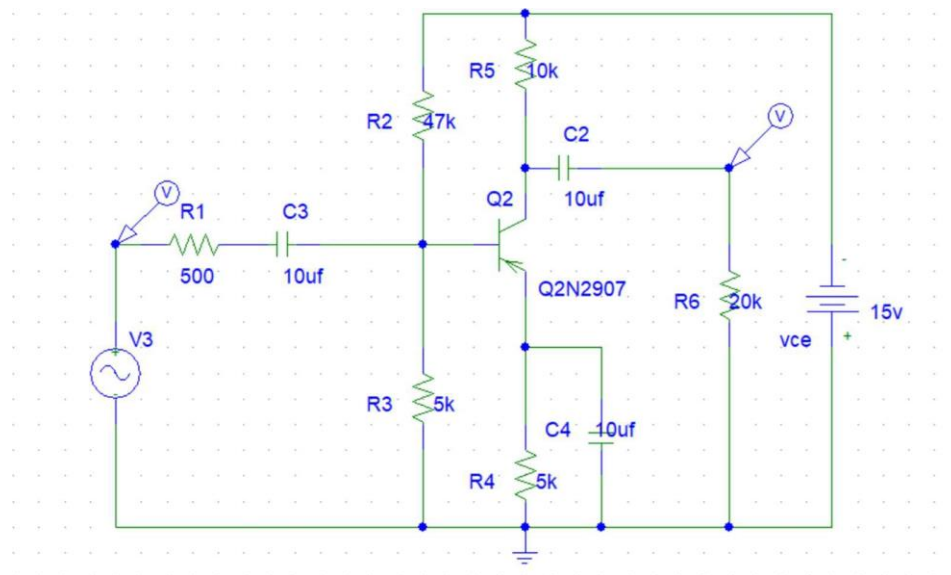

Waveform:

 

Result:


Thus, the transient analysis of common emitter pnp amplifier have been verified.

Input and Output Characteristics of MOSFET


Aim

To verify the input and output characteristics of MOSFET by using the PSPICE software.


Circuit Diagram

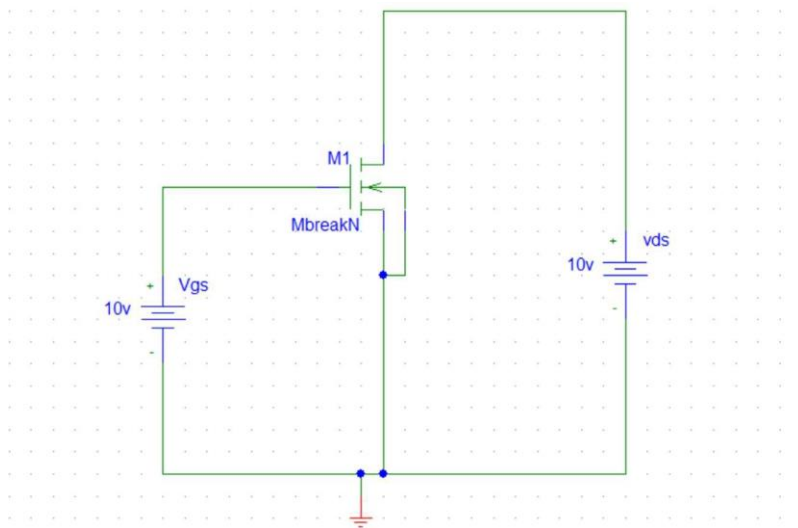

Input Characteristics

 

Output Characteristics

 

Result:


Thus, the input and output characteristics of BJT have been verified.

6. Op-Amp based Wein Bridge Oscillator


Aim:

To verify the characteristics of a WEIN BRIDGE OSCILLATOR circuit by using PSPICE software.

Circuit Diagram:

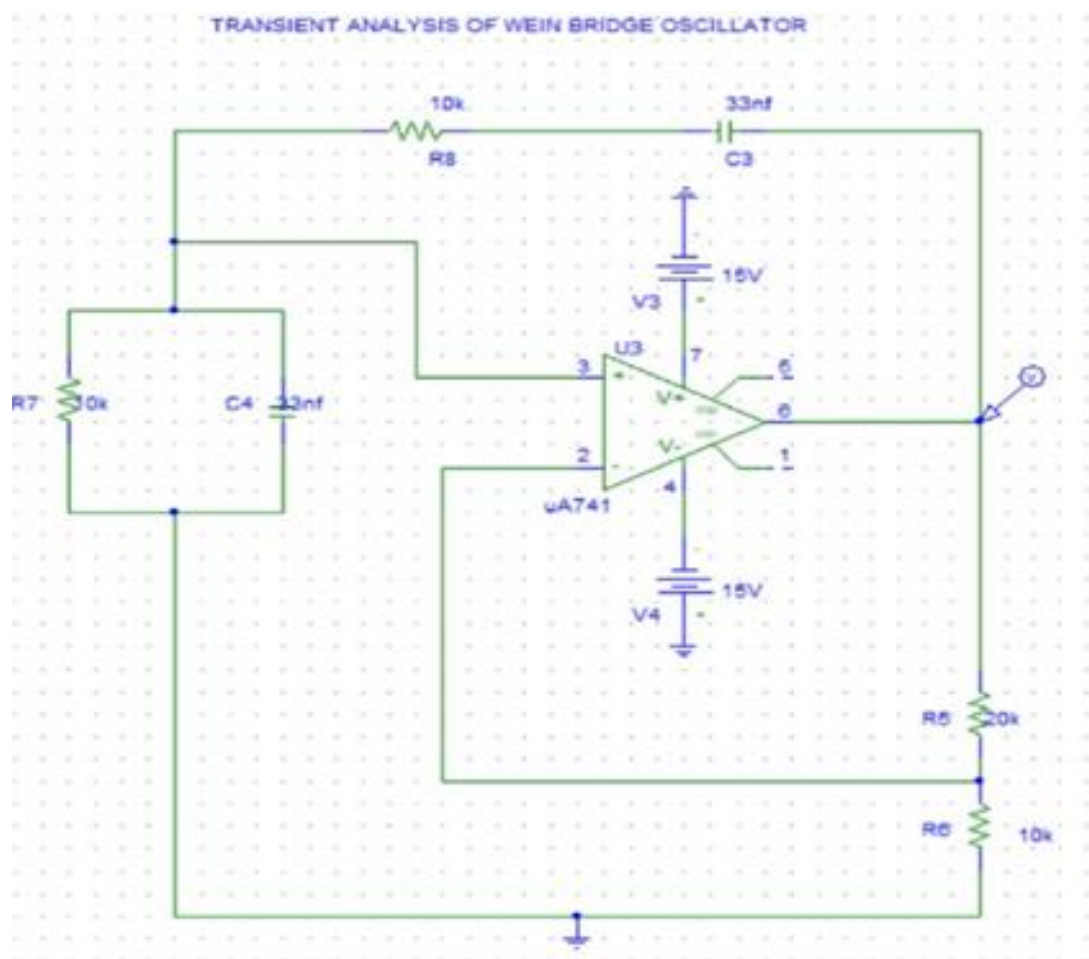

Waveform:

 

Result:

Thus, the characteristics of wein bridge oscillator have been verified.

7. Study of VHDL and Verilog

AIM:

To study the various VHDL commands.

DESCRIPTION:

1. Getting started with Xilinx: Start Xilinx ISE from the start menu by selecting start programs,

Xilinx ISE 14.7 project navigator

2. Creating a new project

A project in ISE is a collection of all files that are necessary to create and download a design to the selected device

1. To create a new project, select file/new project

2. In the new project wizard dialog box, type the desired location in the project location field

3. Use the pull-down arrow to select HDL from the top-level module type field. Click in the field to access the pull-down list and click next

4. In the new project wizard device and design flow dialog box, use the pull-down arrow to select value for each property name

Service family: Spartan 3E

Device: XC3S500E

Package: CPG132

Speed: -4

Synthesis tool: XST (VHDL/Verilog)

Simulator: ISE (VHDL/Verilog)

Generated simulation Language: VHDL

5. Click next

6. Click new source in new project wizard create a new source dialog box to add one new source to your project. Click VHDL module as the source type. Type in file name, click next

7. Click new source next in the define VHDL source dialog box. Click next in the new project wizard add existing source dialog box and click finish.

3. Synthesize a program:

To synthesize a program or to check syntax, in the process window click the synthesis XST+ symbol and expand it then double click the syntax. Tick mark will appear in green colour when no errors are detected in the program.

4. Simulate a program:

1. Click create new source in process window to open new source dialog box, before that select behavioural implementation in the source window list icon and in the new source dialog box select text bench waveform and type the file name and click next.

2. Select the source for which the test bench waveform to be generated from “Select” window and then click next and click finish the test bench waveform file was added to project
3. Click OK to accept the default timing constraints. HDL bench opens within the project navigator frame work
4. Set the I/p values for the project by clicking on I/p waveforms by marking them low or high
5. Then save file and close waveform editor
6. To simulate the program select text, gates flow in source window. Click + beside the ISE simulator to expand the library hierarchy in process window
7. Waveform window: Display the output waveform for specification.

5. Implement design:

1. Click create new source in process window to open new source dialog box and select implementation constraints files and click next.
2. Select the source for which the implementation constraint file to be written from select window.
3. Select gates-VCF in the source window click then + beside user constraints to expand the hierarchy in the process.
4. Double click implement design in the process window.

Result: Thus the study of VHDL and its commands has been done.

8. IMPLEMENTATION OF FULL ADDER

AIM:

To verify and implement full adder using Xilinx ISE simulator software.

SYSTEM REQUIREMENTS: Xilinx ISE simulator software, PC with High configuration

ALGORITHM FOR FULL ADDER:

1. Select a new project
2. Declare the entity full adder and also declare the i/p and o/p variables
3. Begin the architecture data flow of full adder
4. Addition is performed and sum is given by $a\text{-in} \oplus B\text{-in} \oplus \text{carry}$, and carry is given by $(a\text{-in} \text{ and } b\text{-in}) \text{ or } (b\text{-in} \text{ and } c\text{-in}) \text{ or } (c\text{-in} \text{ and } a\text{-in})$
5. Find the architecture dataflow.

Synthesize the program and create test bench waveform and then simulate the program to predict output.

FULL ADDER:

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity full_adder is

Port (a : in STD_LOGIC; b : in STD_LOGIC;

c : in STD_LOGIC; carry : out STD_LOGIC; sum : out STD_LOGIC);

end full_adder;

architecture Behavioral of full_adder is


begin

sum <= a xor b xor c;

carry <= (a and b) or (b and c) or (c and a);

end Behavioral;

Output:

 

RESULT:

Thus, the Full adder Circuit has been simulated with the truth table by using Xilinx ISE Simulator.

9. IMPLEMENTATION OF 8 BIT ADDER

AIM:

To Simulate the 8-bit Adder (RIPPLE CARRY ADDER) with the tools available in Xilinx Project Navigator using Verilog.

SYSTEM REQUIREMENTS:

Xilinx ISE simulator software

ALGORITHM:

Double click the project navigator and select the option

1 File-New project.

2 Give the project name.

3 Select VHDL module.

4 Type your VHDL coding.

5 Check for syntax.

6 Select the new source of test bench waveform and choose behavioural simulation and simulate it by Xilinx ISE simulator.

7 Verify the output.

Program

```
module ripplecarryadder(s,cout,a,b,cin);
```

```
output[7:0]s;
```

```
output cout;
```

```
input[7:0]a,b;
```

```
input cin;
```

```
wire c1,c2,c3,c4,c5,c6,c7;
```

```
fulladd fa0(s[0],c1,a[0],b[0],cin);
```

```
fulladd fa1(s[1],c2,a[1],b[1],c1);
```

```
fulladd fa2(s[2],c3,a[2],b[2],c2);
```

```
fulladd fa3(s[3],c4,a[3],b[3],c3);
```

```
fulladd fa4(s[4],c5,a[4],b[4],c4);
```

```
fulladd fa5(s[5],c6,a[5],b[5],c5);
```

```
fulladd fa6(s[6],c7,a[6],b[6],c6);
```

```
fulladd fa7(s[7],cout,a[7],b[7],c7);
```

```
endmodule
```

```
module fulladd(s,cout,a,b,cin);
```

```
output s,cout;
```

```
input a,b,cin;
```

```
wire s1,c1,c2;
```

```
xor(s1,a,b);
```

```
xor(s,s1,cin);
```


```
and(c1,a,b);
```

```
and(c2,s1,cin);
```

```
xor(cout,c2,c1);
```

```
endmodule
```

Output Waveform:

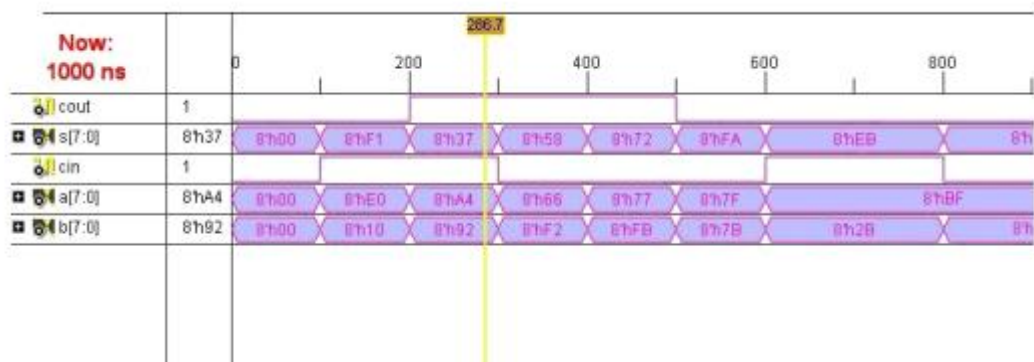

RESULT:

Thus the 8 Bit Adder Circuit has been simulated with the truth table by using Xilinx ISE

Simulator.

10. RIPPLE COUNTER

Aim:

To Simulate the ripple counter with the tools available in Xilinx Project Navigator using Verilog.

Facilities Required:) Xilinx (ISE) simulator 14.1

Procedure:

Double click the project navigator and select the option

1 File-New project.

2 Give the project name.

3 Select VHDL module.

4 Type your VHDL coding.

5 Check for syntax.

6 Select the new source of test bench waveform

Choose behavioural simulation and simulate it by Xilinx ISE simulator.

7 Verify the output.

VERILOG SOURCE CODE: //Structural description of Ripple Counter

```
module ripplecounter(A0,A1,A2,A3,COUNT,RESET);
```

```
output A0,A1,A2,A3;
```

```
input COUNT,RESET;
```

```
//Instantiate Flip-Flop
```

```
FF F0(A0,COUNT,RESET);
```

```
FF F1(A1,A0,RESET);
```

```
FF F2(A2,A1,RESET);
```

```
FF F3(A3,A2,RESET)
```

```
endmodule
```

```
//Description of Flip-Flop
```

```
module FF(Q,CLK,RESET);
```

```
output Q;
```

```
input CLK,RESET;
```

```
reg Q;
```

```
always @(negedge CLK or negedge RESET)
```

```
if(~RESET)
```


Q=1'b0;

else

Q=(~Q);

endmodule

Output Waveform:

 

RESULT:

Thus the 4 bit Ripple Counter Circuit has been simulated with the truth table by using Xilinx

ISE Simulator.